

Basic EMI Pre-Compliance and Troubleshooting Techniques

최 회 광, Field Application Engineer

Overview

- Basic EMI Measurements and the LISN
- Common and Differential Noise Sources
- EMI Pre-Compliance Analysis Using Simulation Models
- Layout Considerations
- Field Probes, Signal Splitters and Simple Current Probes
- An Extensive Troubleshooting Example Case History


Foreword

If you work with Power Electronics, sooner or later you will need to know something about EMI. It is better to learn about it sooner and prepare for the day when you may have to solve a difficult problem. Often the problems will not happen at the most convenient time nor will you have the luxury of extended time to learn how to solve the problem. If you begin to think about it early in the design phase and design for it, you will develop tools that will someday allow you to respond quickly and solve the problem or recognize the problem before it becomes one. I hope you enjoy the material.....


What Is EMI?

- EMI stands for “Electromagnetic Interference” and it has been used to describe many different types of noise phenomena observed in modern power electronic systems in use today.
- The term “interference” is used somewhat loosely today. Interference means that one piece of equipment’s actual operation is disrupted by either another piece of equipment or an external signal source. Actual interference is not usually implied by the term EMI unless describing a prevention device, method or test.
- The two basic types of EMI are:
 - Radiated EMI; measured in the far-field using antennas
 - Conducted EMI; measured at the power entry port using a line impedance stabilization network (LISN)
- There are two general categories of Conducted EMI (the focus of this seminar):
 - Differential-Mode Noise (sometimes referred to as Normal Mode)
 - Common-Mode Noise

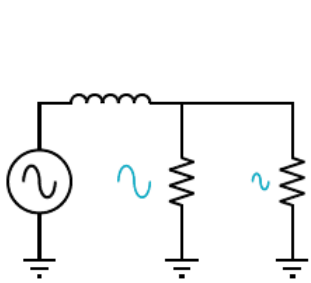
How is EMI coupled? There are four basic noise-coupling mechanisms in electrical systems



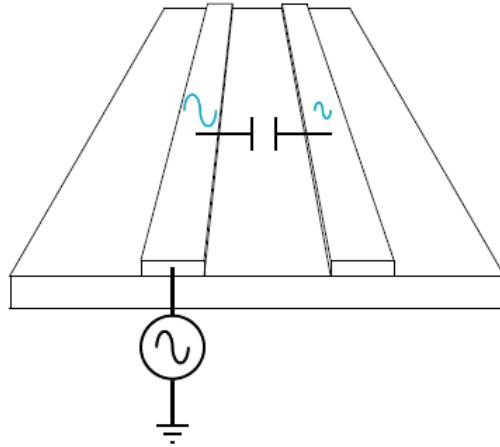
Conductive
caused by direct
contact with metal
conductors (ripple or
grounding issues)



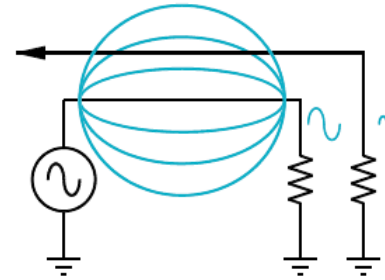Capacitive
caused by fast-
changing voltages
applied to
capacitance between
conductors




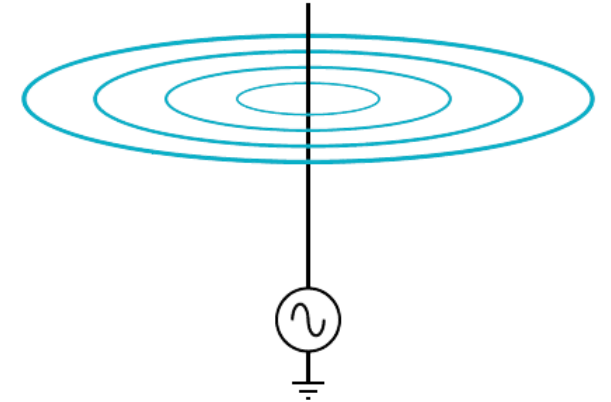Inductive
caused by fast-
changing currents
flowing in a loop
(transformer action)




Radiated
caused by far-field
electromagnetic
coupling (antenna
effect)

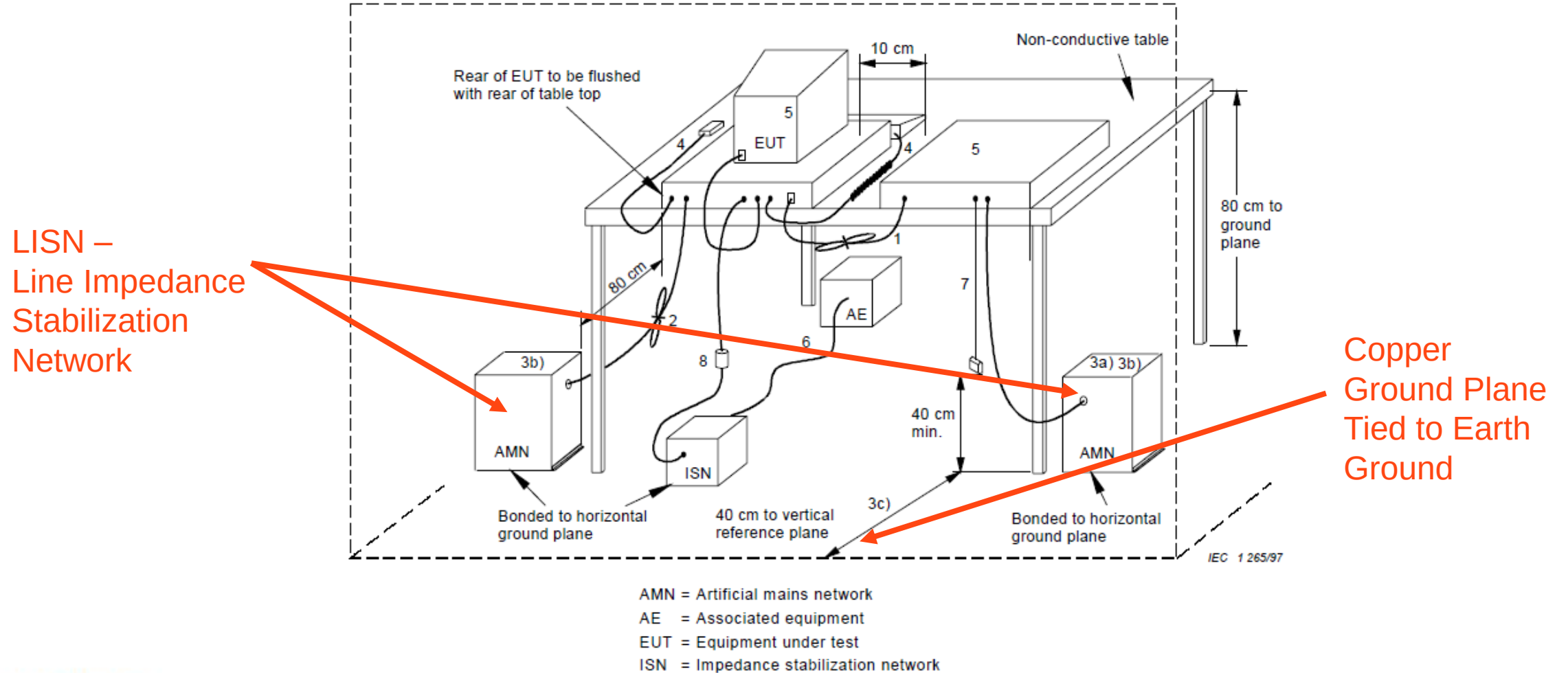
How is conducted EMI measured in commercial equipment?



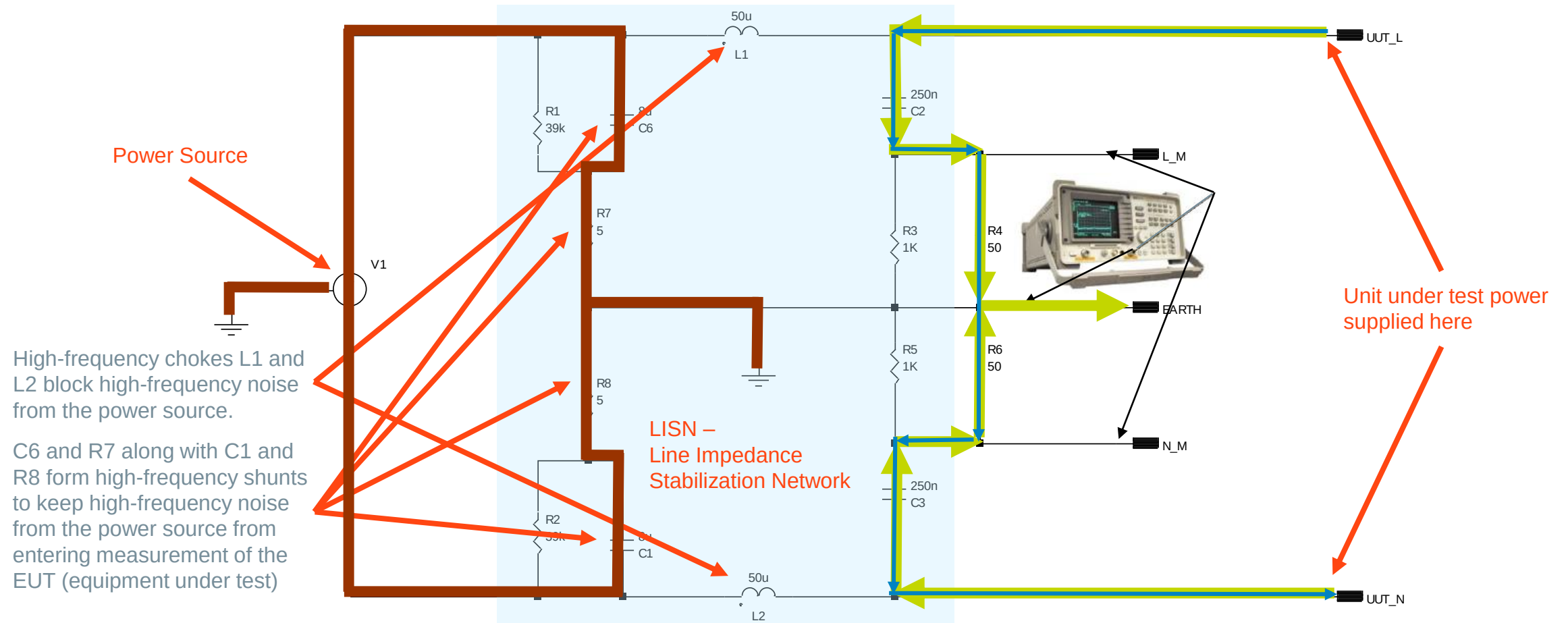
The Line Impedance Stabilization Network (commercial products)



The LISN impedance plot (simulated)

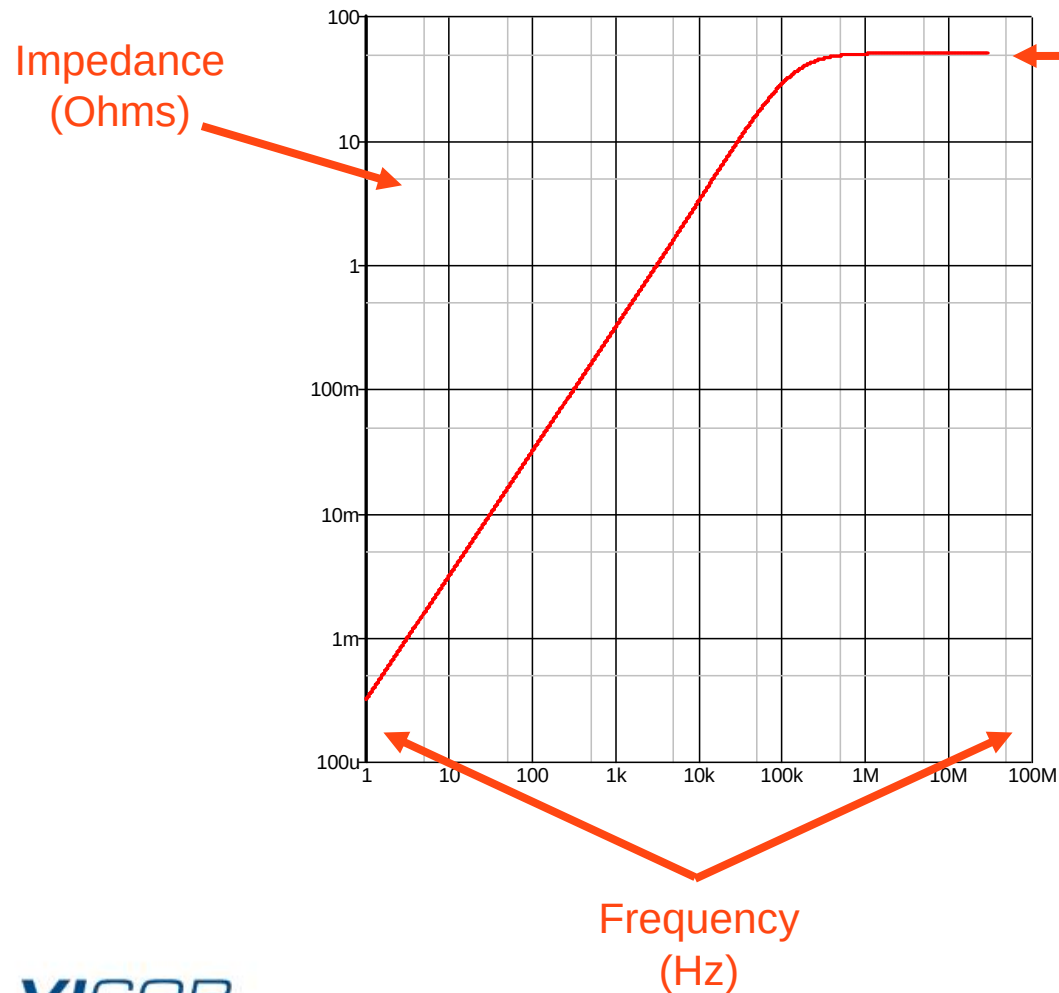

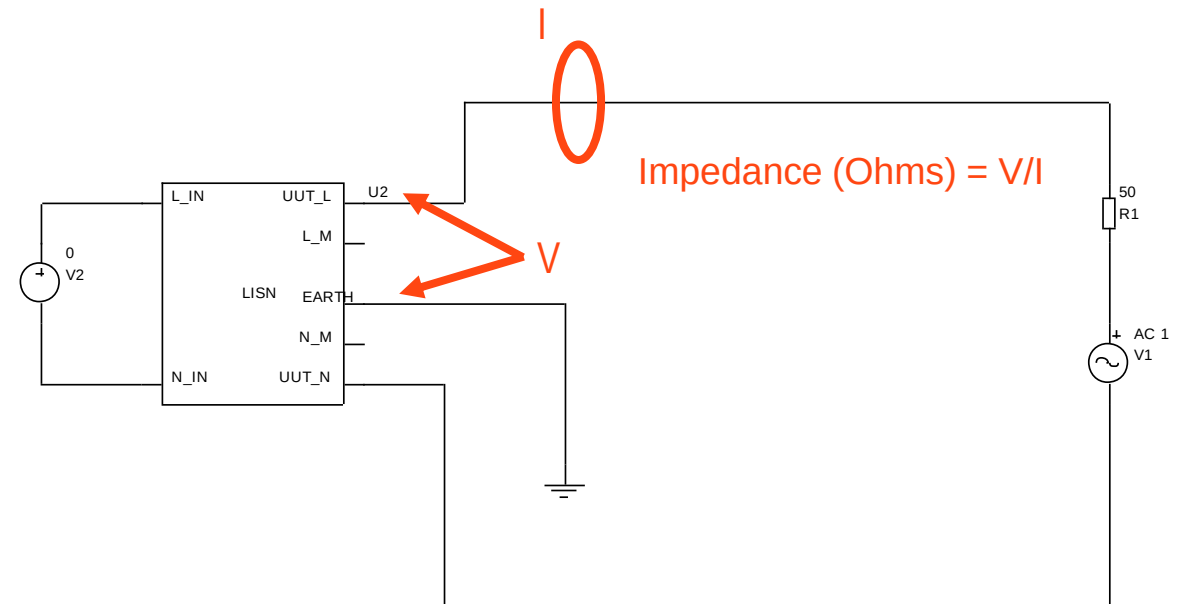Impedance approximates 50 Ohms from 150kHz to 30MHz, the measurement standard for conducted EMI. The LISN will vary depending on the measurement standard but the goal is a flat impedance in the area of interest



Measurement Filters

There are several measuring-filter techniques that you should know about:

Peak Detection

This method is the fastest of all EMI scans. It also generates the highest amplitude results.

An envelope detector is employed that can respond very quickly to amplitude changes in the envelope but without the ability to track the instantaneous value of the input signal.

Quasi-Peak Detection

This detection method is a form of weighted averaging that has a fast rise-time constant but a slow fall-time constant.


Narrow duty cycle signals will measure a lower value than peak but as frequency or duty cycle increases, the measured value will start to approach peak detection. Quasi-Peak detection takes the longest of all EMI sweeps. Quasi-Peak Detection has higher limits to allow for an “annoyance factor” of the offending signal.

Average

This method is peak detection followed by a filter with a bandwidth that is lower than the resolution bandwidth.

The result is that the higher frequency peaks get averaged to a lower value. Average detection is slower than peak but faster than quasi-peak.

Measurement Flow

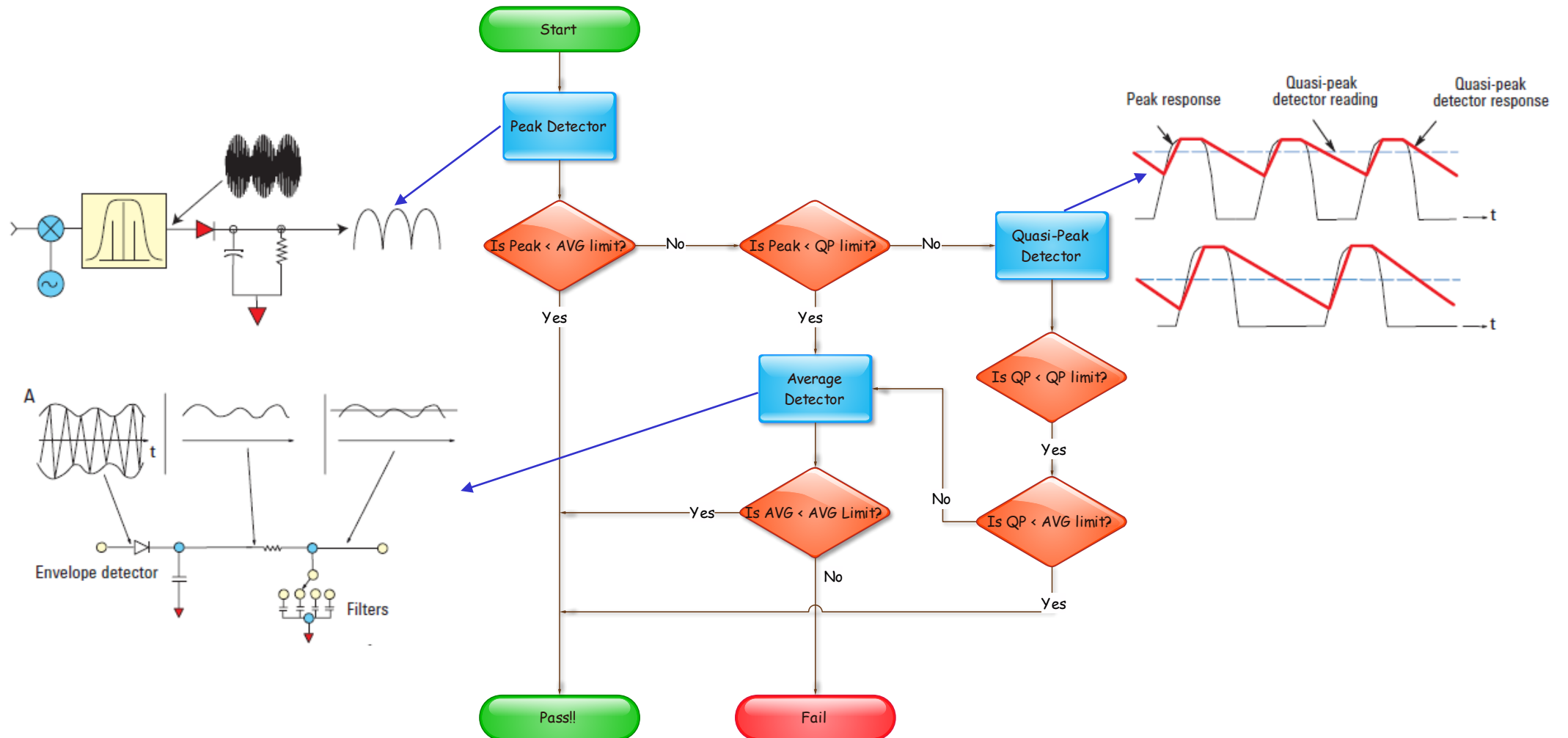


Differential-mode noise (A.K.A. normal mode)

- Differential-mode noise is sometimes referred to as Normal-Mode noise. There is a good reason for this. It results from an applied voltage differential (of opposite polarity) between the noise source and the noise return.
- It can be caused by any or all (hopefully not!) of the four coupling methods previously discussed
- Normal circuit operation is also differential in nature
- Differential noise requires only two wires or a single wire and ground
- Differential-noise currents flow in opposite directions in input feeds or AC line and Neutral
- Input voltage ripple, output voltage ripple are common examples of differential-mode noise
- Differential noise appears in all forms of power feeds: both two- and three-wire feeds

Differential-mode noise ideal CCM buck converter model SIMPLIS

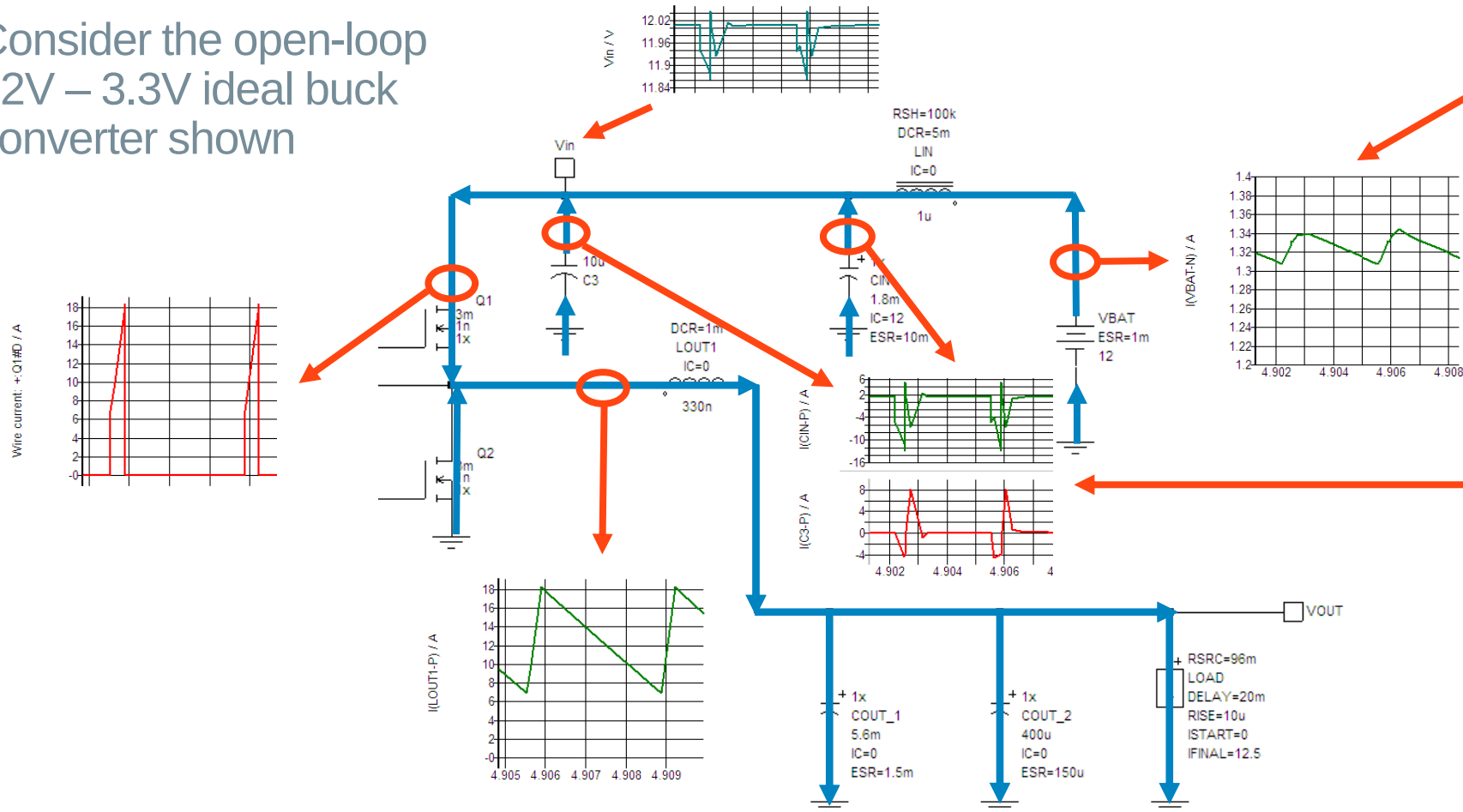Consider the open-loop 12V – 3.3V ideal buck converter shown




This ripple current is responsible for the differential-mode EMI that will be measured at the LISN.

We are concerned about these ripple currents, as they are responsible for the ripple voltage measured at the node V_{in} . This ripple voltage is the source for the differential-mode EMI that occurs at the fundamental as well as the much of the harmonic content.

Differential-mode noise ideal buck converter

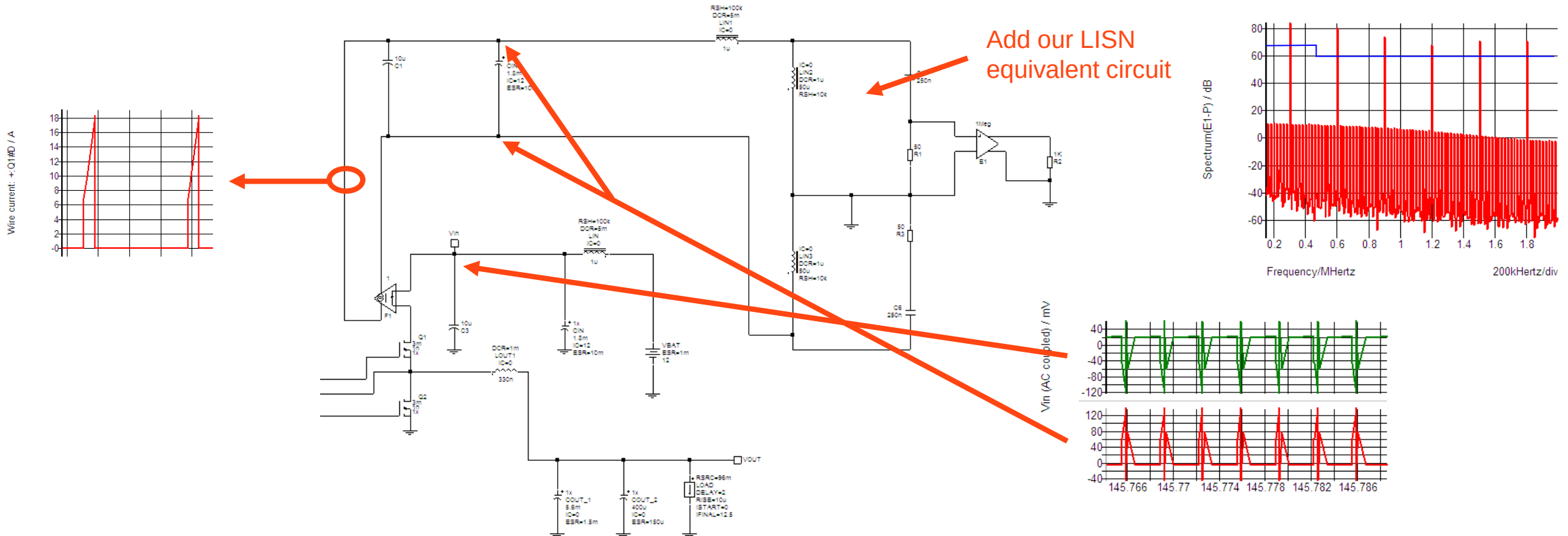
To generate the noise model, we modify the circuit as shown below:




Common-mode noise

- Common-mode noise always flows in the same direction in both input feeds (L and N) from an applied voltage between those common lines and earth ground (chassis, baseplate, test equipment, etc.)
- It can be most difficult to determine the path since it can involve virtually any equipment connected to earth ground.
- Earth ground or a three-wire system with an isolated ground is required.
- Non-isolated DC-DC Converters need not have much consideration for common-mode noise (sometimes!!).
- Test equipment can be very vulnerable based on the type of circuitry being measured.
- Isolated converters that connect output (-) to earth ground will have common mode + differential-mode ripple at the output.
- Common-mode noise can cause problems with non-isolated DC-DC converters if grounded test equipment has high common-mode noise flowing between them.

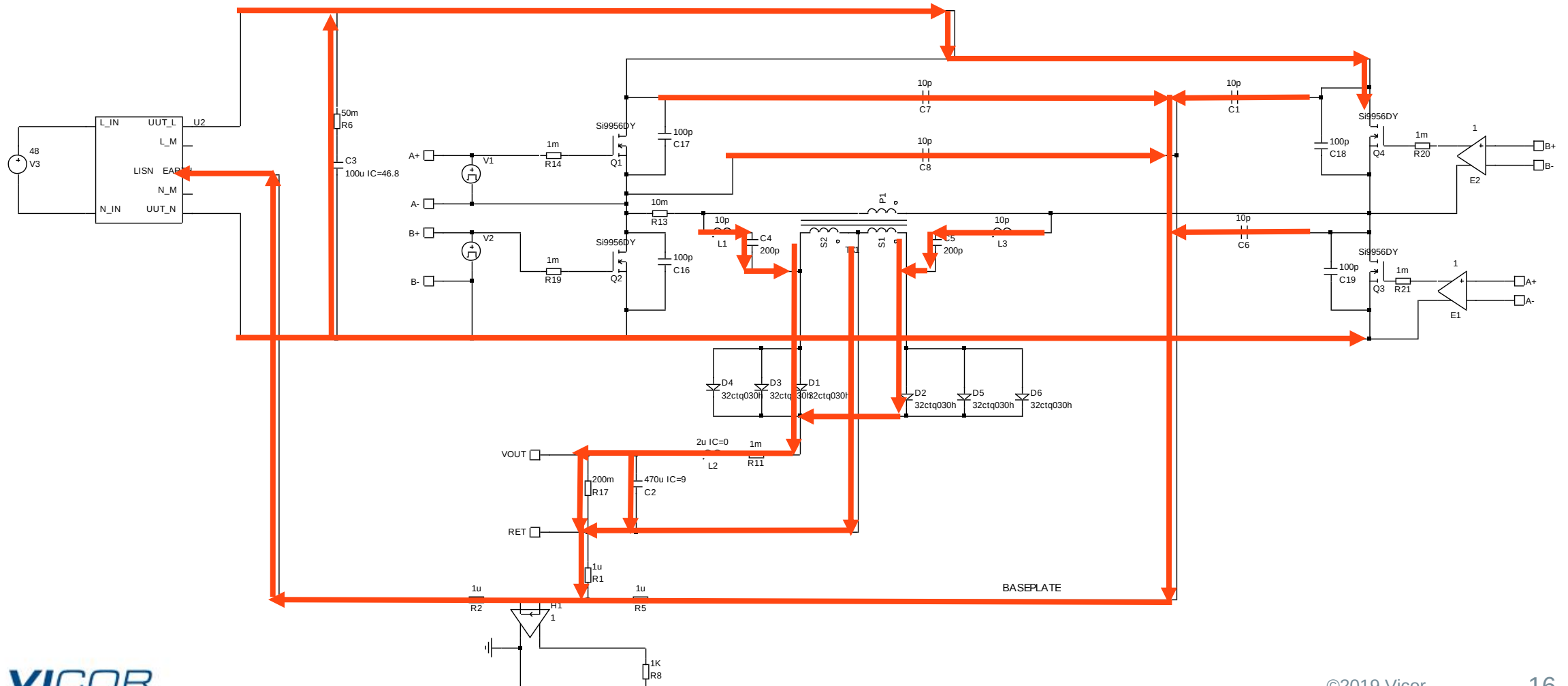Common-mode noise origin – isolated full-bridge topology




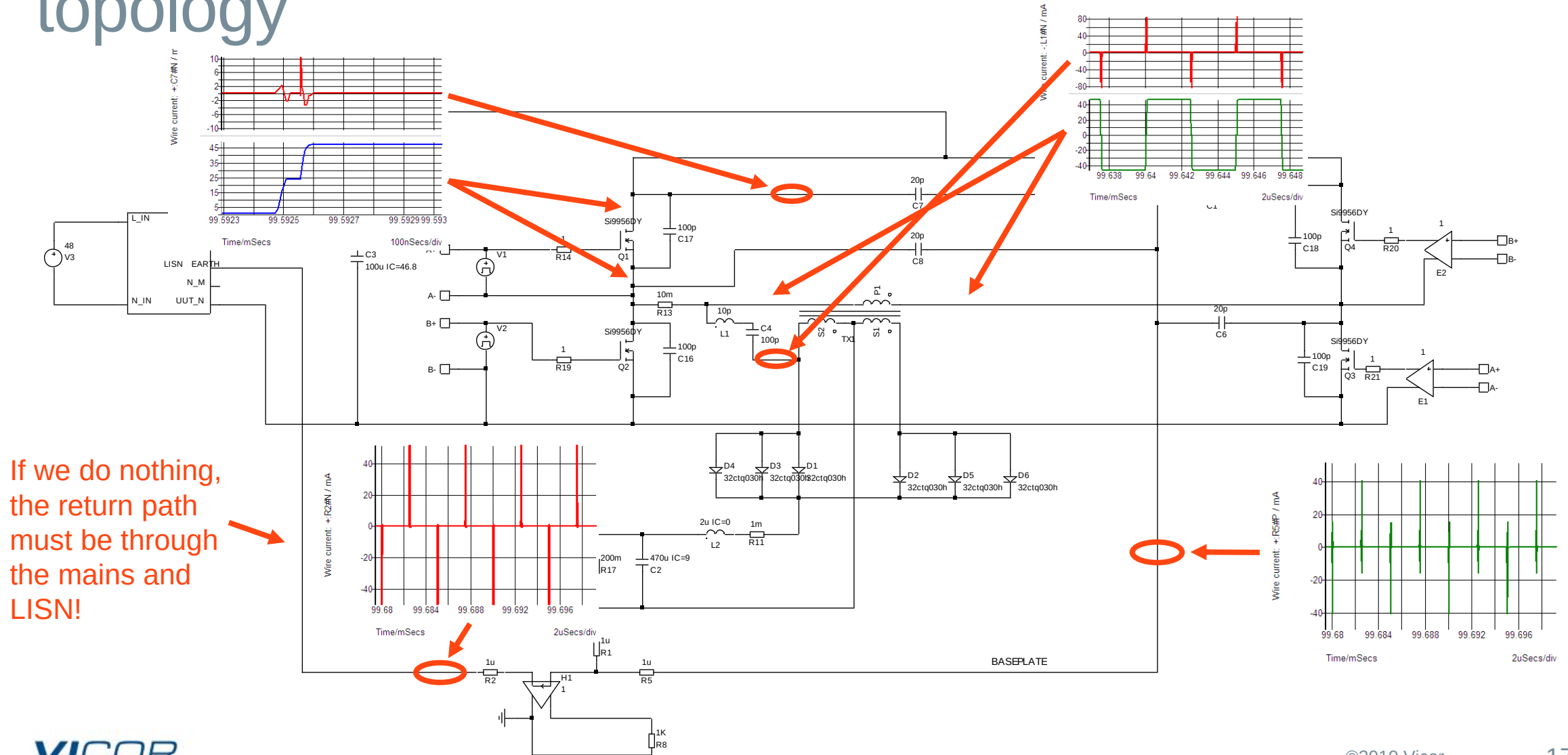Common-mode noise origin – isolated full-bridge topology



Common-mode noise origin – isolated full-bridge topology

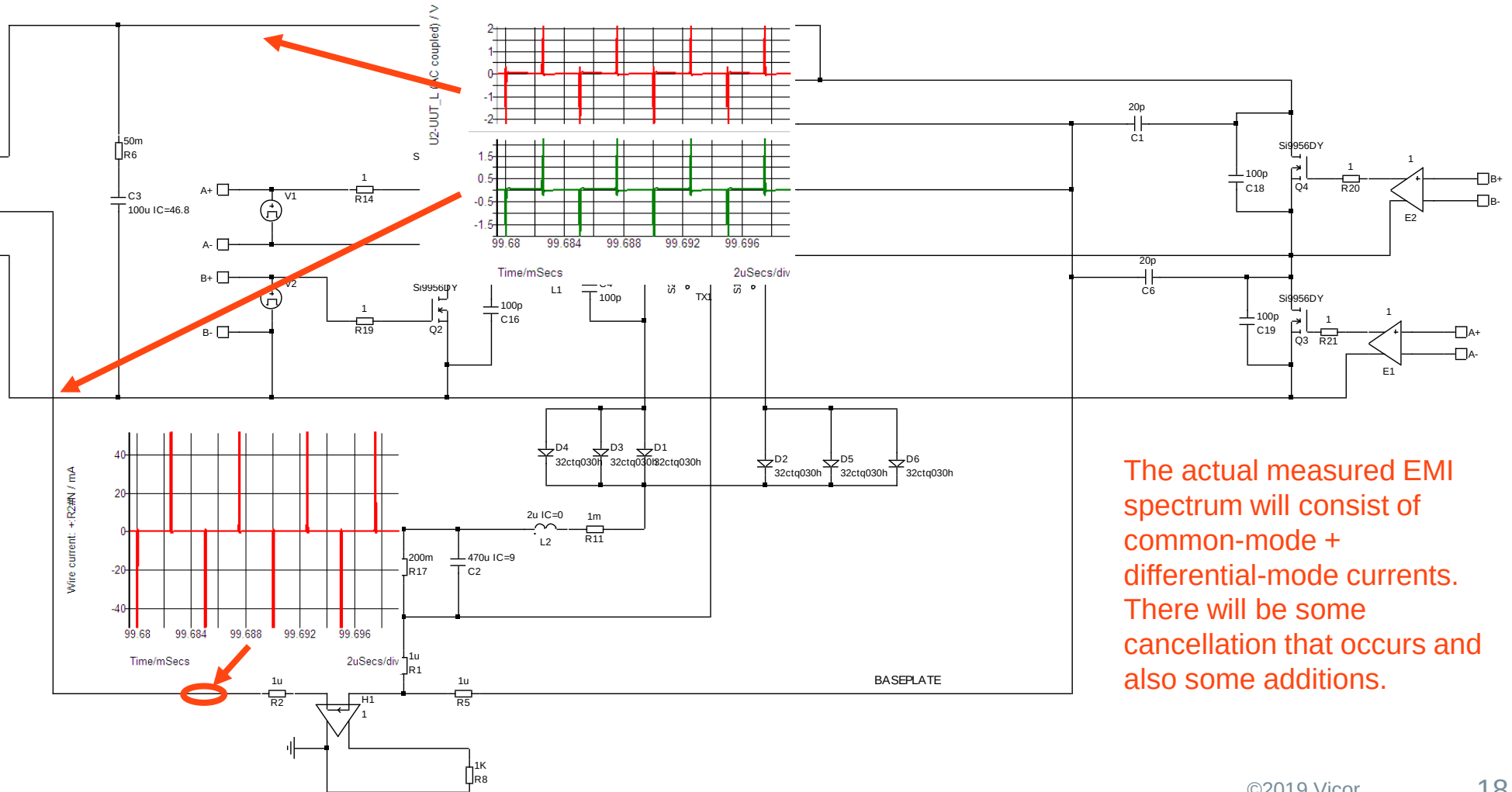
The current that passes through the LISN is the common-mode voltage measured from each line to ground divided by the LISN impedance. The common-mode voltage is the source for the common-mode portion of the EMI.



The actual measured EMI spectrum will consist of common-mode + differential-mode currents. There will be some cancellation that occurs and also some additions.


When does a buck regulator generate common-mode noise?

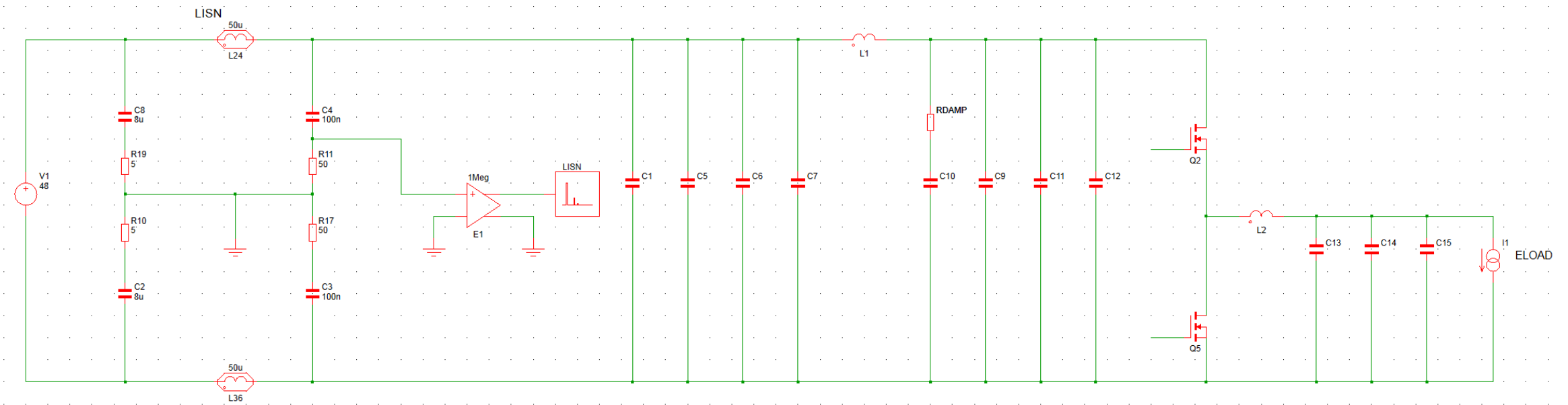- Consider the simplified Buck regulator circuit shown below connected to an electronic load
- It is powered from a LISN and set up to measure EMI. Can anyone find a common-mode EMI source?



When there is parasitic capacitance to earth ground

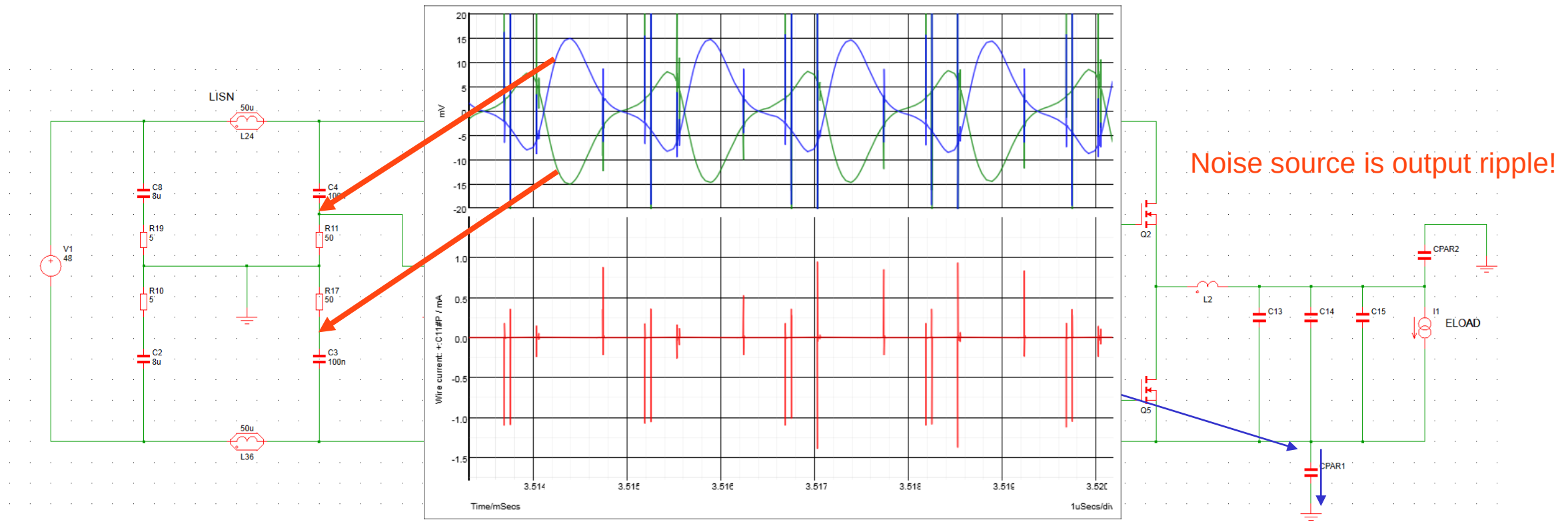Voltages at LISN that are in phase with respect to earth are common mode, out of phase are differential-mode EMI




Current through parasitic capacitance shows up at LISN as in phase voltages when measured across each 50 Ohm port to earth ground!


Layout Matters!

- Up to now, we have been simulating and discussing ideal layout filters. No layout is ideal. Most layouts are a compromise as there are many resources requiring the PCB area.
- Parasitic inductance will limit the high-frequency performance of capacitors when it appears as ESL!
- The layout can make your filter require more stages if it is not done to optimize the performance of the filter.
- Two-sided PCBs without a dedicated ground plane can be the most difficult to achieve optimum filtering.
- You can also model inductance and resistance of each interconnecting via and trace.
- Extraction of parasitic inductance and resistance is very important to understand potential EMI sources (ringing) and the overall performance of the EMI filter.


From Schematic...

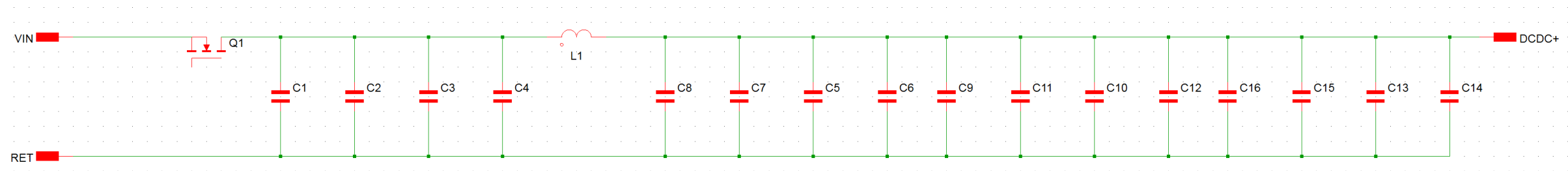

To PCB Layout...

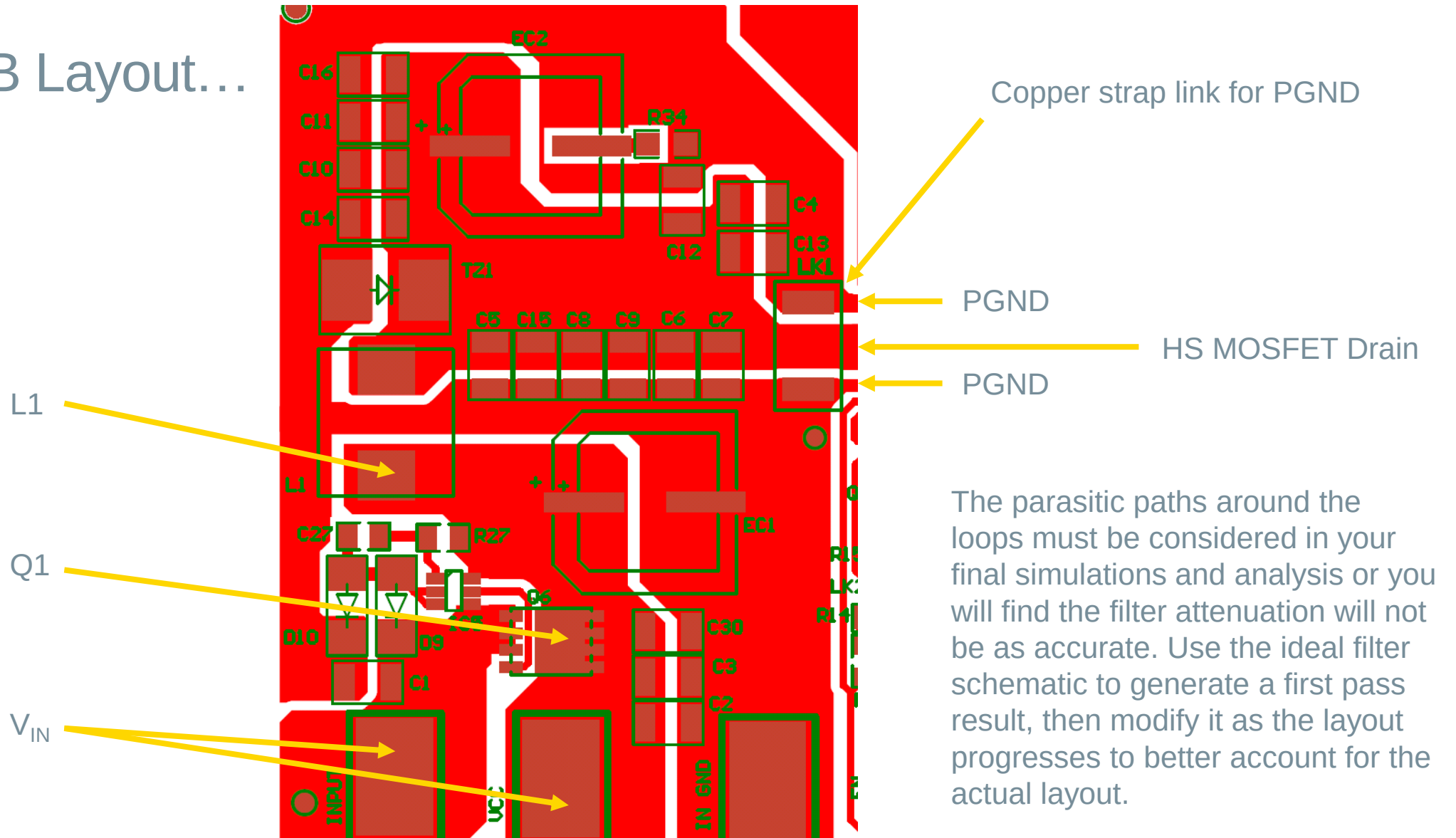

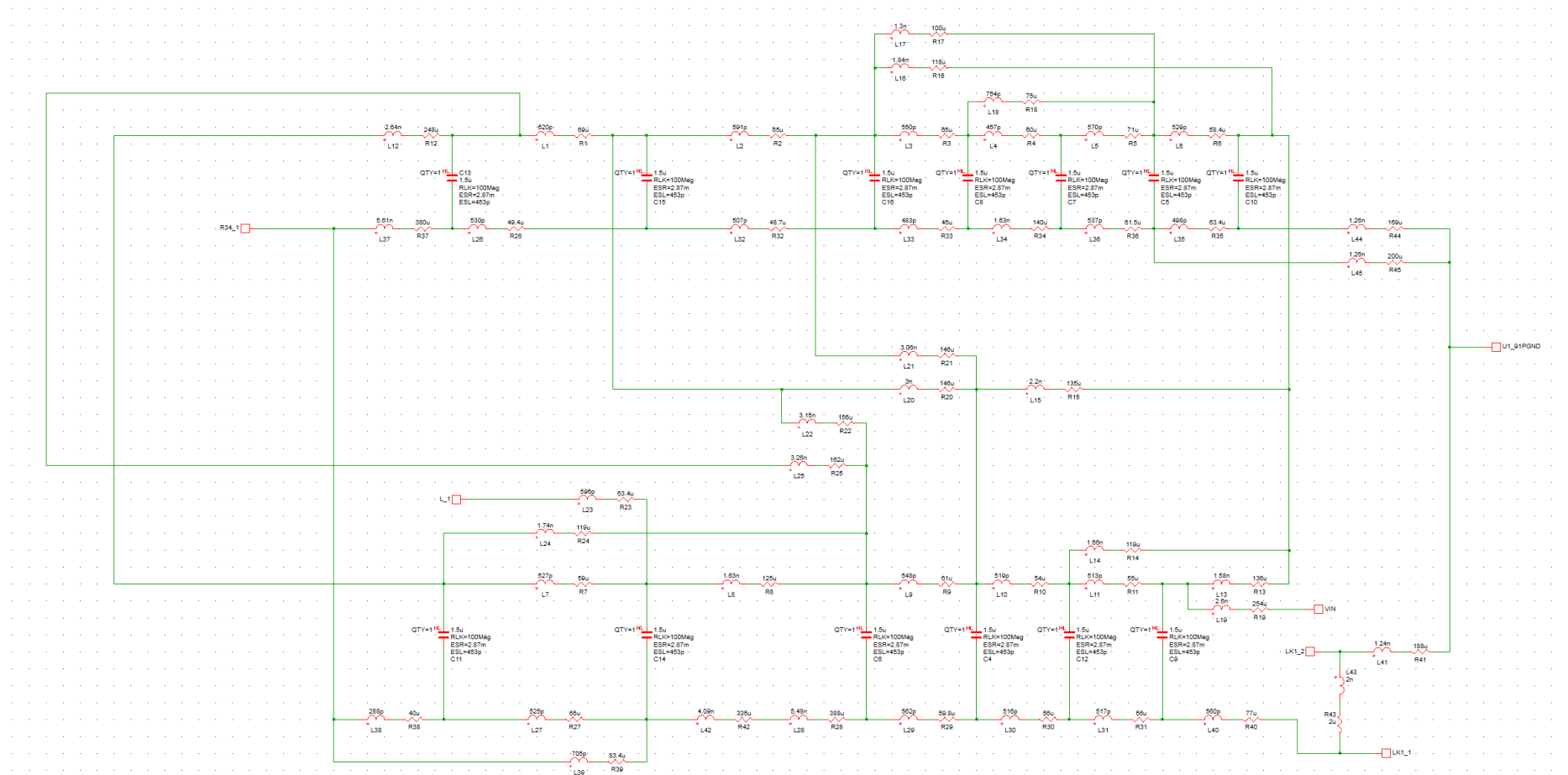Extracted layout from L1 to HS MOSFET-drain and PGND



Tools – Beehive 100


- Includes wideband RF amplifier and cables
- Three H-field probes and one E-field probe
- 100D is the E-field probe to the far right
- Buy as a kit, a must have!



Use the amplifier for the small field probes as they are less sensitive. The bigger probes allow you to find the approximate area of the offending signal while the smaller ones let you trace it more closely.

Tools – power splitters

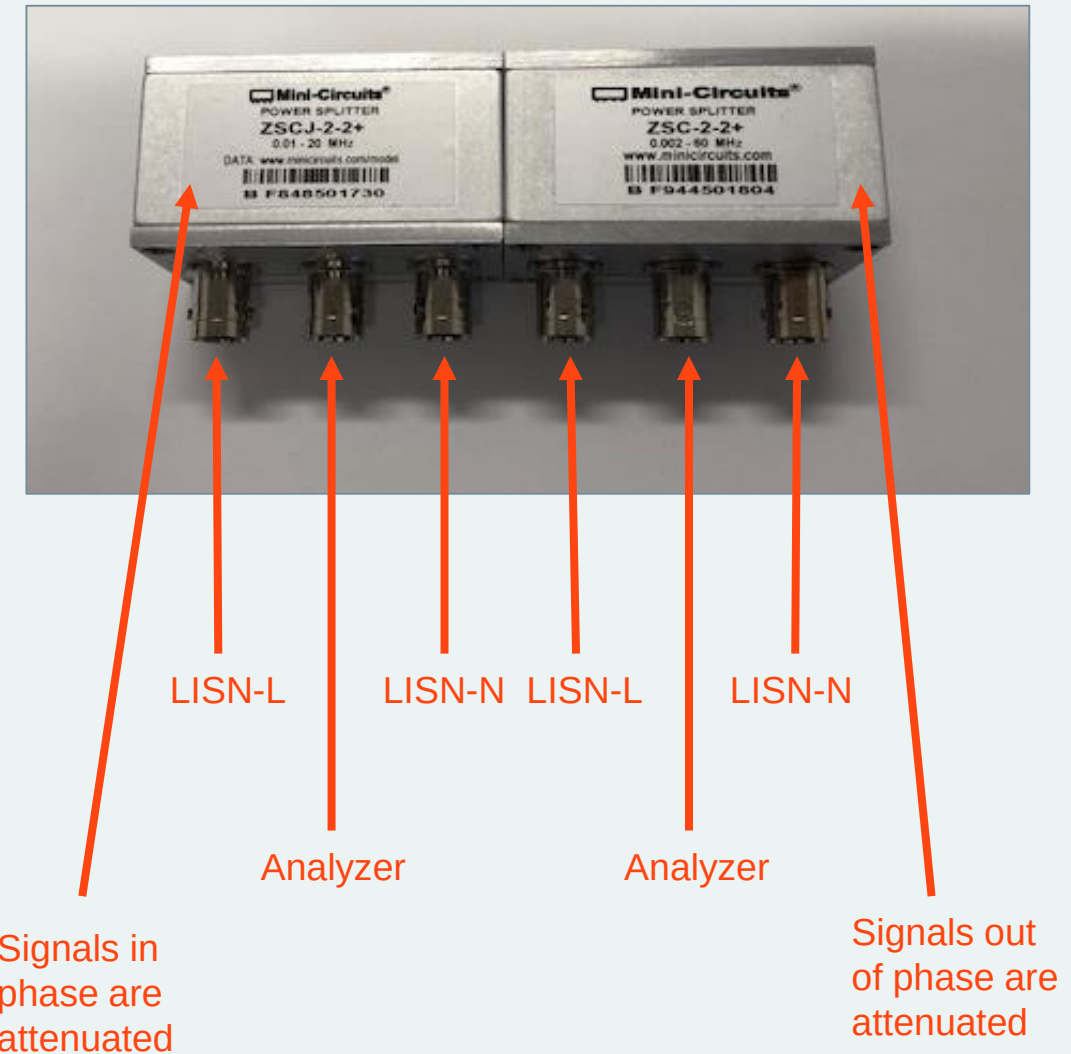- ZSCJ-2-2+ Mini-Circuits
- Blocks Common-Mode
- ZSC-2-2+ Mini-Circuits
- Blocks Differential-Mode
- Both require dual or two single LISN(S)
- Must use matched equal-length coax cables. Length should be as short as possible



Tools – Swartzomatic-1

- Hand-wound HF current probe
- Measures CM and DM current
- High-permeability core
- 50 Ohm cable
- Wide BW, high sensitivity
- Much better for high-frequency current with very low amplitudes than traditional current probe.



Pass wires through core in same direction to measure common-mode current, opposite directions for differential current.

Tools – Swartzomatic-2

- Hand-wound near-field probe
- Helps find high H-fields on PCB
- Hand-made using RG-58U
- 50 Ohm cable
- Common-mode beads can be added to cable as an option



Connect to 50 Ohm termination on scope. Start with higher volts/div while moving around PCB. Then reduce volts/div to allow location of near-field to be determined. Then use lower sensitivity probes (Beehive) to trace offending H-field caused by noise currents of interest. Makes an excellent trigger without connecting to circuit.

Troubleshooting – design challenges


- 250W+ Critical Conduction Buck Regulator
 - Efficiency had to be 96% or higher, high switching frequency 700kHz
 - PCB area was small, isolated metal box enclosure, potted.
 - High ambient environment up to 65°C
- Thermal Management
 - Power SiP and PCB needed thermal connection to plate for cooling
 - This caused less-than-optimal ground plane, increasing parasitic inductance
- CISP25 Conducted EMI
 - Required two-stage filter as second harmonic needed –40dB attenuation

Tools – at my disposal

- An excellent simulation model of powertrain and filter design
 - Performed AC and transient analysis of power system with filter, no issues
 - Performed parasitic extraction of layout after it was done.
- Test Equipment
 - All tools shown previously plus Spectrum Analyzer and Oscilloscope.
 - LISNs, differential amplifiers and a good network analyzer.

Troubleshooting EMI – the filter used

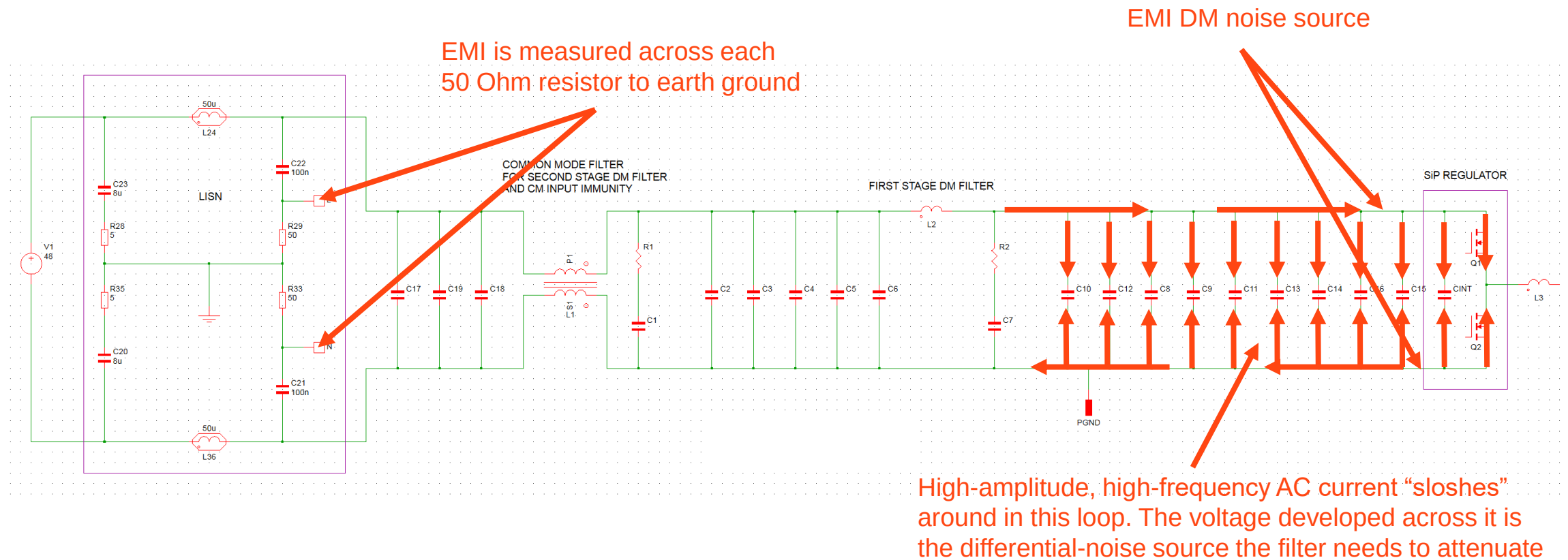
The EMI filter is shown below (idealized) for purposes of illustration




Troubleshooting EMI – the initial measurements

The initial measurement spurred my work on a new book entitled “What You Thought You Knew About EMI” !! 😊

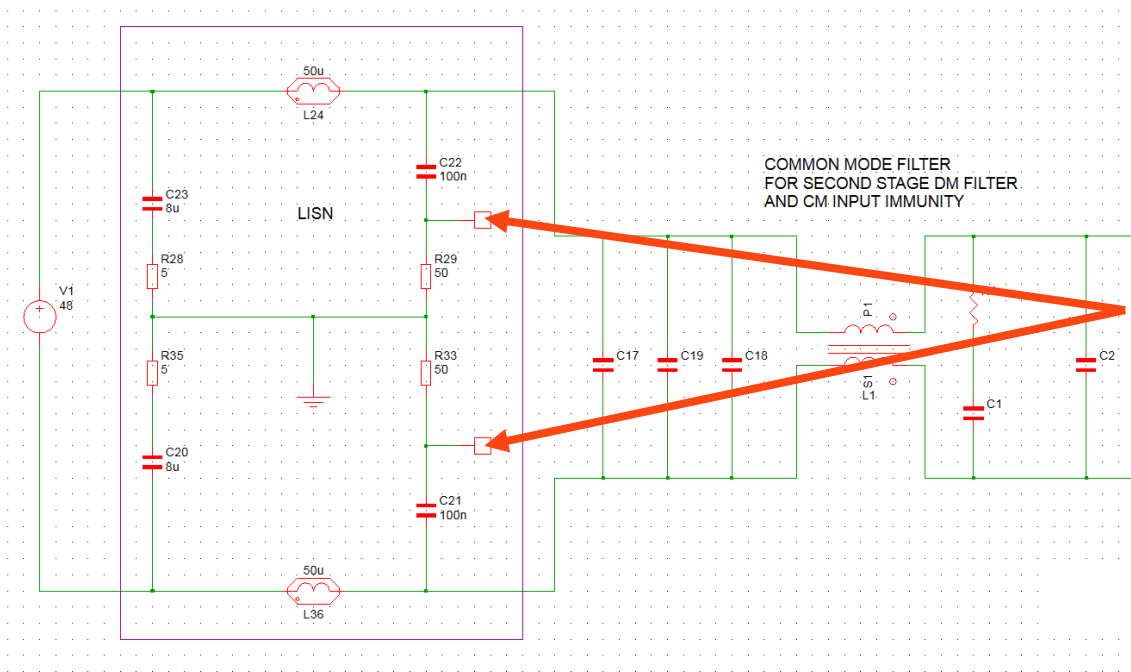High-frequency EMI was totally unexpected. The only thing that matched expectations was the fundamental.




Peaks	Frequency	Amplitude
1	8.1583 MHz	63.4221 dBμV
2	8.6682 MHz	62.7268 dBμV
3	7.6484 MHz	62.0954 dBμV
4	7.1385 MHz	59.0767 dBμV
5	9.1781 MHz	58.8904 dBμV
6	6.6287 MHz	57.3537 dBμV
7	6.1187 MHz	56.1336 dBμV
8	5.6088 MHz	53.7328 dBμV
9	3.5693 MHz	53.6681 dBμV
10	3.0594 MHz	53.4649 dBμV
11	4.0792 MHz	53.2542 dBμV
12	5.0990 MHz	52.9415 dBμV
13	10.1979 MHz	52.7300 dBμV
14	9.6880 MHz	52.7015 dBμV
15	4.5891 MHz	52.5385 dBμV
16	1.5297 MHz	52.2561 dBμV
17	2.0395 MHz	51.9603 dBμV
18	2.5495 MHz	51.8715 dBμV
19	509.9 kHz	50.4446 dBμV
20	1.0198 MHz	49.3241 dBμV

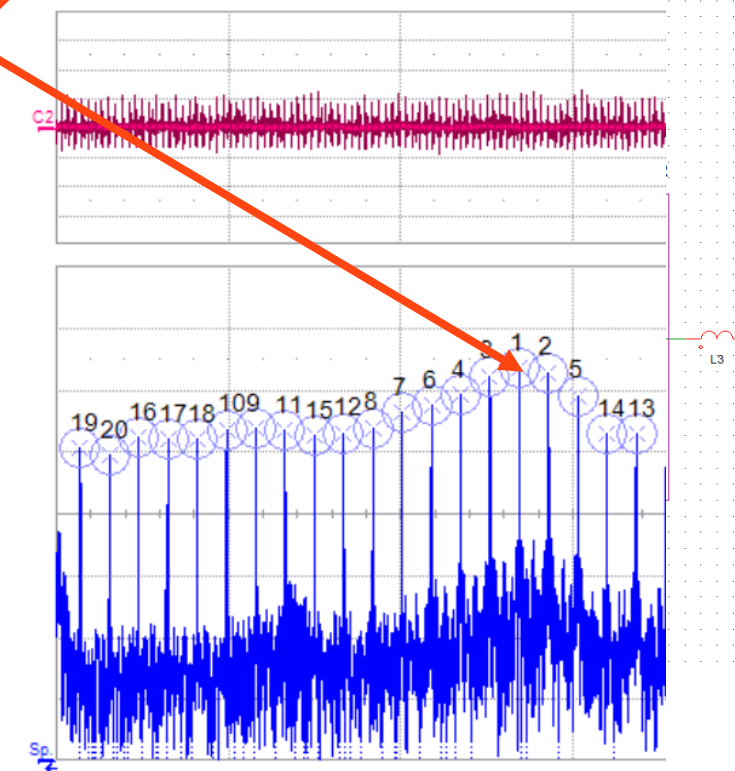


Troubleshooting EMI – the initial measurements

DM signal measured at SiP input on customer board:
high frequency (6 – 10MHz) is higher by
8 – 12dB, a noticeable ringing observed


Peaks	Frequency	Amplitude
1	512.7 kHz	106.282 dBμV
2	1.0254 MHz	100.282 dBμV
3	1.5380 MHz	92.7580 dBμV
4	2.0507 MHz	84.1562 dBμV
5	2.5634 MHz	82.3457 dBμV
6	3.0761 MHz	80.7273 dBμV
7	4.1015 MHz	80.0420 dBμV
8	3.5888 MHz	80.0107 dBμV
9	4.6142 MHz	73.7851 dBμV
10	8.7157 MHz	72.5730 dBμV
11	9.2283 MHz	72.2168 dBμV
12	9.7409 MHz	70.3115 dBμV
13	8.2030 MHz	69.9668 dBμV
14	10.2535 MHz	68.4108 dBμV
15	7.6903 MHz	67.8472 dBμV
16	267.0 kHz	65.9995 dBμV
17	6.6649 MHz	65.3908 dBμV
18	7.1776 MHz	64.7504 dBμV
19	246.0 kHz	64.6311 dBμV
20	6.1522 MHz	64.5793 dBμV

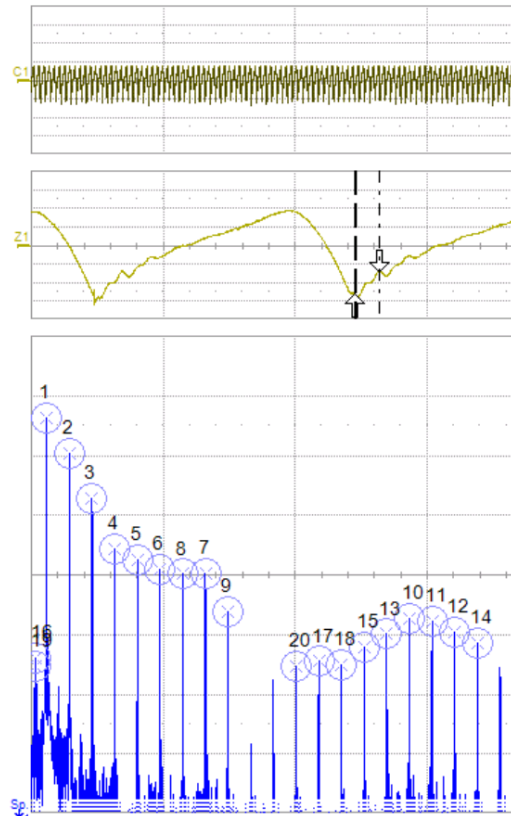


Peaks	Frequency	Amplitude
1	525.5 kHz	107.144 dBμV
2	1.0509 MHz	99.1488 dBμV
3	1.5764 MHz	92.6918 dBμV
4	2.1018 MHz	86.2262 dBμV
5	2.6273 MHz	83.1736 dBμV
6	3.1527 MHz	80.7635 dBμV
7	3.6782 MHz	80.4213 dBμV
8	4.2036 MHz	78.1610 dBμV
9	237.4 kHz	66.4721 dBμV
10	9.9837 MHz	65.1480 dBμV
11	288.0 kHz	64.3286 dBμV
12	4.7291 MHz	64.0228 dBμV
13	10.5092 MHz	63.8556 dBμV
14	9.4581 MHz	62.8661 dBμV
15	186.9 kHz	61.4649 dBμV
16	8.9328 MHz	61.1135 dBμV
17	813.9 kHz	59.5388 dBμV
18	762.9 kHz	59.4055 dBμV
19	8.4073 MHz	59.2458 dBμV

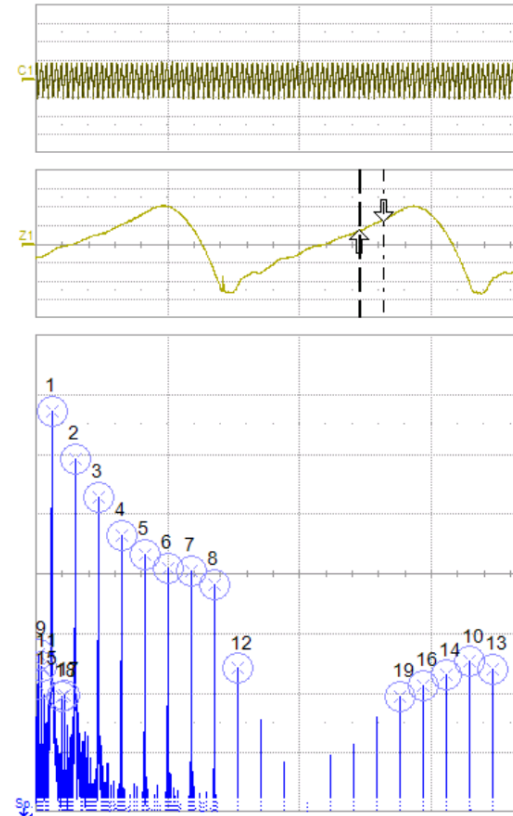

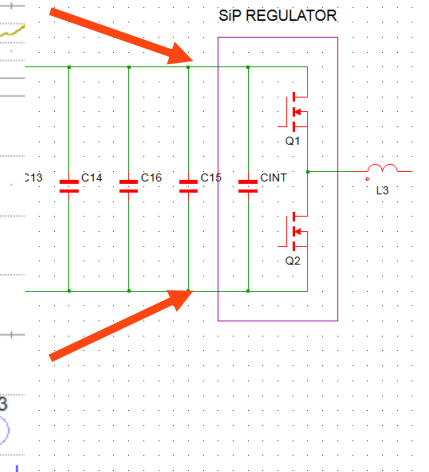
DM Signal measured on evaluation
board with better ground plane



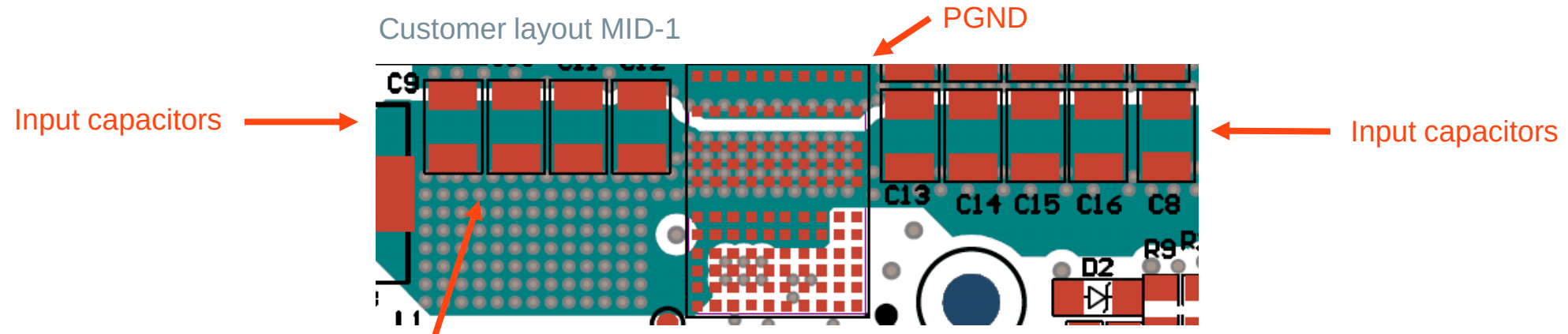Troubleshooting EMI – the ground plane differences



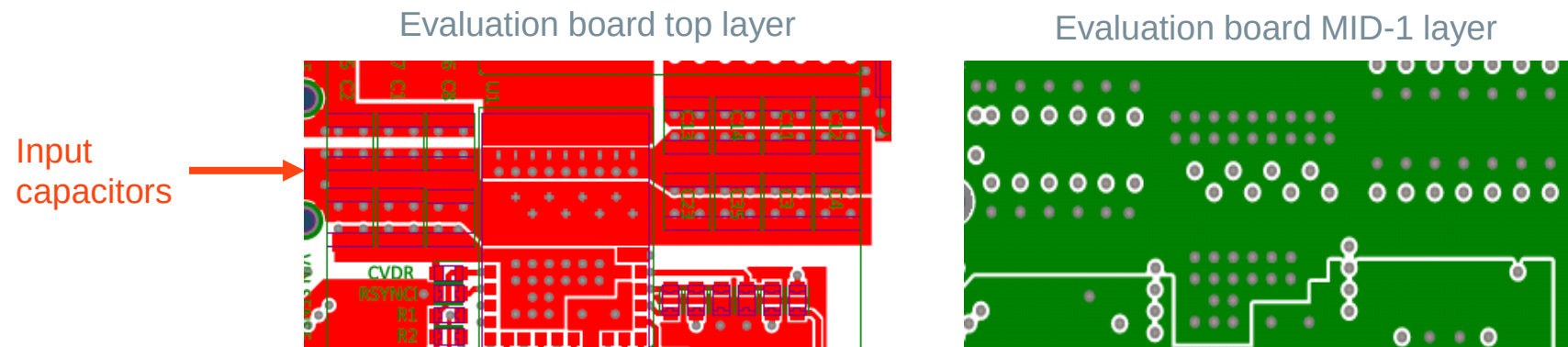V_{IN} is major heat source. Needed to be carried through all 4 layers in customer design to form robust pad to thermally bond to plate. Notice the large amount of via's needed to carry the heat load through the board to the plate. Ground plane is broken up.



Notice ground plane is only broken by a small number of vias with flooded copper around them. Much lower parasitic inductance but thermal impedance is too high to meet thermal requirements.


Troubleshooting EMI – what I know and don't know – what next?

- The measured EMI at input to SiP shows significant high-frequency ringing in the area where EMI is failing.
- I believe this ringing to be caused by layout – result of higher parasitic inductance and higher Q noise loop
- How does this frequency get through the EMI filter? Is Filter deficient somehow?
- Is the noise bypassing the filter?
- Near-field contamination by high flux in inductor?
- Capacitive coupling due to high-voltage transitions?
- Radiated EMI into LISN?
- Common-mode noise or differential-mode noise?

Troubleshooting EMI – next steps

Determine if noise is CM or DM...

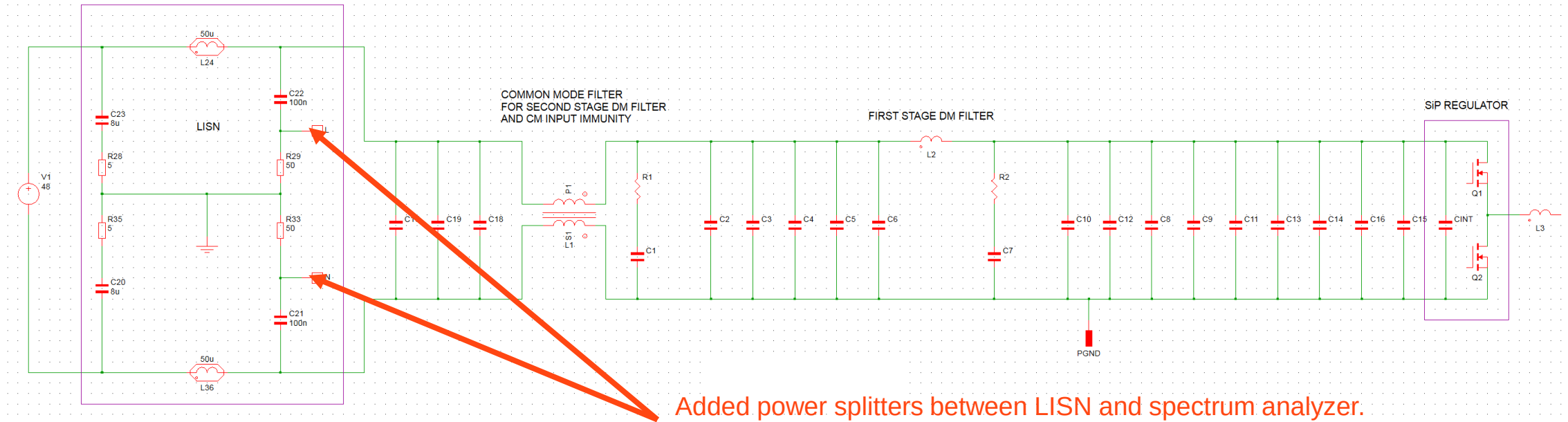EMI is measured across each 50 Ohm resistor to earth ground



Added power splitters between LISN and spectrum analyzer. Blocking CM noise showed no change to high-frequency measurement. Blocking DM noise knock all high-frequency emission down by 30dB.


Conclusion: Offending signal is differential

Troubleshooting EMI – next steps

Determine which parts of EMI filter are working properly...

Use diff-amp to measure this voltage. Take FFT and measure attenuation of first stage filter.

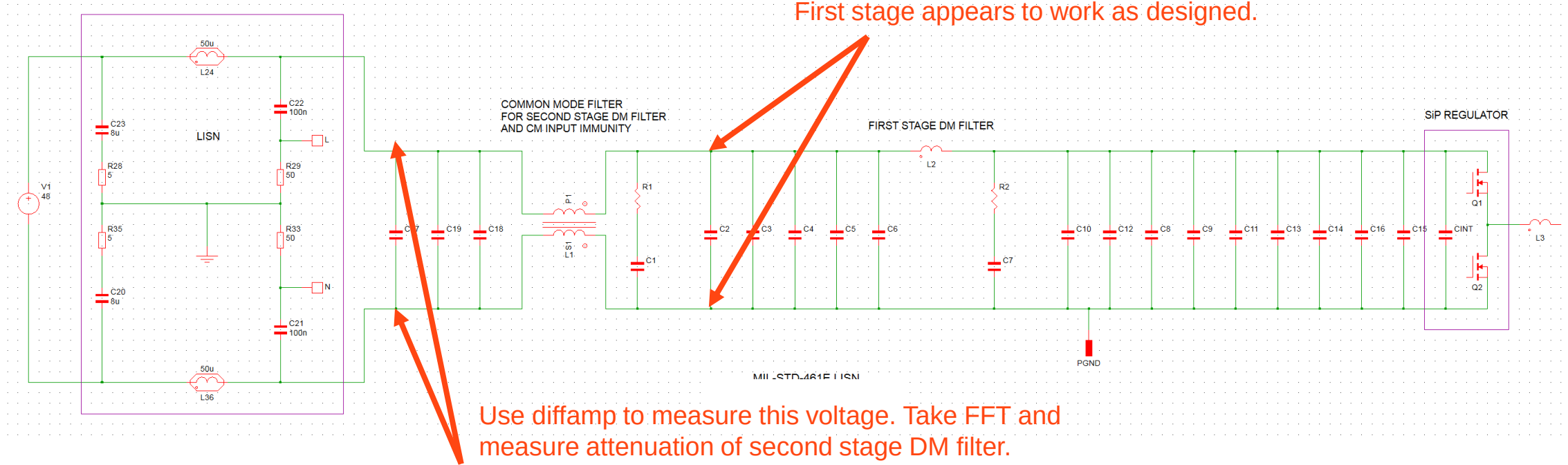- Does it match simulated expected results? Yes!
First stage appears to work as designed.



Use diffamp to measure this voltage. Take FFT and measure attenuation of second stage DM filter.

- Does it match simulated expected results? No!
8MHz and other high-frequency noise here.
No correlation to simulation whatsoever.


Troubleshooting EMI – next steps

Check simulation model of second-stage filter.
Was anything missed like self resonance of inductor core?

Open circuit and use network analyzer to sweep both filters.


- Does attenuation appear as shown in simulation to be close? Yes!

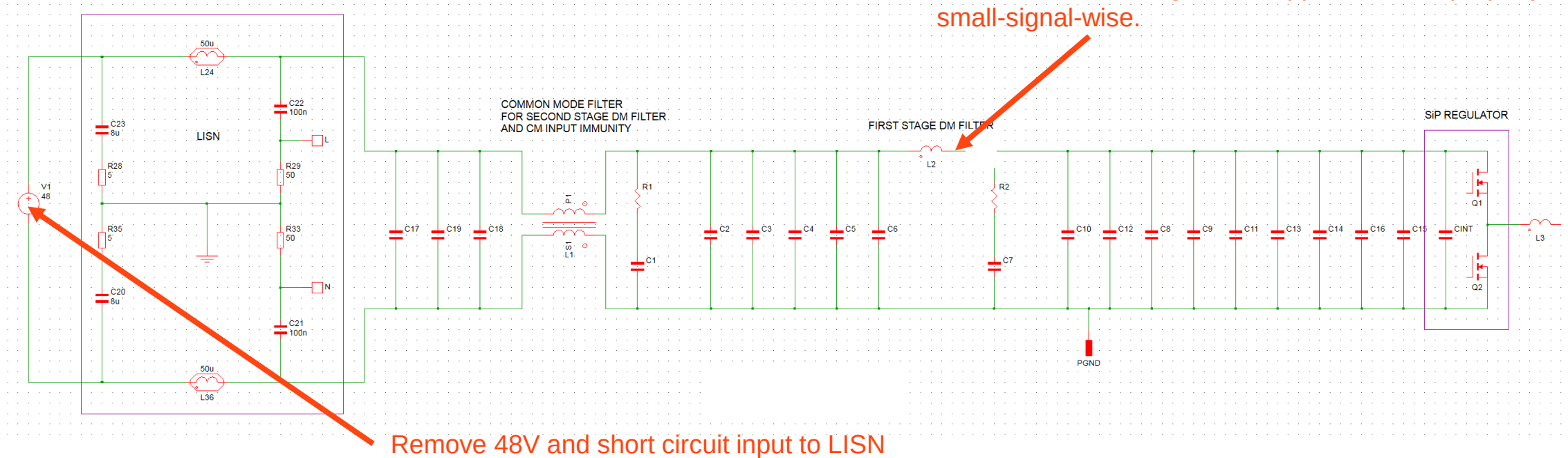First and second stage filters appear to work properly small-signal-wise.



Troubleshooting EMI – next steps

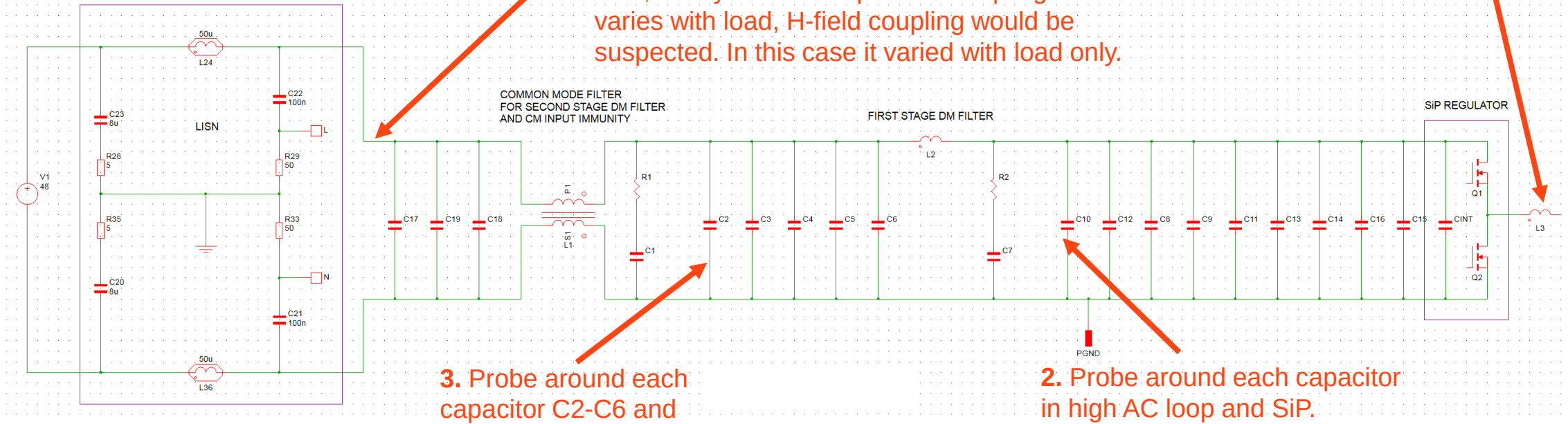Use field probes to isolate where contamination is coming from



4. Probe C17-C19. 8MHz and other frequencies detected! Next, vary the line voltage.

- Does the EMI amplitude go up with line going up?

If so, it may indicate capacitive coupling. If EMI varies with load, H-field coupling would be suspected. In this case it varied with load only.

1. Highest H-field is inductor. Good starting point.

- Any evidence of 8MHz ringing here? No!

No evidence here or output capacitors.

3. Probe around each capacitor C2-C6 and around L2.


- Any evidence of 8MHz? No evidence. Very quiet here.

2. Probe around each capacitor in high AC loop and SiP.

- Any evidence of 8MHz? Yes, around each capacitor and slightly higher around SiP


Troubleshooting EMI – fix layout

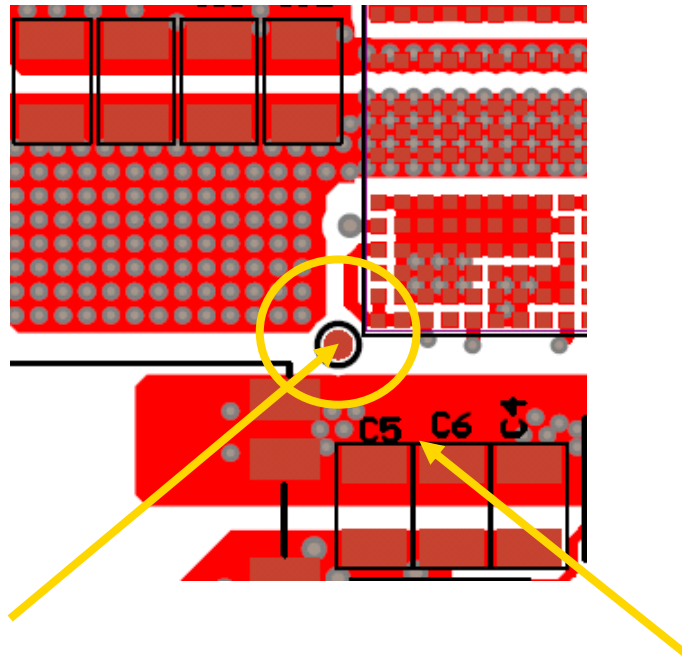Problem area isolated and fix implemented



Area of suspected coupling

8MHz detected here with near field probe

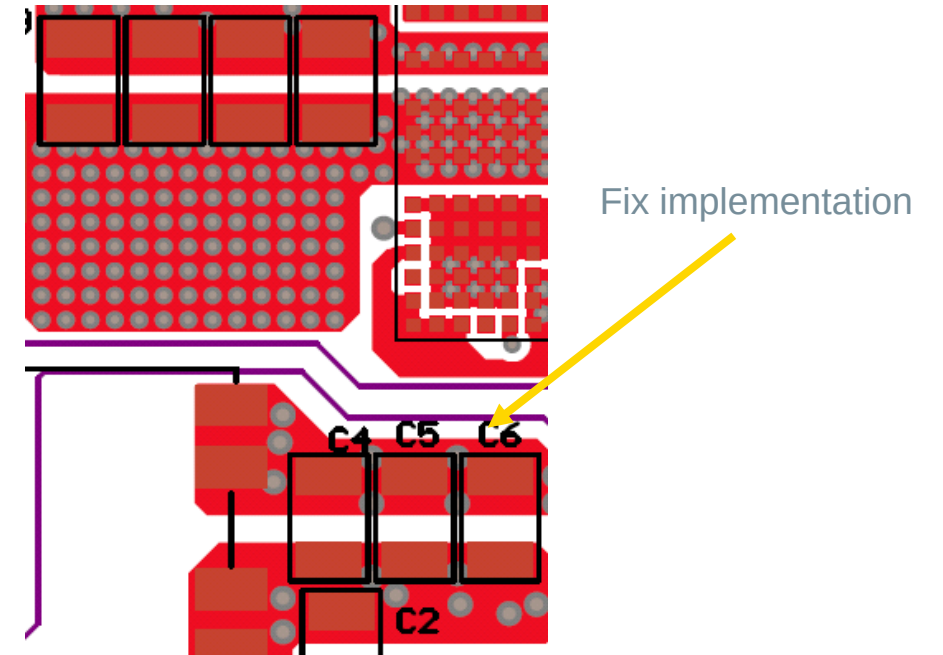

Fix implementation

Acknowledgements

- The following material was used as references in the presentation :
 - *Controlling Conducted Emissions By Design* by John C. Fluke
(an excellent book, highly recommended)
 - *Predict Differential Conducted EMI with a SPICE Simulator*
Christophe Basso; April 12, 1996
 - *Making EMI Compliance Measurements*
Agilent Technologies Application Note
 - *CISPR 22* Fourth Edition



Thank you

Questions?

The information contained herein and presented by Vicor is for general informational purposes only. Vicor assumes no responsibility for inaccuracies, errors or omissions in this presentation. Users of power supply products remain responsible for the design, testing and operational safeguards related to such use.