



Linear Technology Corporation


Power Business Unit

EMI solution & Layout


JM Park

Field Applications Engineer

2x2A 1.1Mhz in a AM Radio

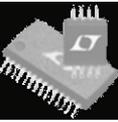


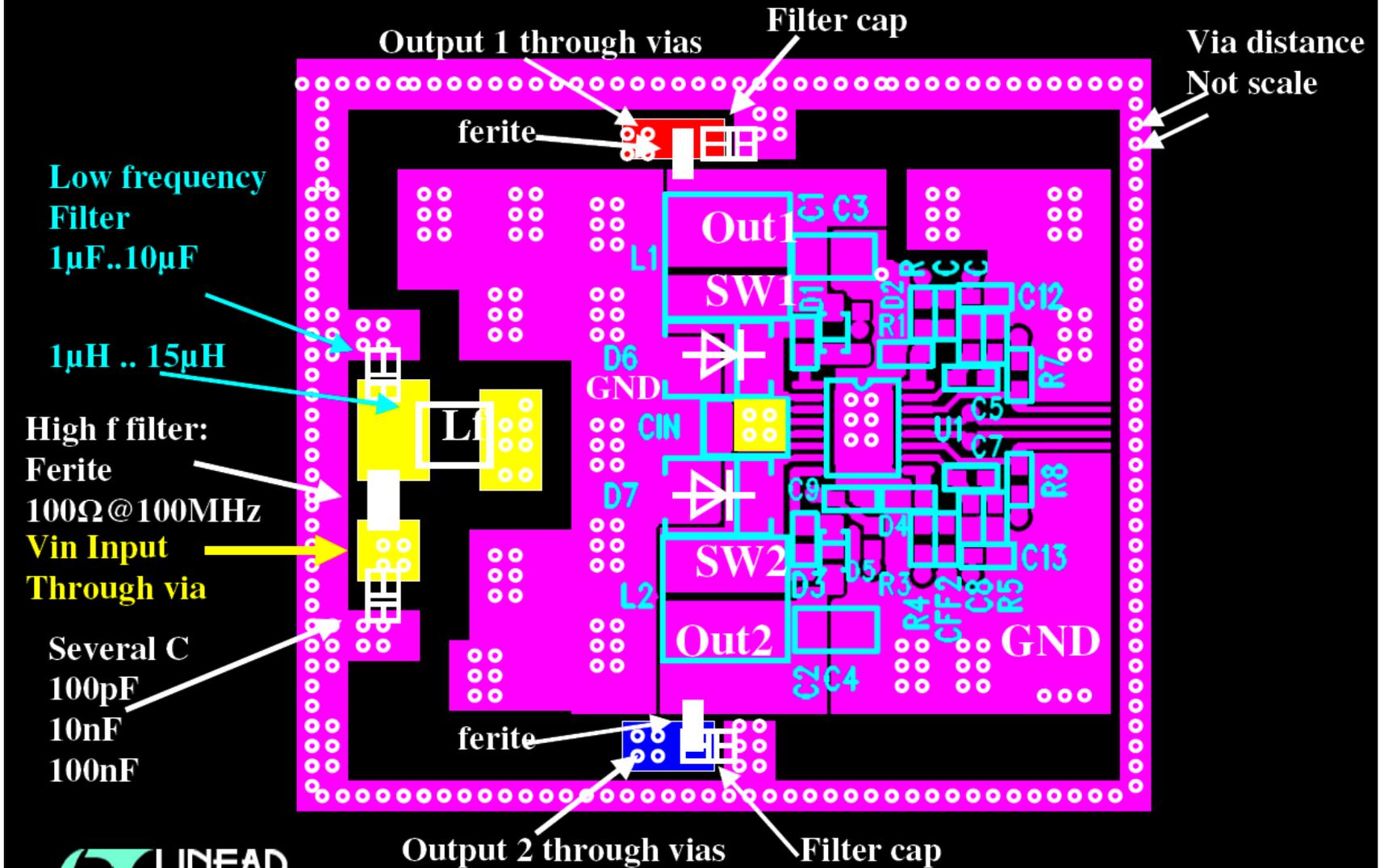Layout example for LT1940EFE with EMC filters



LINEAR

LINEAR
TECHNOLOGY

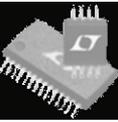


1. Why EMI Noise come from DC/DC converter?


- 1) EMI Noise
- 2) EMI Noise Source on switching regulator
- 3) Noise Hot loop as topology

2. How to reduce EMI Noise?


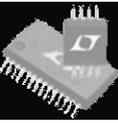
- 1) Layout design & Filter
- 2) LTC EMI solution



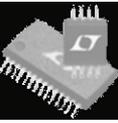
Why EMI Noise comes from DC/DC converter?



EMI Noise

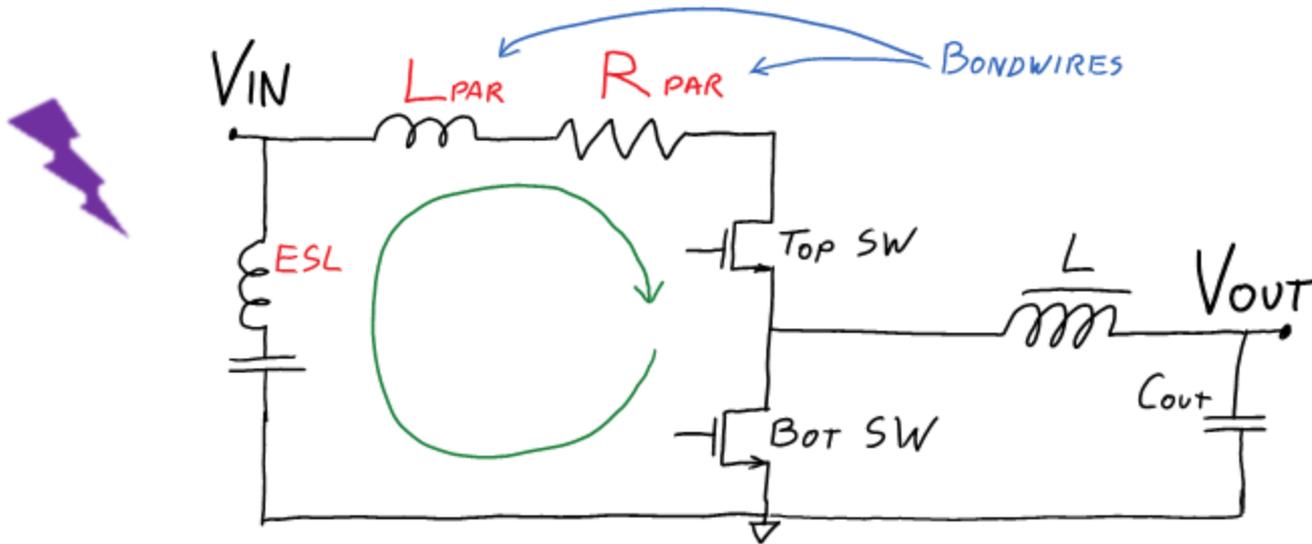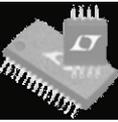


$$V_{\text{noise}} = L * di/dt$$

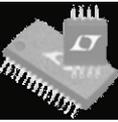

dBm and dBuV


Relationship between dBm, W, dB μ V, V			
dBm	W	dB μ V	V
-100	0.1pW	7	2.2 μ V
-90	1pW	17	7 μ V
-80	10pW	27	22 μ V
-70	100pW	37	70 μ V
-60	1nW	47	220 μ V
-50	10nW	57	700 μ V
-47	20nW	60	1mV
-40	100nW	67	2.2mV
-30	1 μ W	77	7mV
-20	10 μ W	87	22mV
-10	100 μ W	97	70mV
0	1mW	107	220mV
10	10mW	117	700mV
20	100mW	127	2.2V
30	1W	137	7V

dbmW	dbuV
33	140
23	130
13	120
3	110
-7	100
-17	90
-27	80
-37	70
-47	60
-57	50
-67	40
-77	30
-87	20
-97	10
-107	1

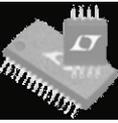


EMI Noise Source on Switching regulator


Buck is like a L/C filter

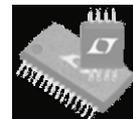

$V_{in} = 10V$



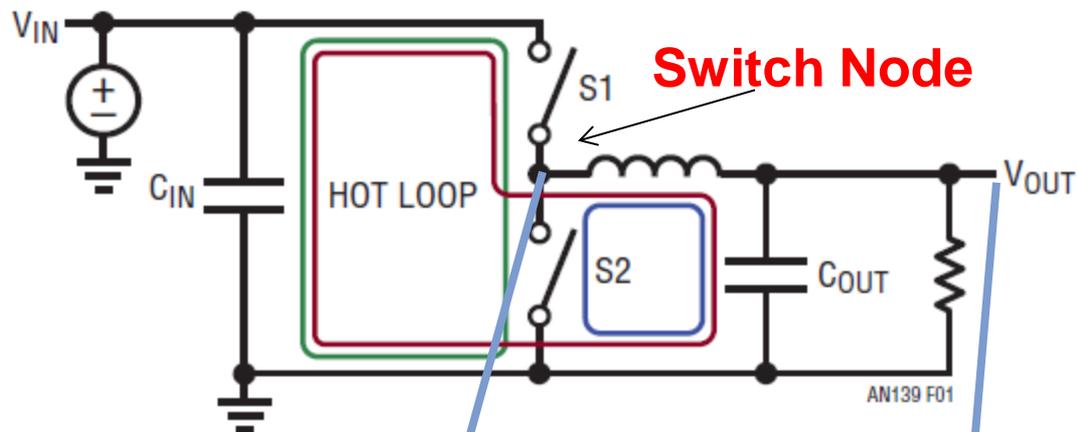


$V_{out} = 5V$

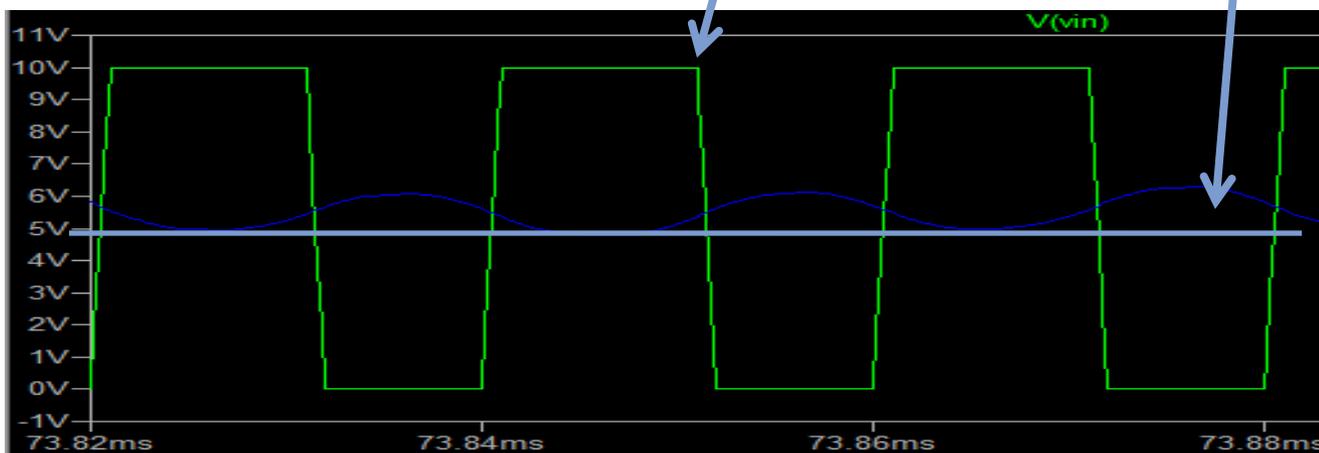


$$\text{Duty} = V_{out} / V_{in} = 50\%$$



Buck is like a L/C filter

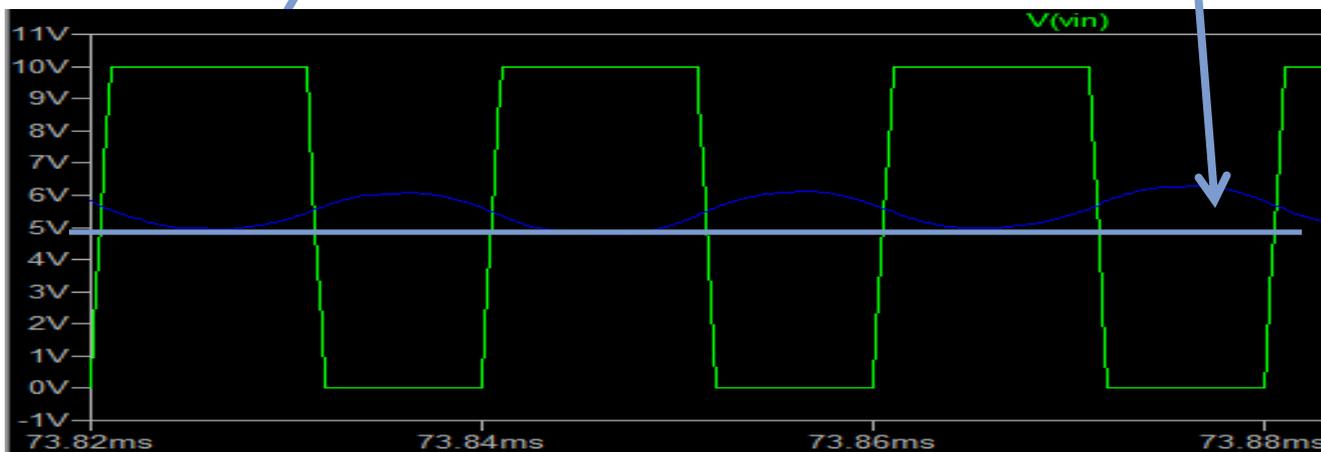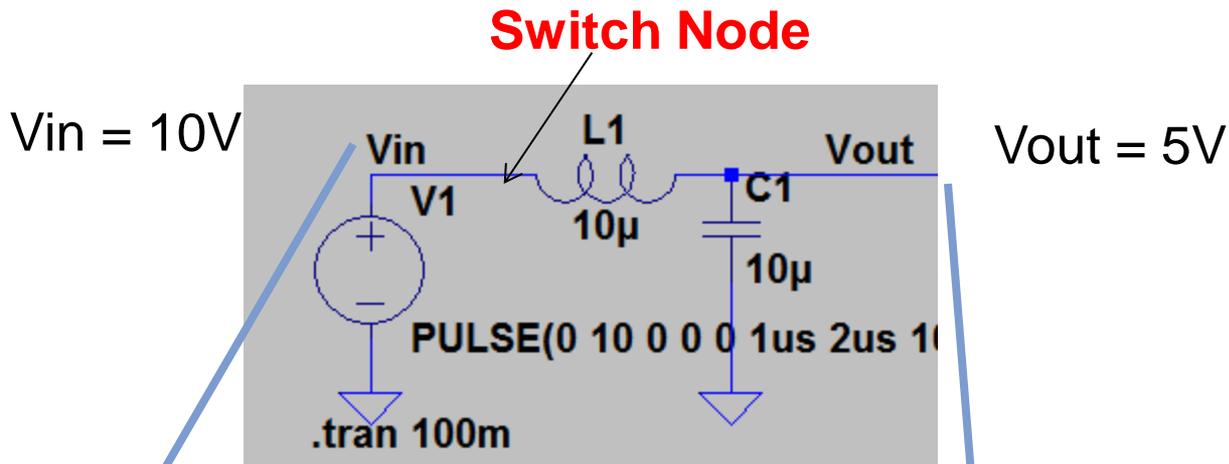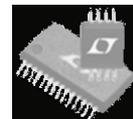

Freq : 50kHz
Ripple : 1Vp-p
Duty : 50%

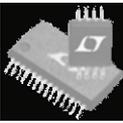


Buck is like a L/C filter

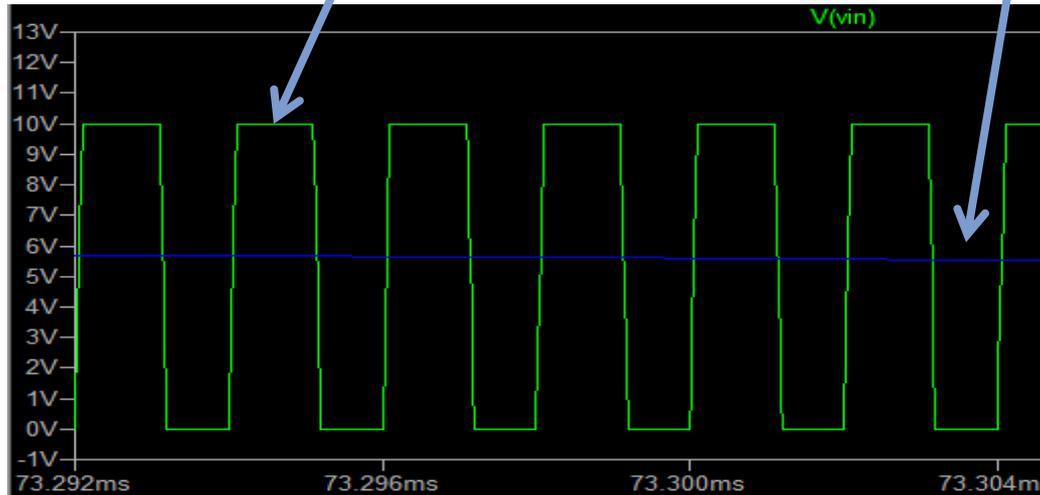
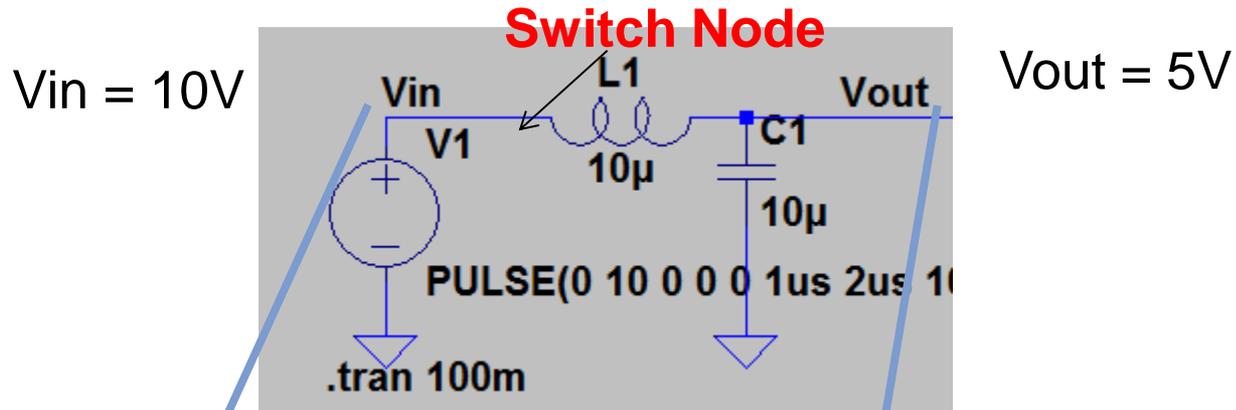


Freq : **500kHz**
Ripple : **50mVp-p**
Duty : **50%**

주파수 증가 시 ripple voltage 감소

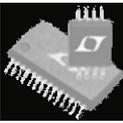


Buck is like a L/C filter

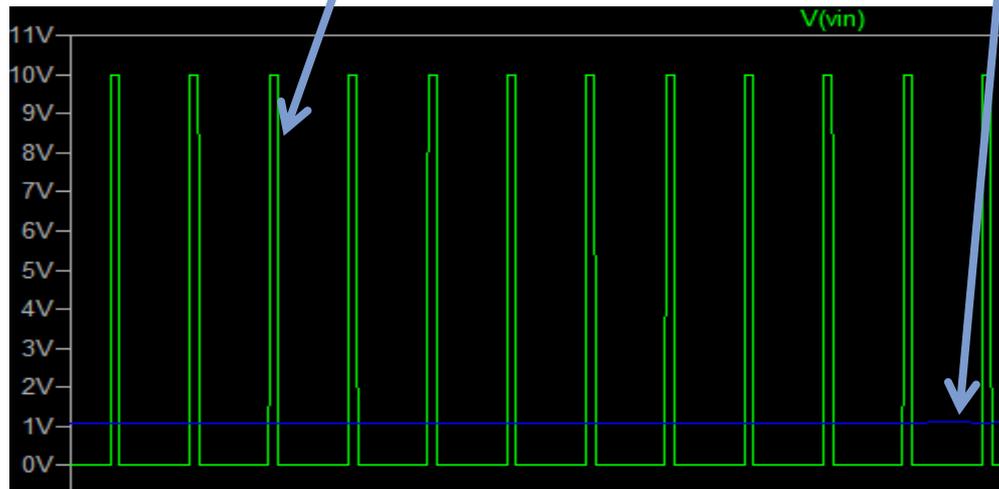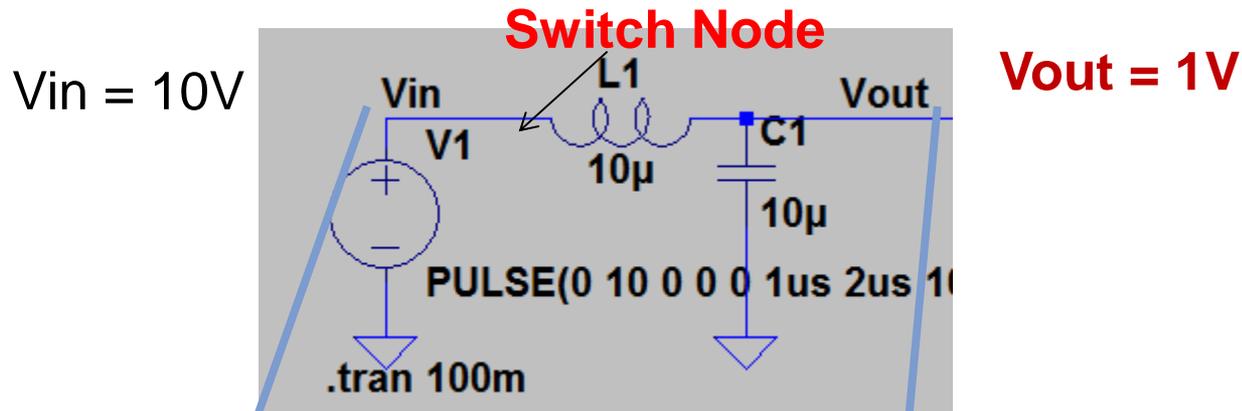



Freq : **500kHz**
Ripple : **50mVp-p**
Duty : **10%**

Duty 감소시 V_{out} 전압 낮아짐

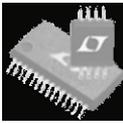



Inductor Behavior

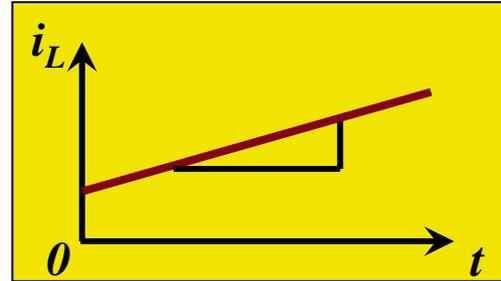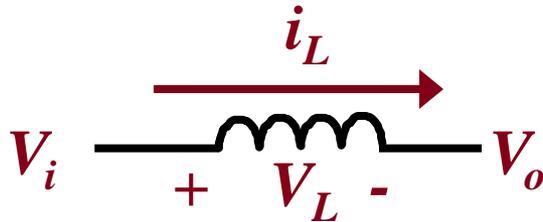- ◆ As a positive voltage is applied ($V_i > V_o$), **current** through an inductor increases



$$\frac{di_L}{dt} = \frac{+V_L}{L}$$

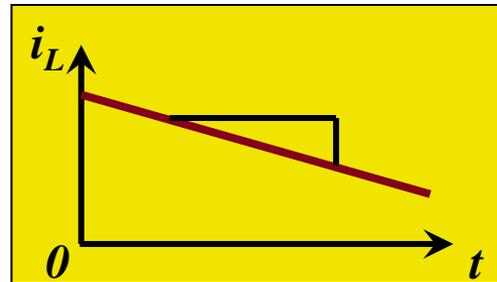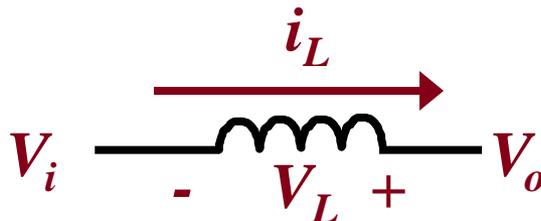
- ◆ If we reverse the polarity of the voltage ($V_i < V_o$), the current through the inductor decreases



$$\frac{di_L}{dt} = \frac{-V_L}{L}$$


Inductors do not like instantaneous changes in current

Switching an Inductor

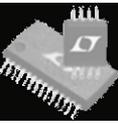



◆ Switch ON

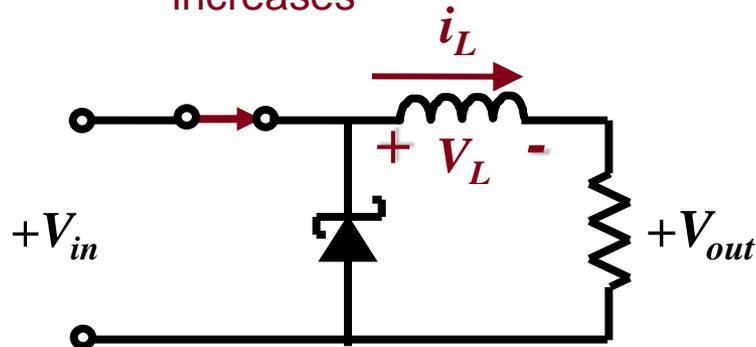- ◆ Current through the inductor increases





◆ Switch OFF

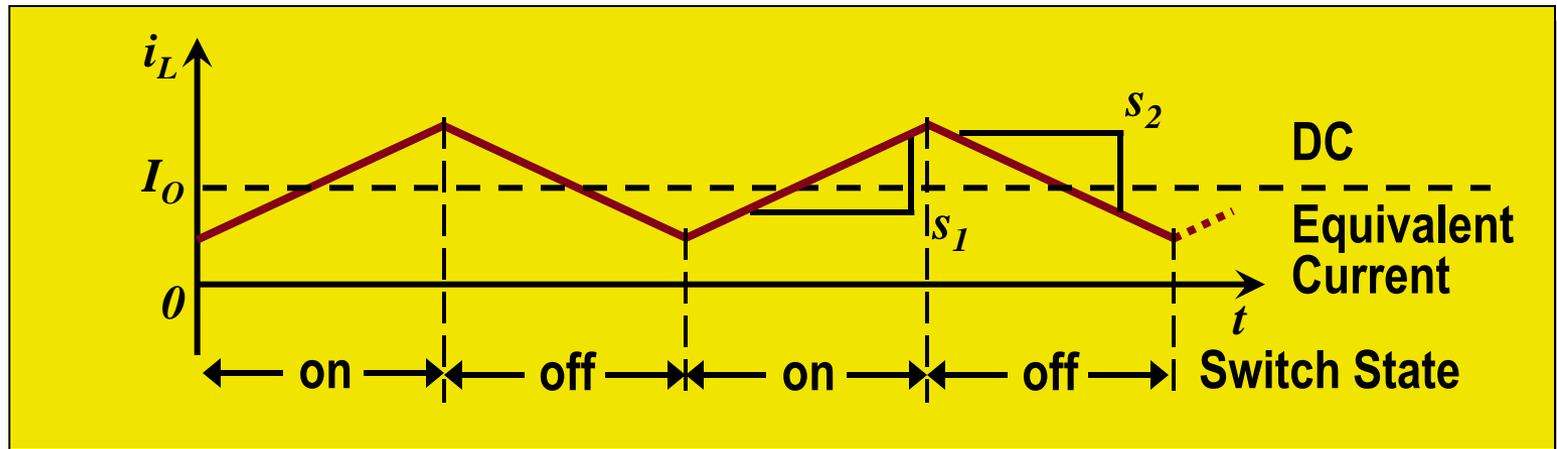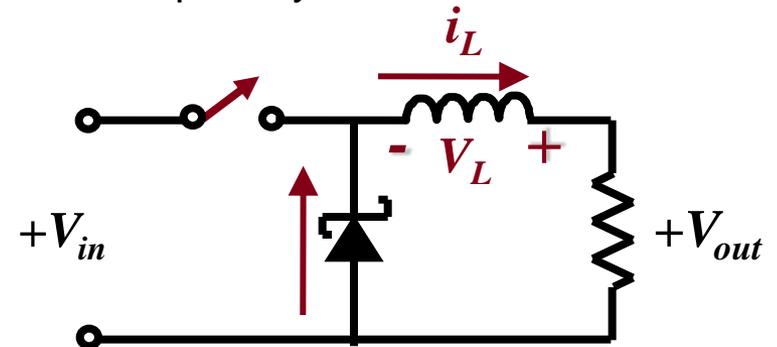- ◆ Current through the inductor decreases, reverses polarity




Switch current vs inductor current

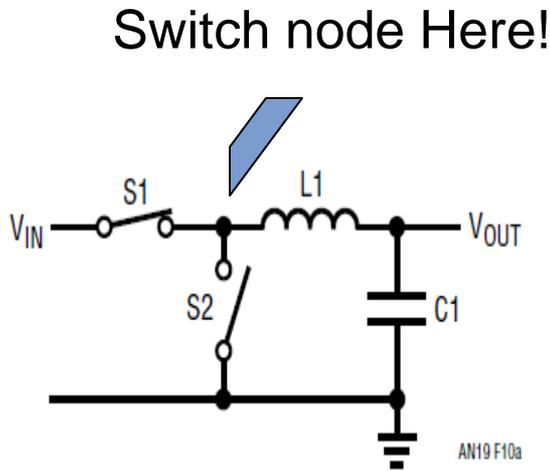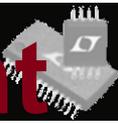



Buck Topology

DISCONTINUOUS MODE

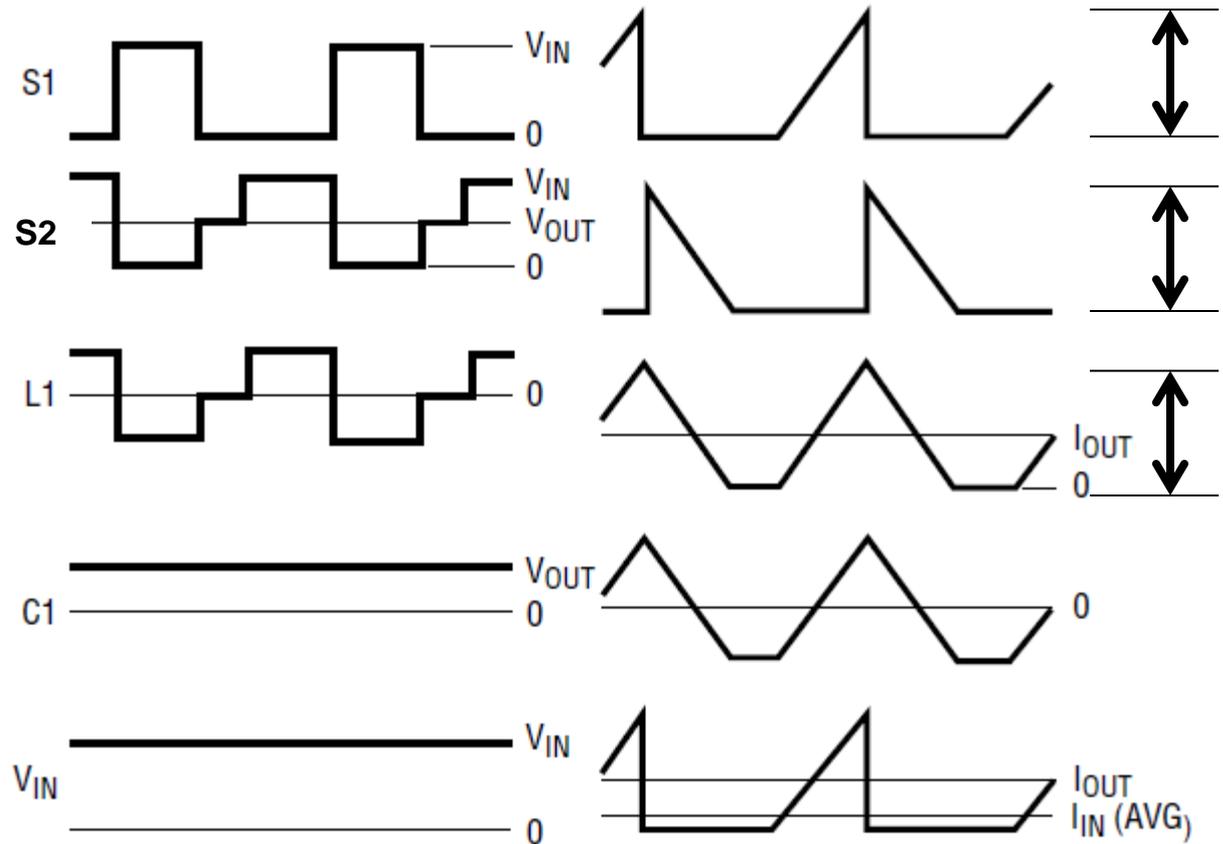


S1 전류변화 = S2 = L1 inductor 전류변화 !!

Switch current vs inductor current

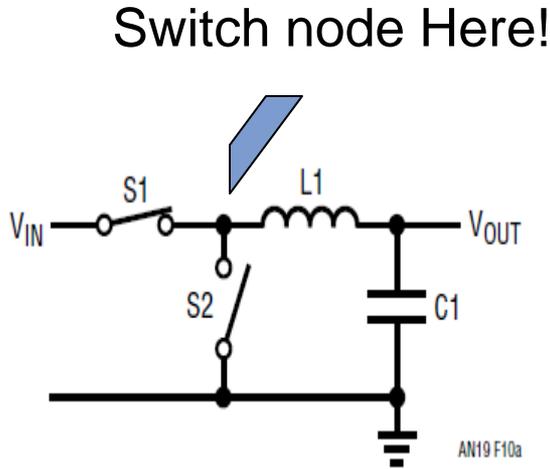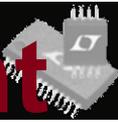


Buck Topology

CONTINUOUS MODE

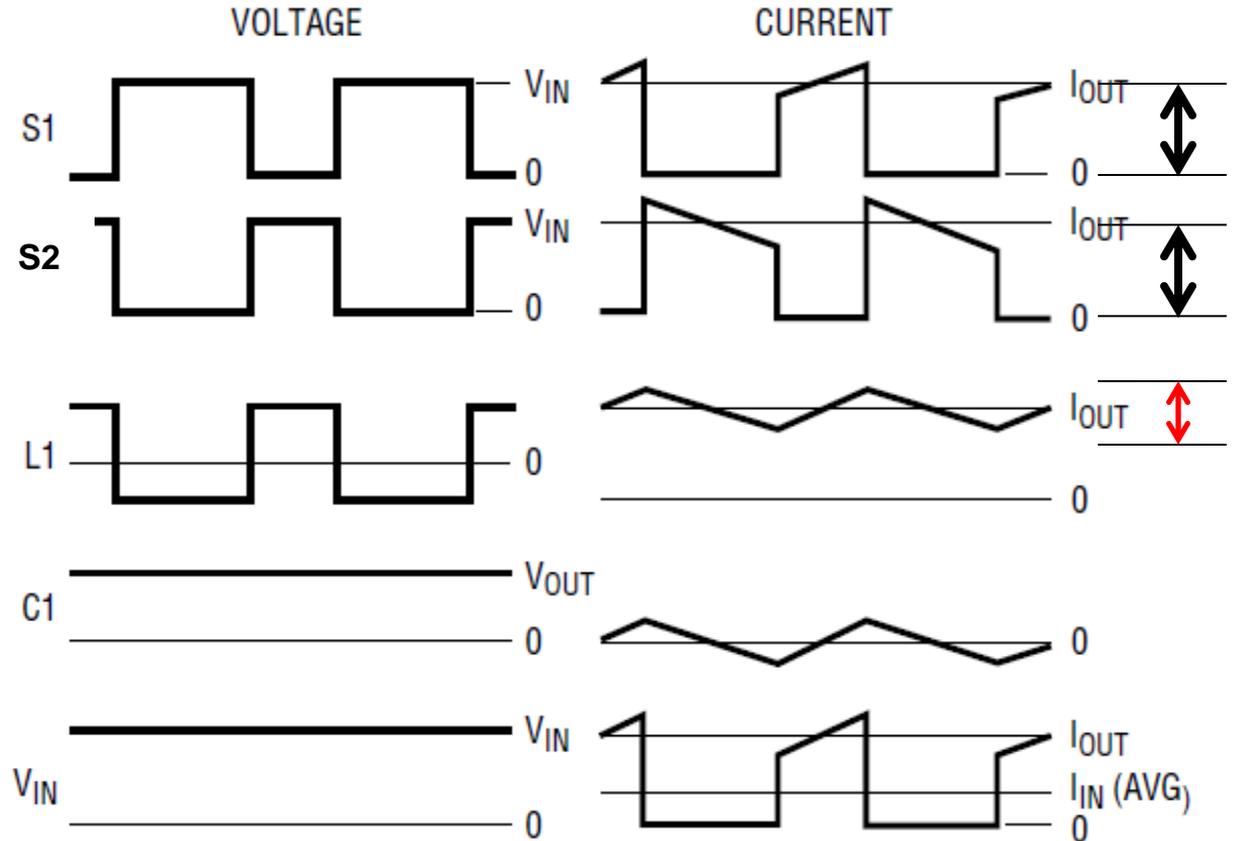


S1 전류변화 = S2 >> L1 inductor 전류변화 !!

Switch current vs inductor current

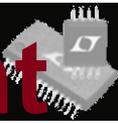


S1

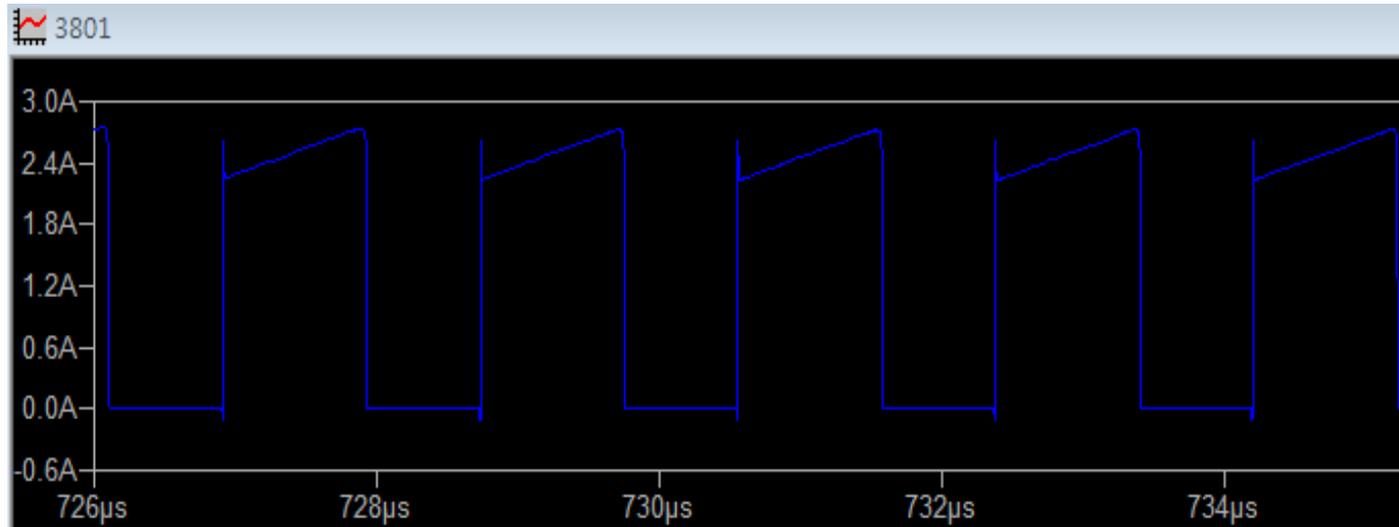

2.75A



S2

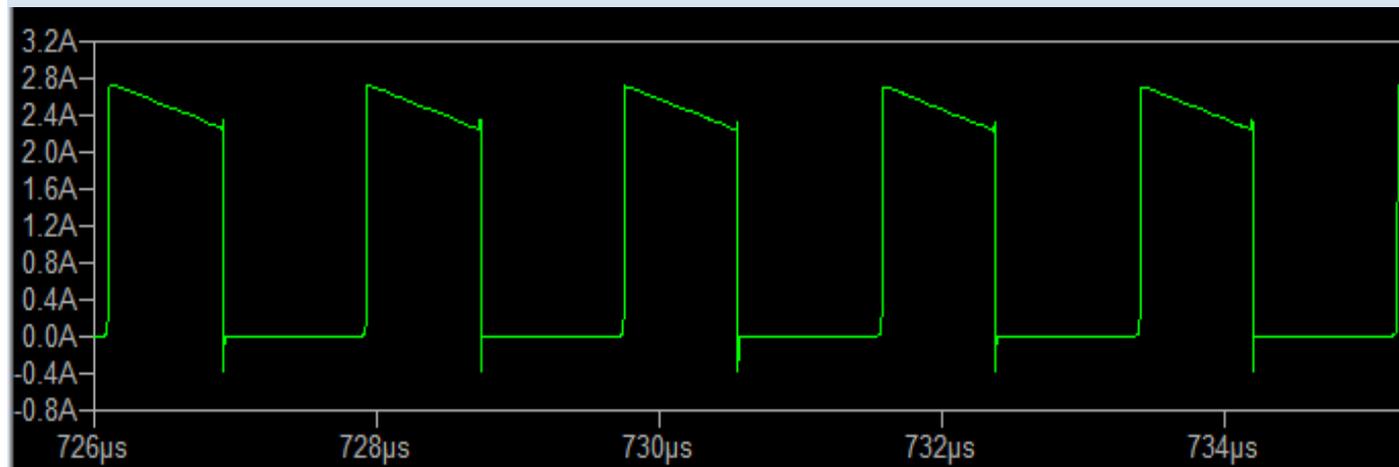

2.75A

$$di/dt = 2.75A$$



Switch current vs inductor current

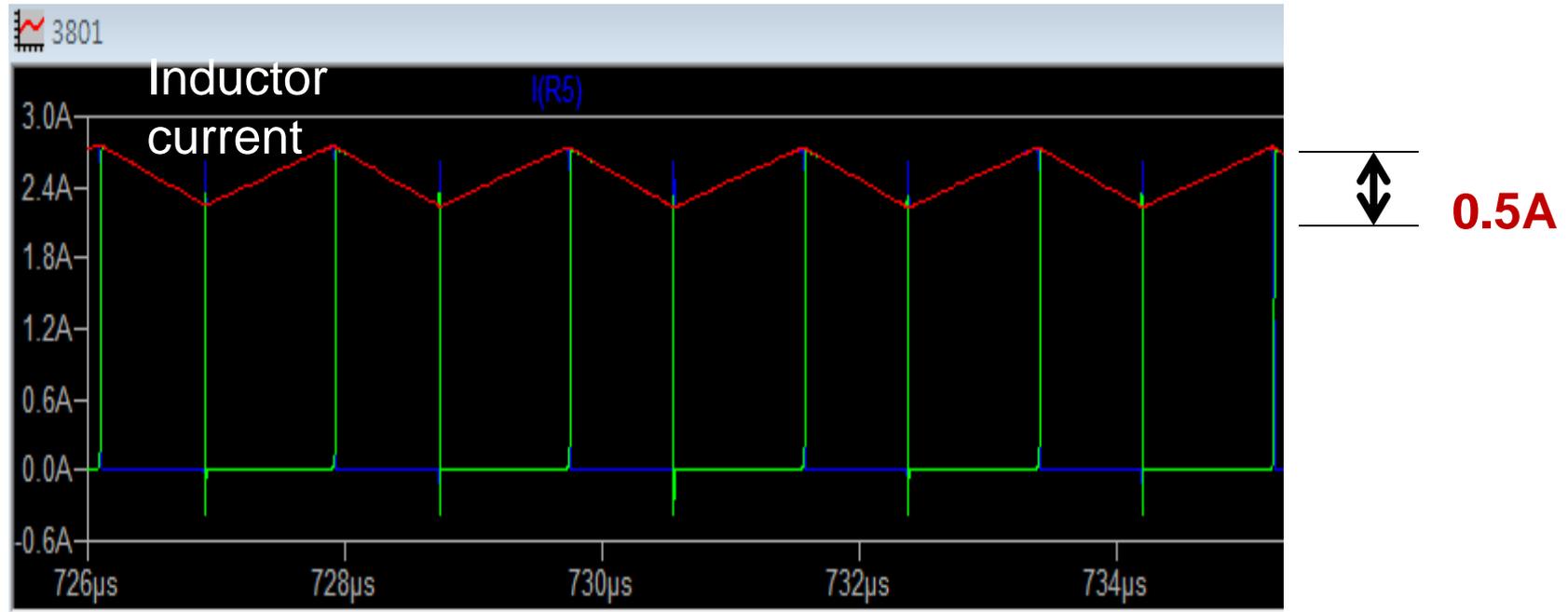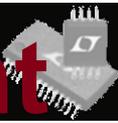

S1 + S2 current waveform =
output inductor current


But $di/dt = 0.5A$

Switch current vs inductor current

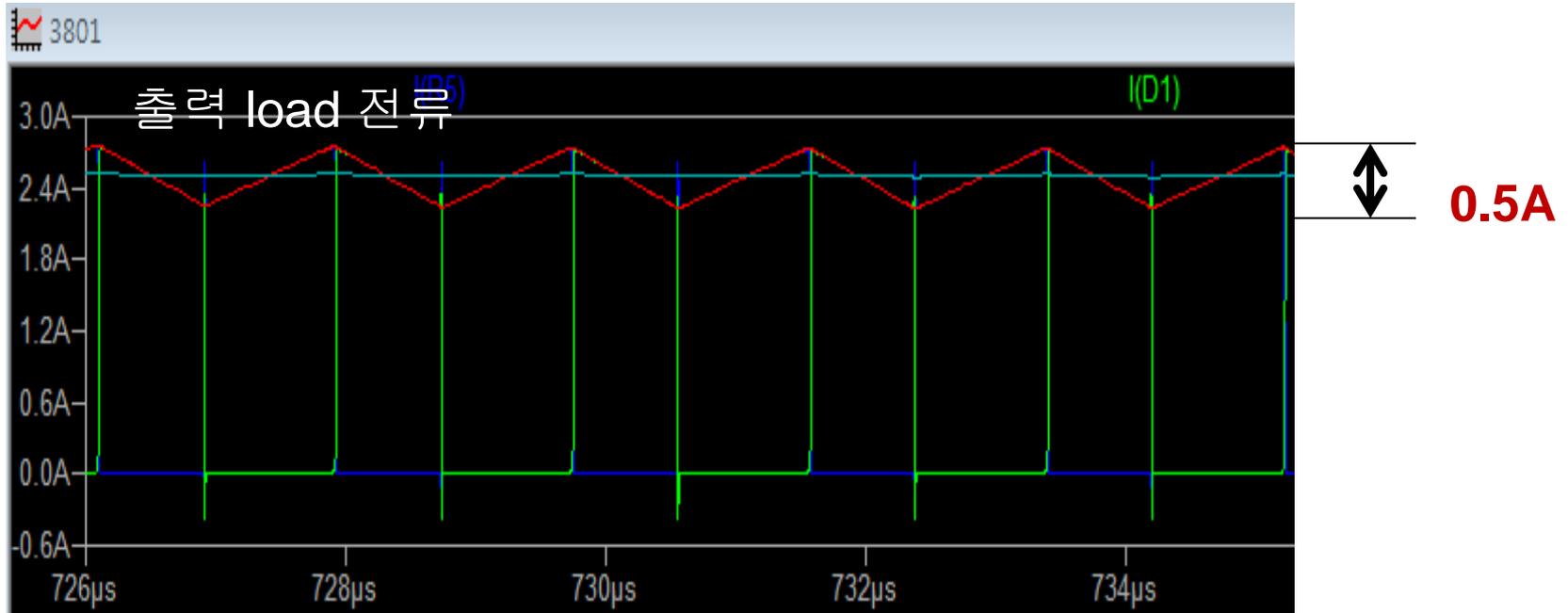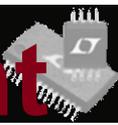

Load current = 2.5A(average inductor current)
But **di/dt** of S1&S2 is **5 times bigger than inductor current.**

Hot Loop on Buck Regulator

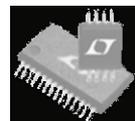

$$V_{\text{noise}} = L * di/dt$$


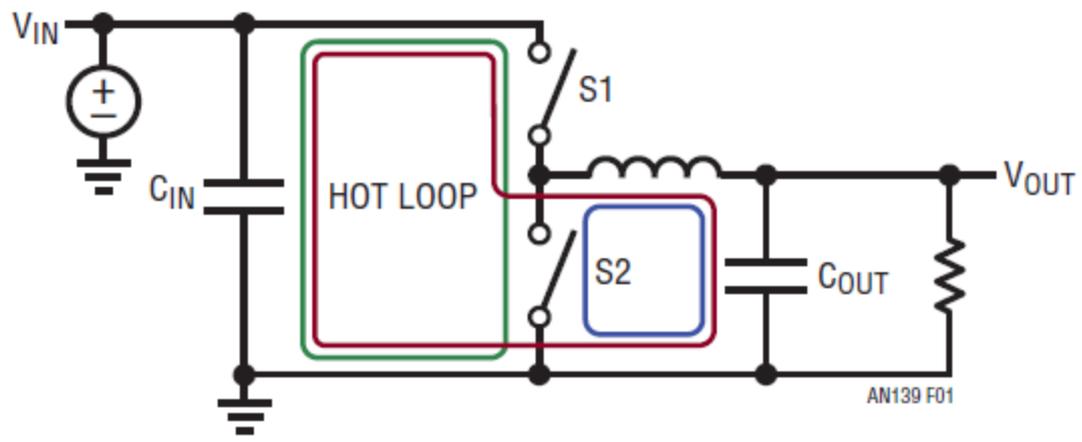


Figure 1

Hot loop area 감소 -> L 값 감소

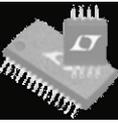

Noise Hot loop as Topology

Hot Loop as topology


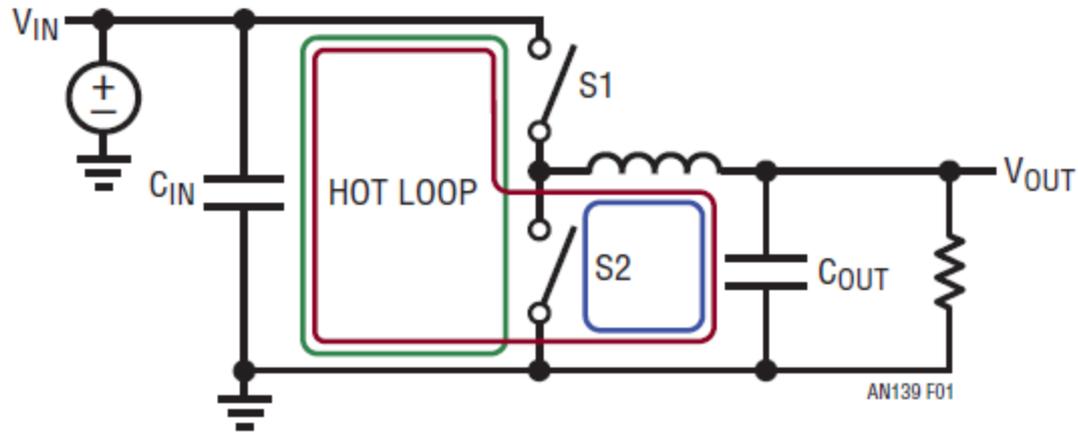
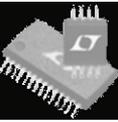
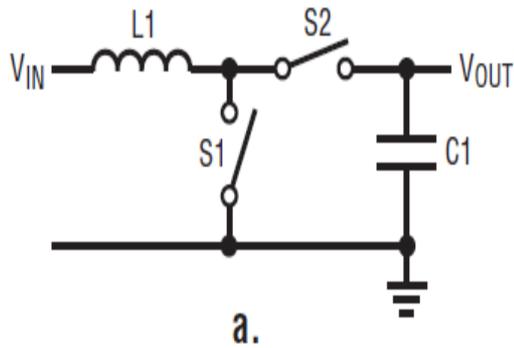


Figure 1


Buck Regulator

Hot Loop as Topology

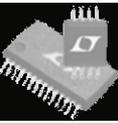


Boost Topology


DISCONTINUOUS MODE

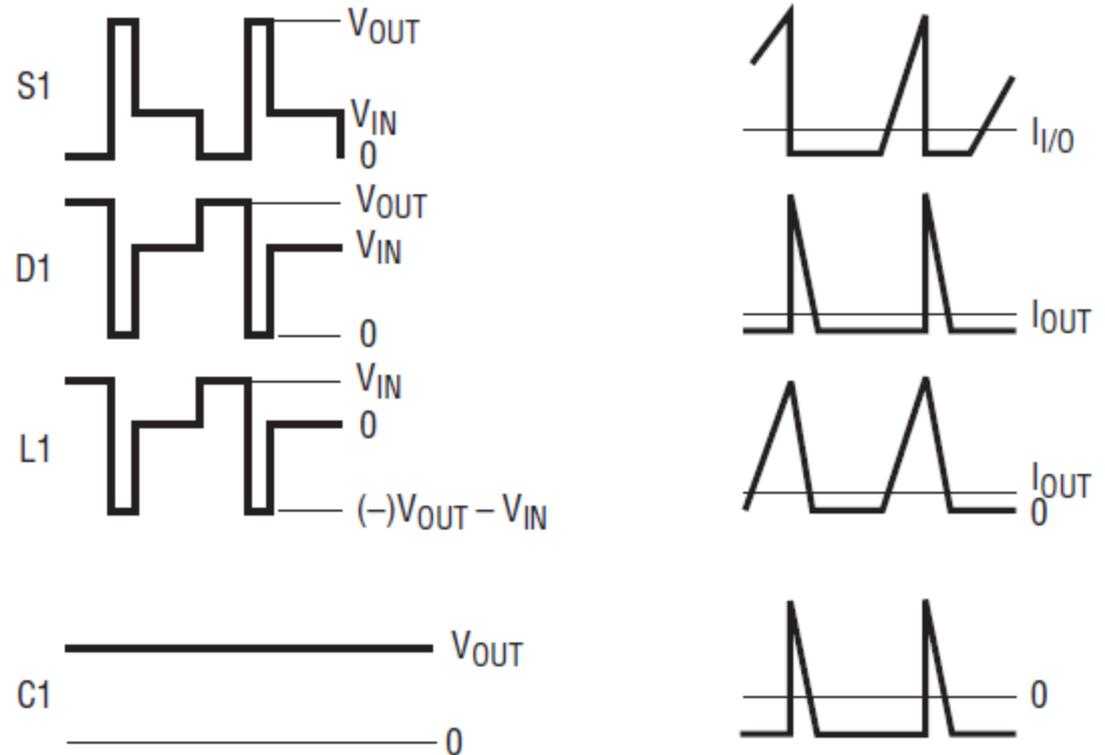


Hot Loop as Topology

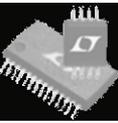



CONTINUOUS MODE

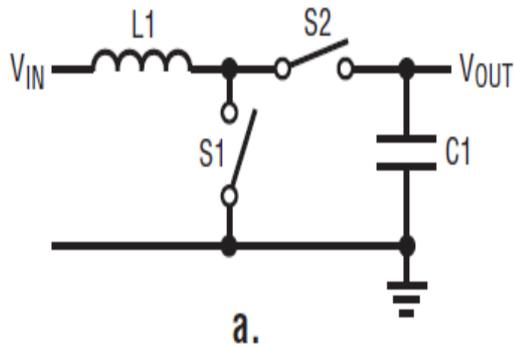

Boost Topology


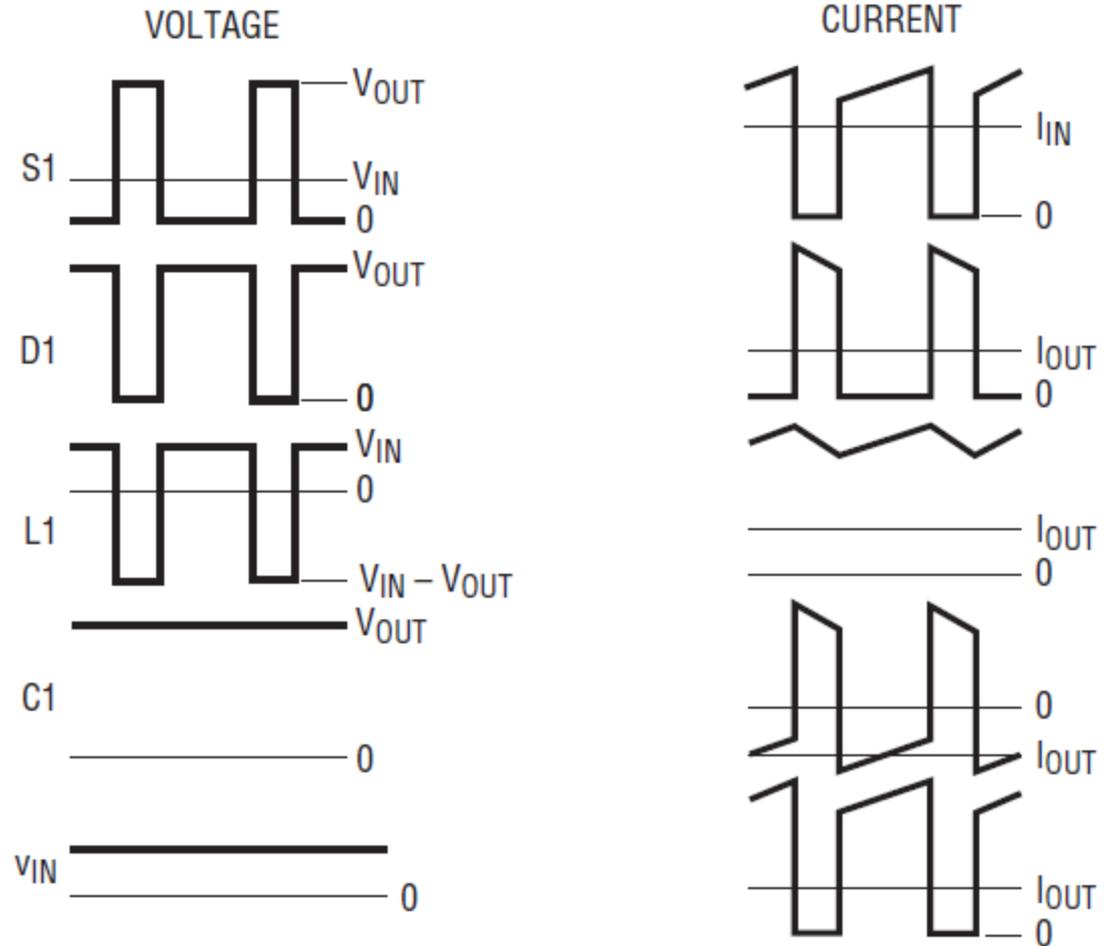


Hot Loop as Topology

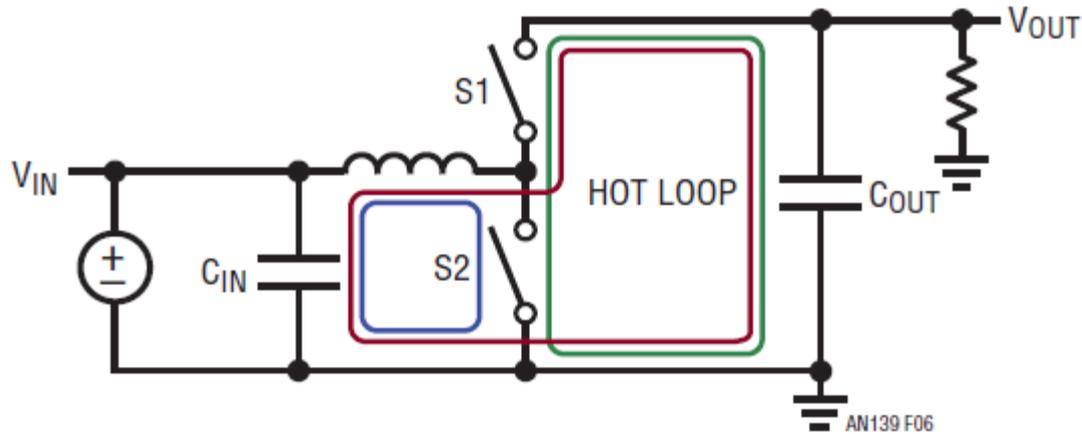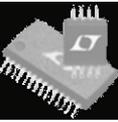



Boost Regulator

Hot Loop as Topology

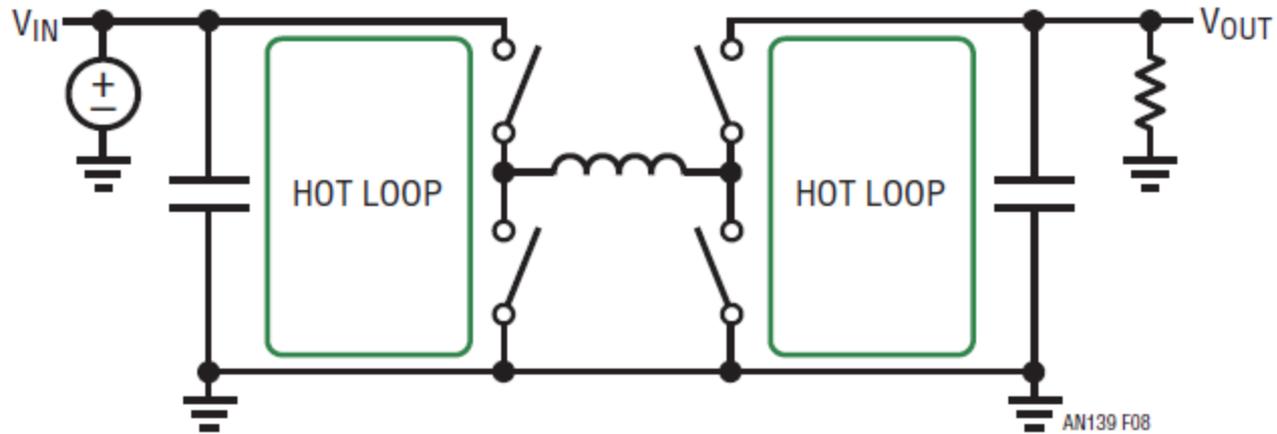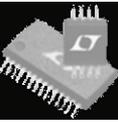



Buck-Boost Regulator

Hot Loop as Topology

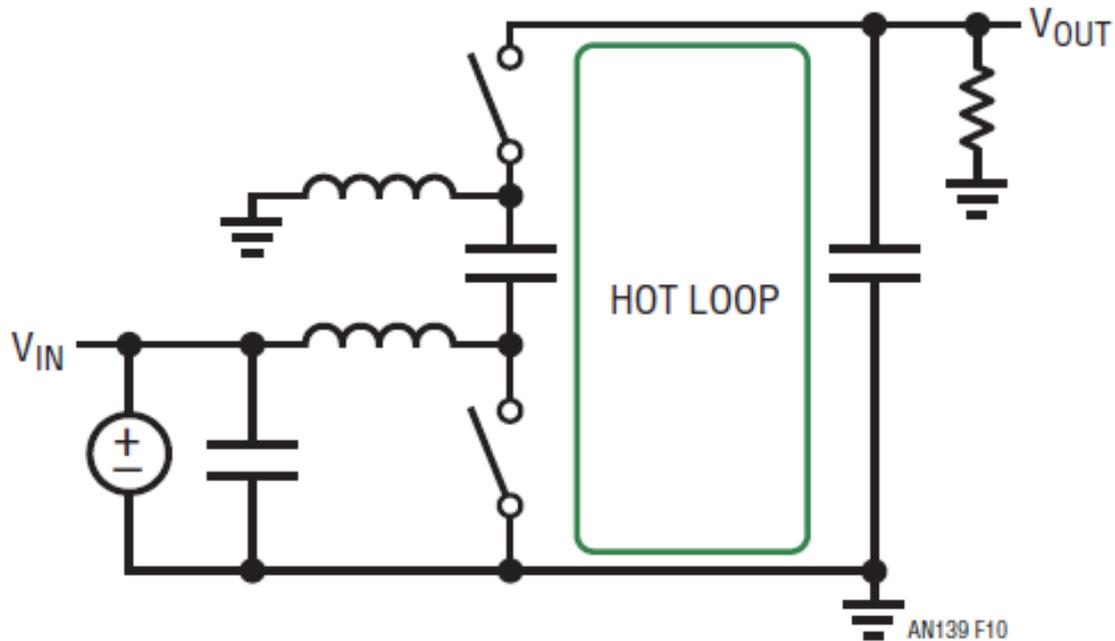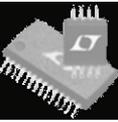


Sepic Regulator


Hot Loop as Topology

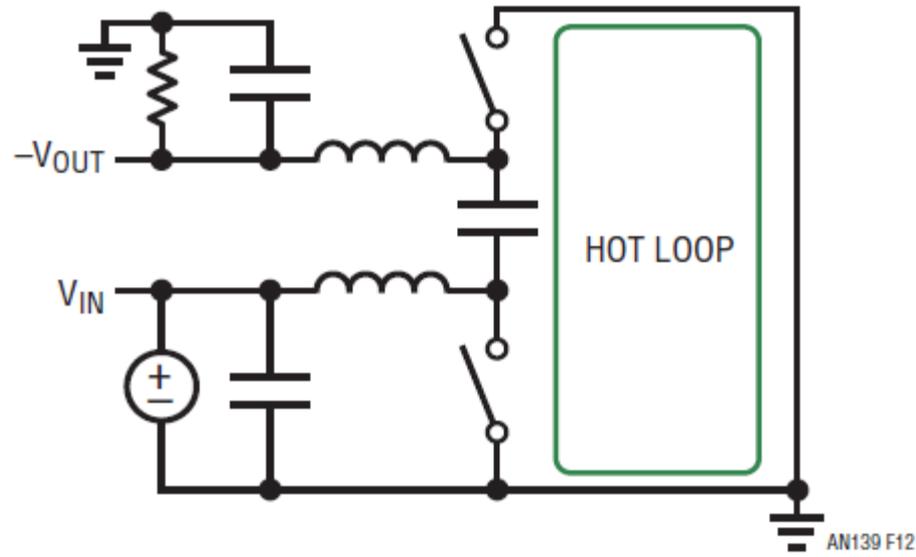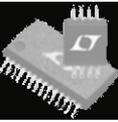


Inverting Regulator

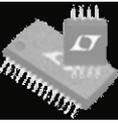


How to reduce EMI Noise?

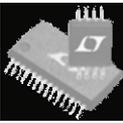


EMI – need to reduce Hot Loop

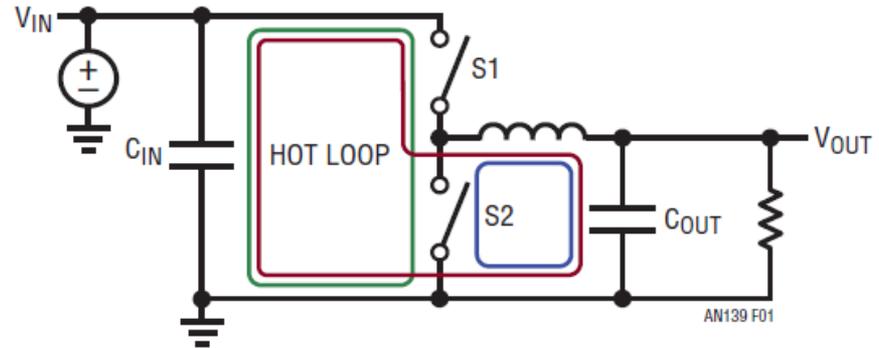


EMI Performance

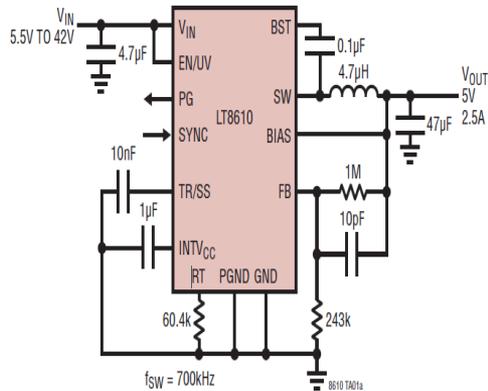

Synchronous
Monolithic





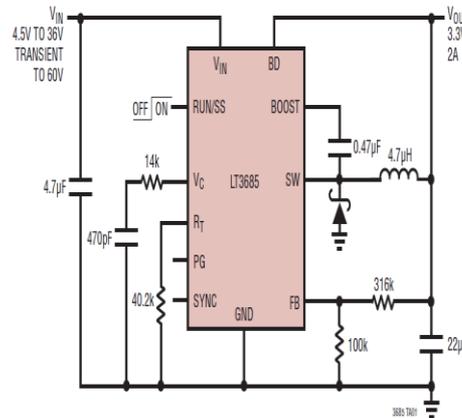


Non-Synchronous
Monolithic

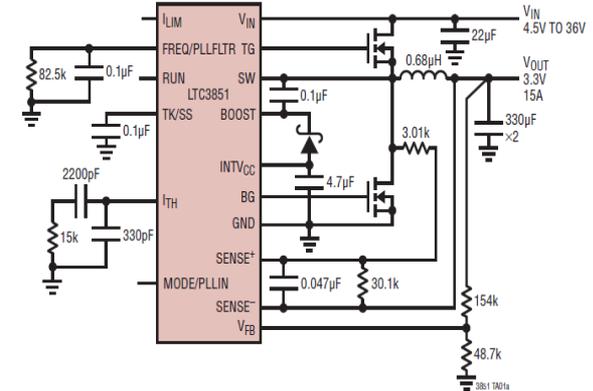


Controller


Hot loop size = EMI Performance

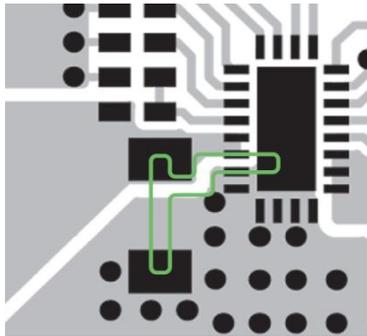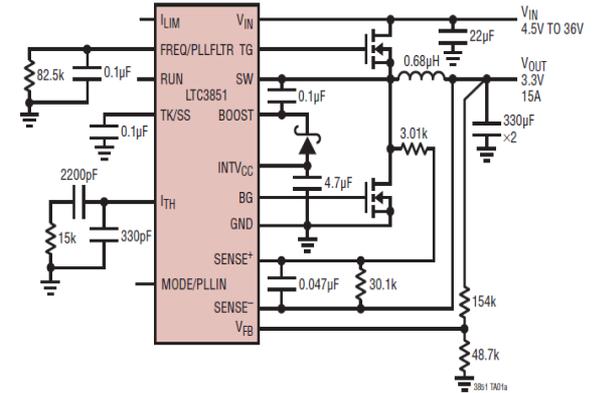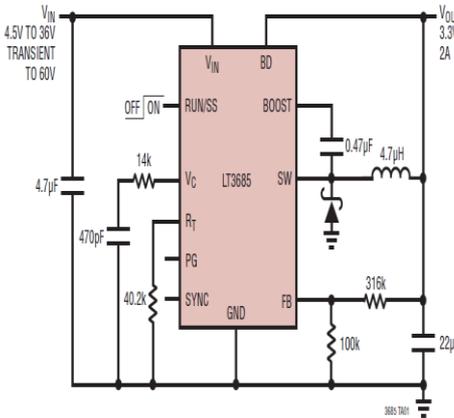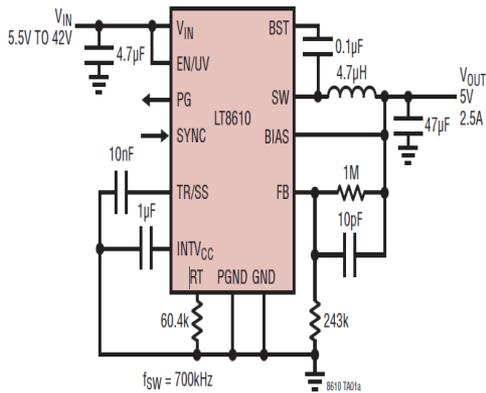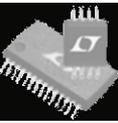


Synchronous Monolithic

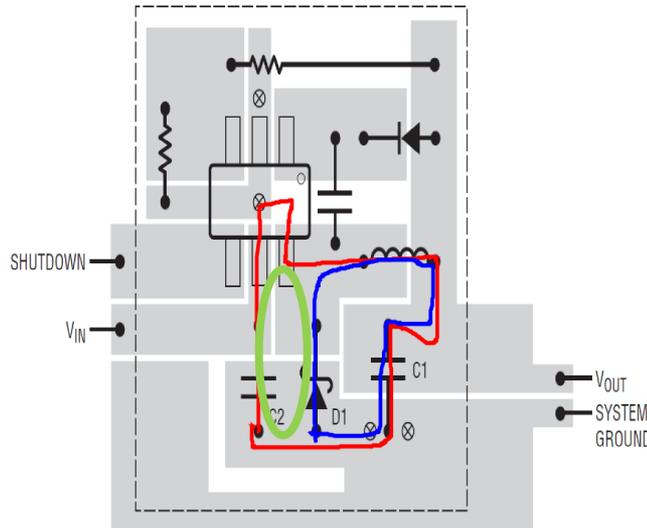

Non-Synchronous Monolithic



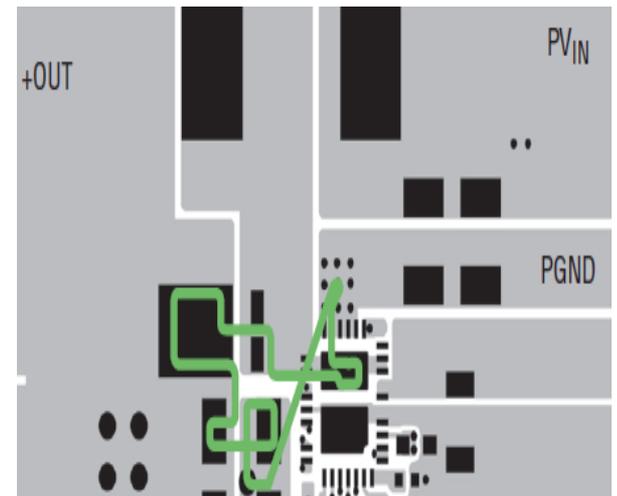


Controller

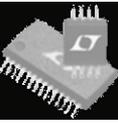


Layout Guide

Layout guide - Input capacitor

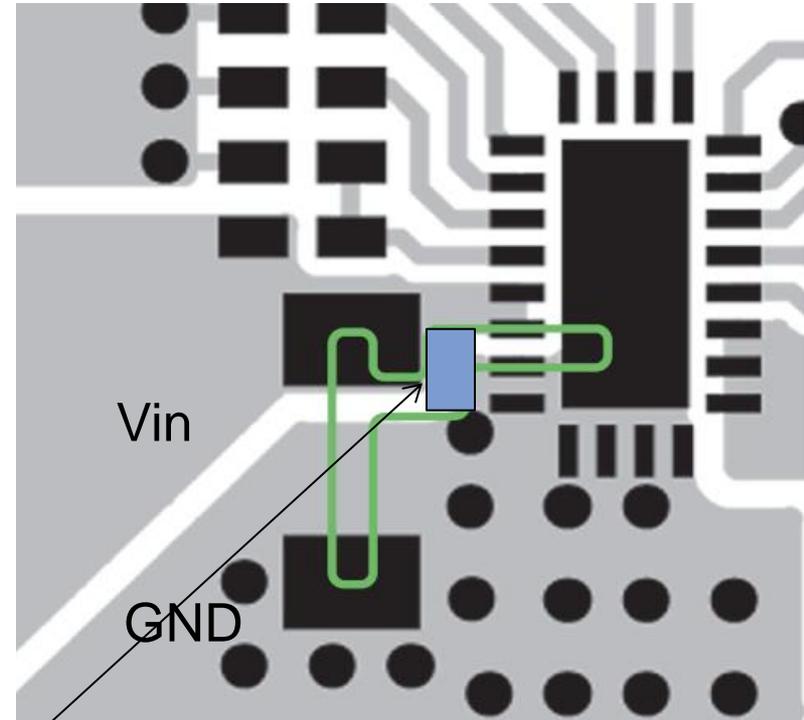
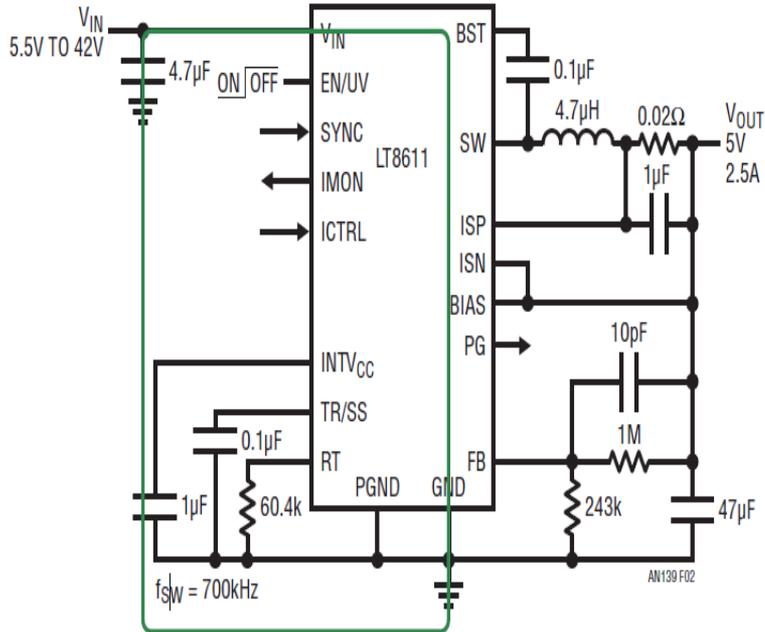
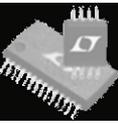


작은 입력 cap 배치 시 hot loop 더 줄일 수 있음.
0.1uF 정도 배치하면 좋음.

Layout guide - Input capacitor



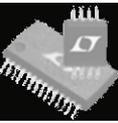


$$V = L * di/dt$$

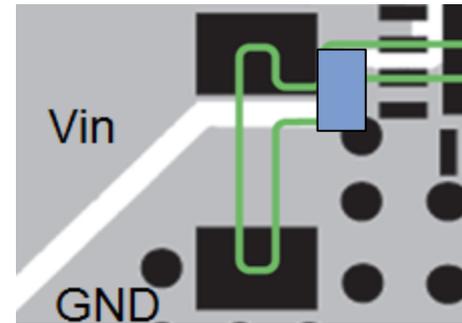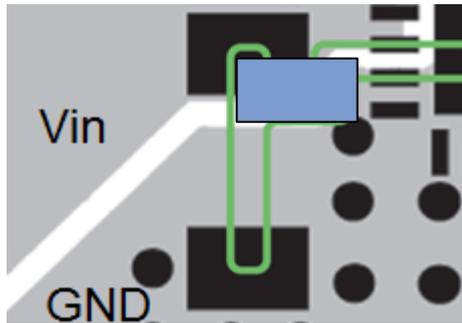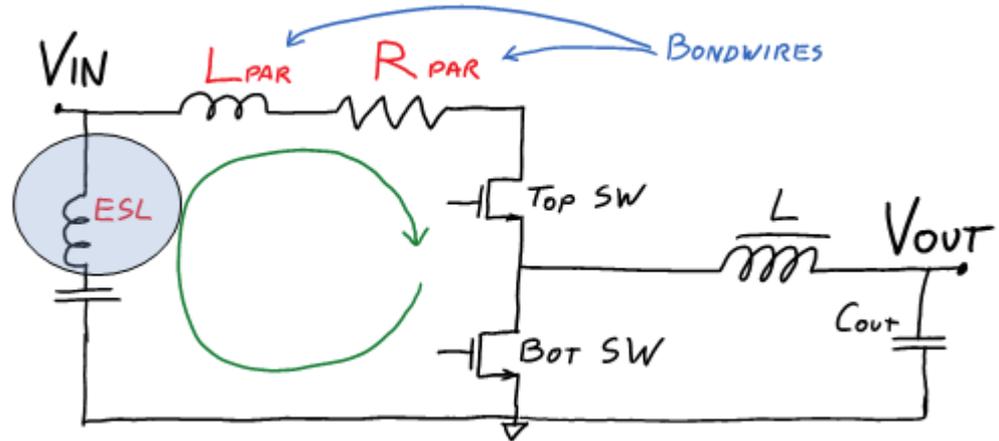

ESL 이 작은 Cap 이 더 좋음 : Capacitor 가로 면적이 넓으면 ESL이 낮음

Layout guide - GND copper

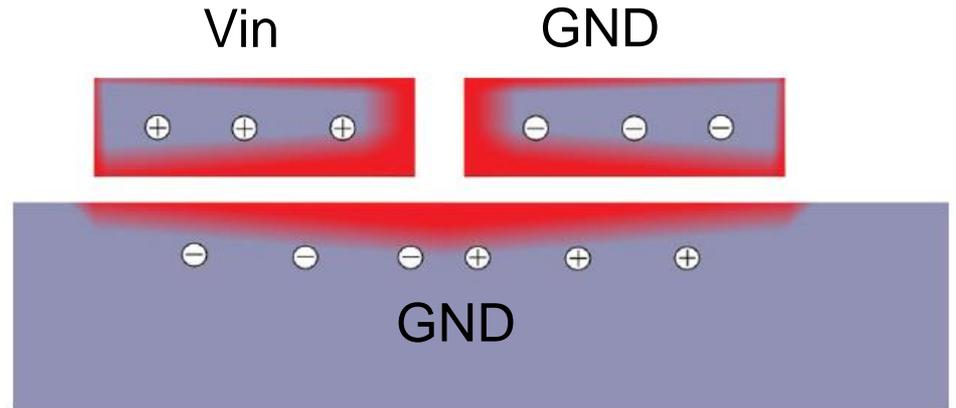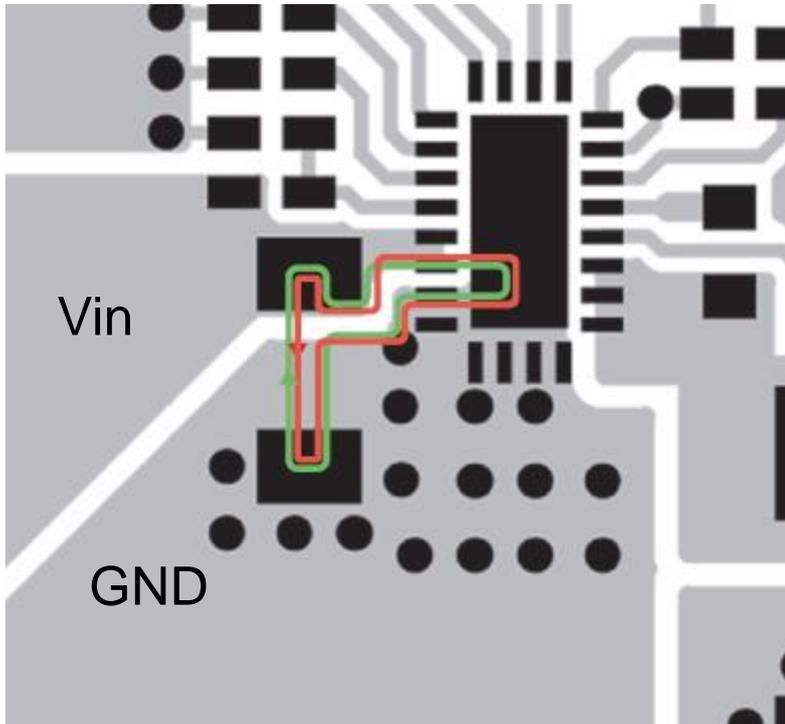
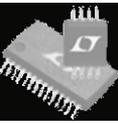


PCB 단면적 전류밀도

Green : Top 면 흐르는 전류(시계방향)



Red : 2nd layer GND plane 에 흐르는 전류(반 시계방향)

Layout guide - GND copper

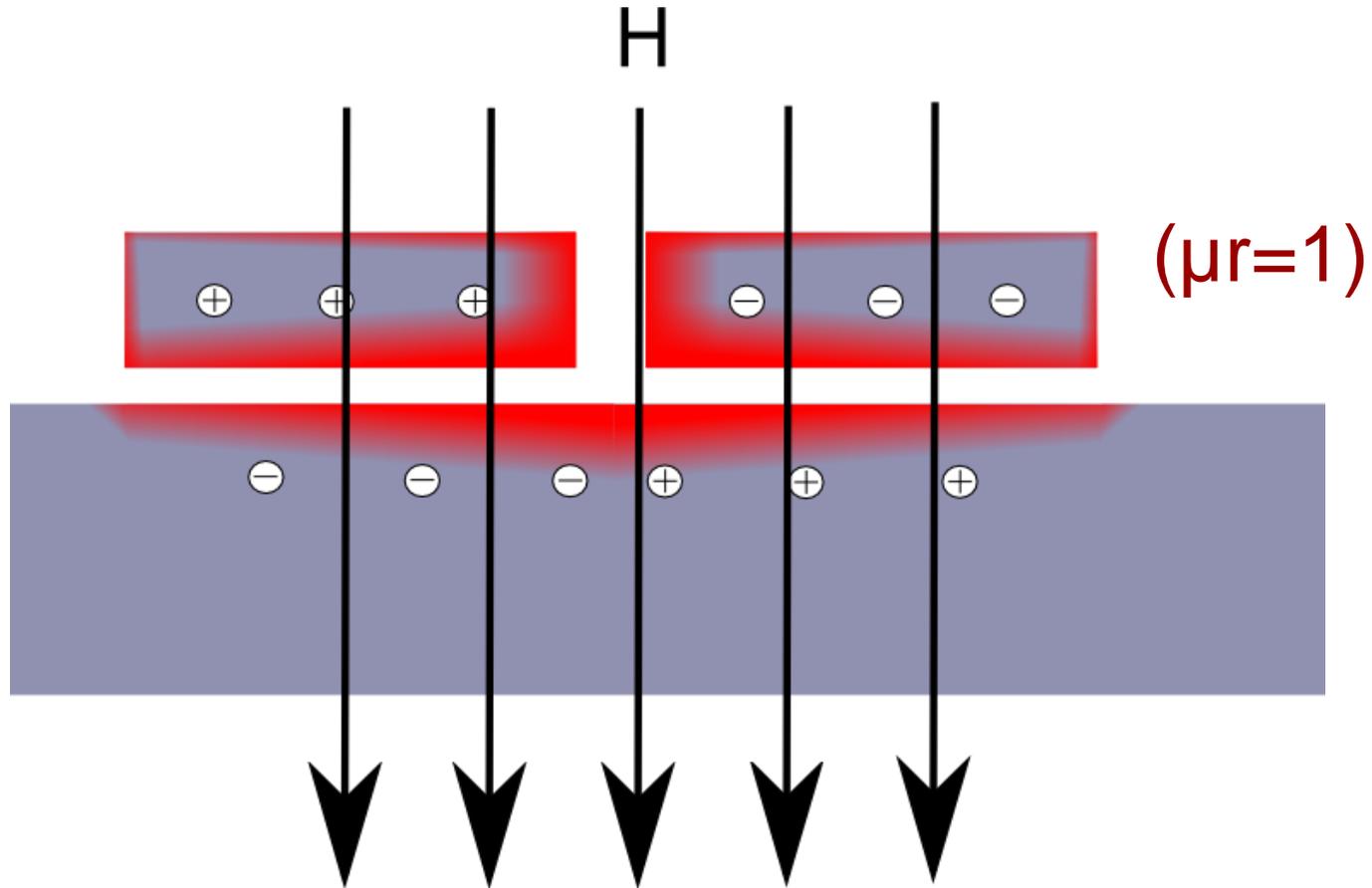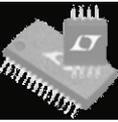


만약 밑에 GND copper가 없다면 큰 자기장 성분이 board 안으로 들어감.

Layout guide - GND copper

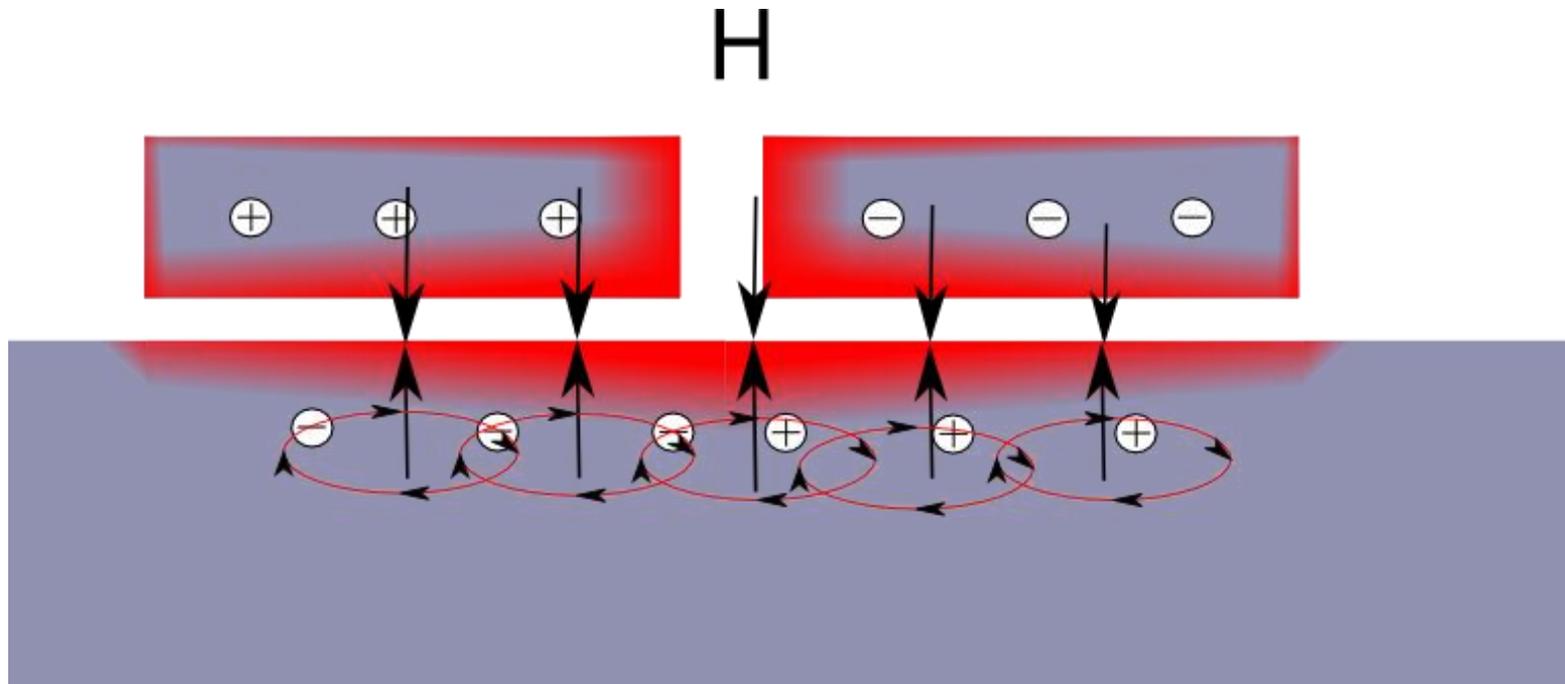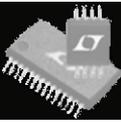

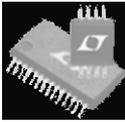도체인 GND copper 가 유도된 자기장에 의해 수직인 전류 생성, GND copper의 전류는 Top 면과 반대로 흐르는 전류. 이 Eddy current가 전체 자기장의 크기를 낮춤.




Inner GND copper layer

Table 1


d (mm)	f (MHz)	C (pF)	L (nH)		FACTOR OVER 0.12mm
	18, 4	400	187	Single-Layer Open Loop	14, 4
	21, 2	400	141	Inner Copper Short-Circuit Loop	10, 85
1, 5	38, 9	400	42	Solid Plate	3, 23
1, 5	34, 7	400	53	Rectangular Loop No Overlap	4, 08
0, 5	52, 1	400	23	Thin Rectangular	1, 77
0, 27	55	400	21		1, 61
0, 12	69	400	13	Paper	

A solid plane on the next layer in a multilayer board (four layers or more) will have over 3× less inductance than a normal 1.5mm 2-layer board with a solid bottom plane, and over 14× less over a single-layer board. A solid plane with minimum distance to the hot loop is one of the most effective ways to reduce EMI.


Layout guide - Land Pattern

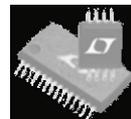


Undesired

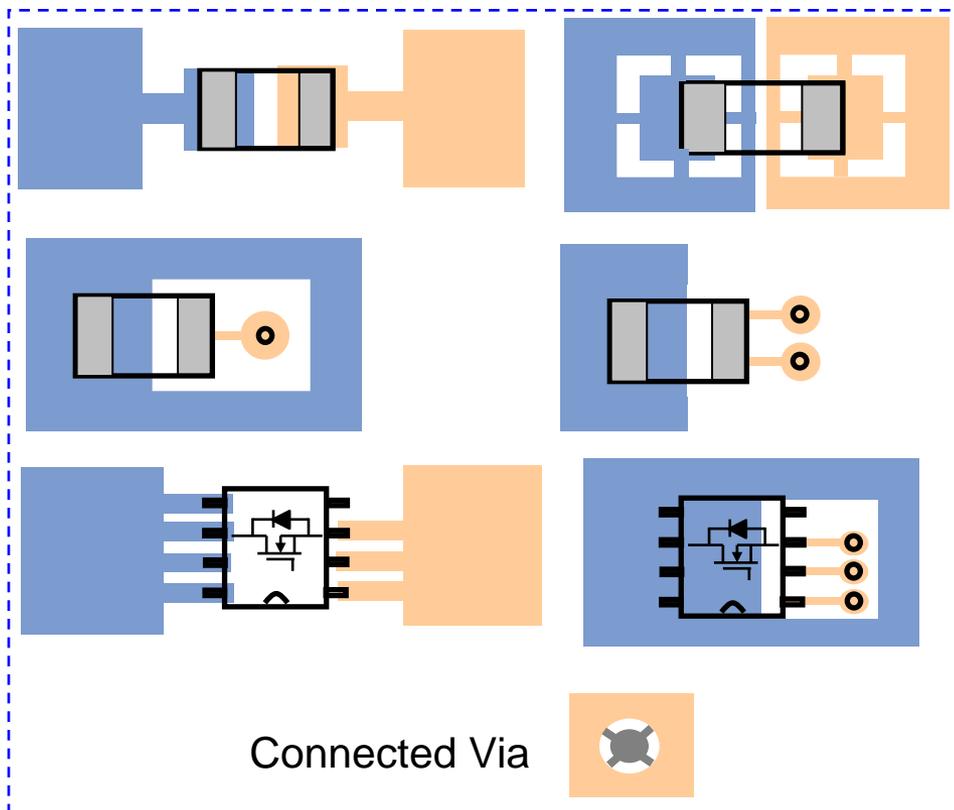

Desired

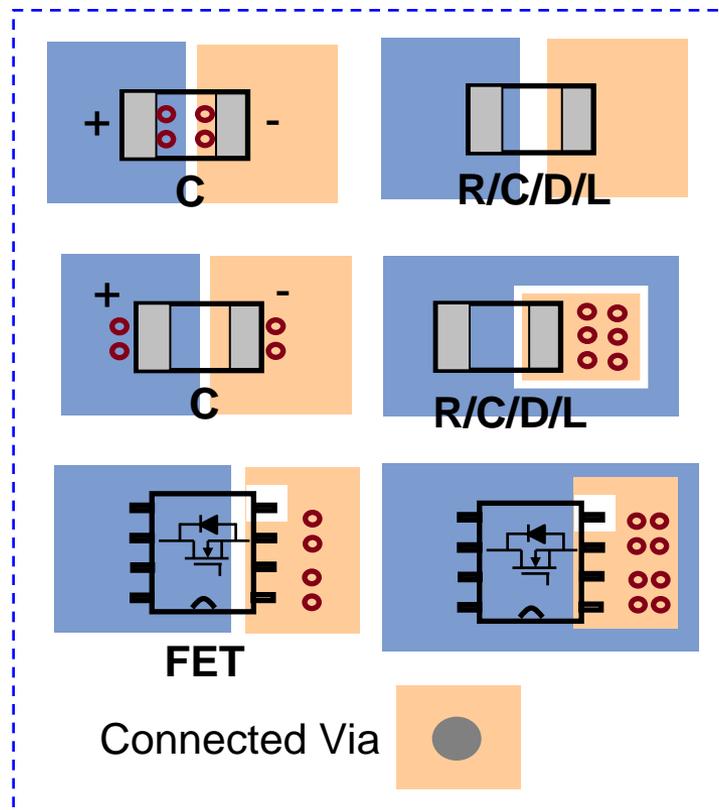


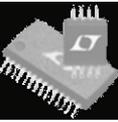- Use wide / short copper trace for power components
- Use multiple vias for inter-layer connections
- Avoid improper use of “thermal relief”
- **Minimize resistance and inductance**




LTC EMI Solution



Spread Spectrum Oscillator

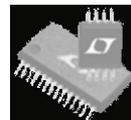

2.25MHz, 2.5V/8A Step-Down Regulator

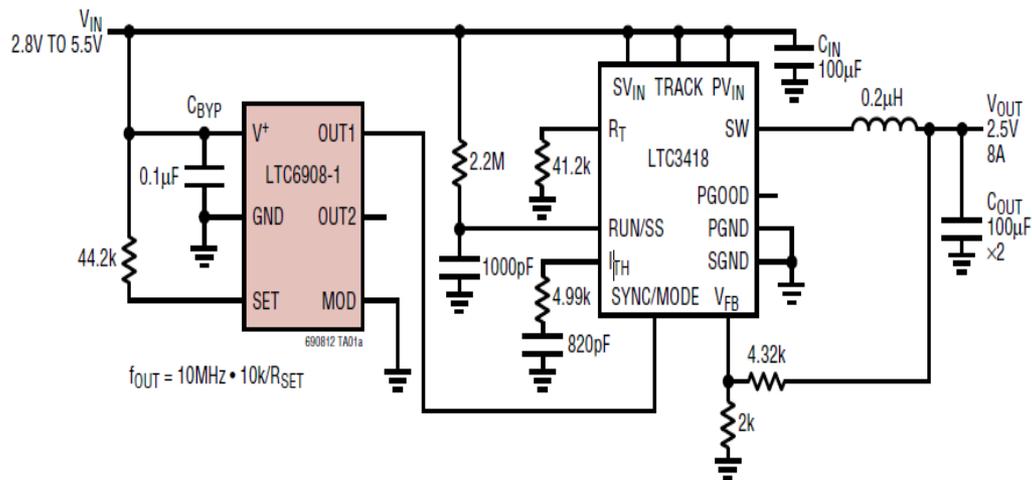

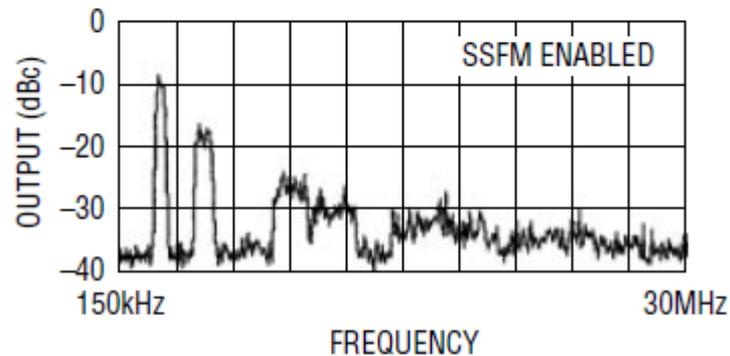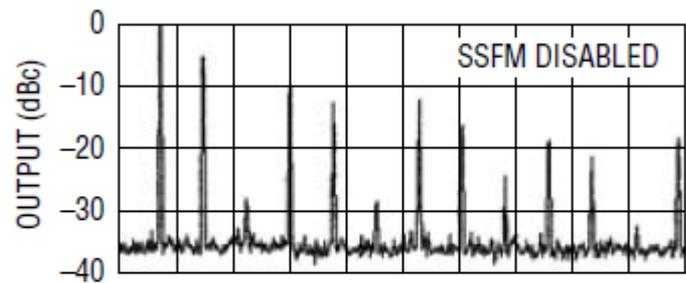150kHz to 30MHz Output Frequency Spectrum (9kHz Res BW)



주파수 가변 및 Spread Spectrum function
으로 10dB 이상 Margin

Spread Spectrum Oscillator


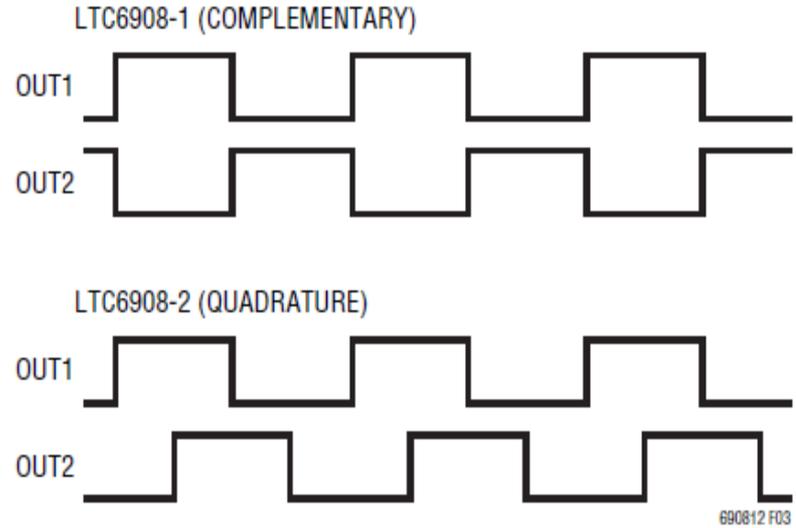
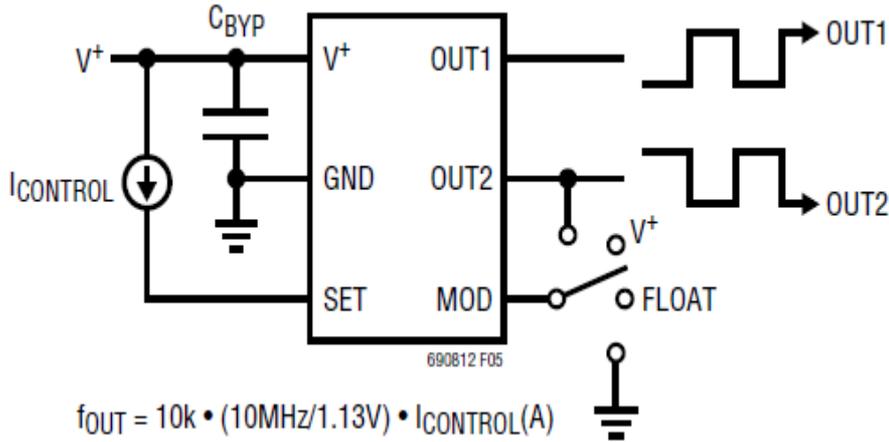
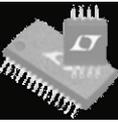



Figure 3. Output Waveforms for LTC6908-1, LTC6908-2

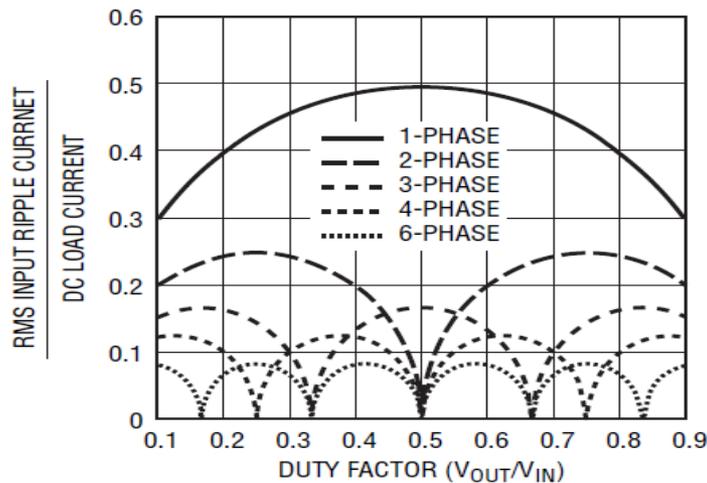

3729 F04


Figure 4. Normalized Input RMS Ripple Current vs Duty Factor for 1 to 6 Output Stages


di/dt 감소!!

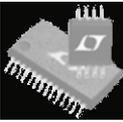


LTC Pinout Advantage

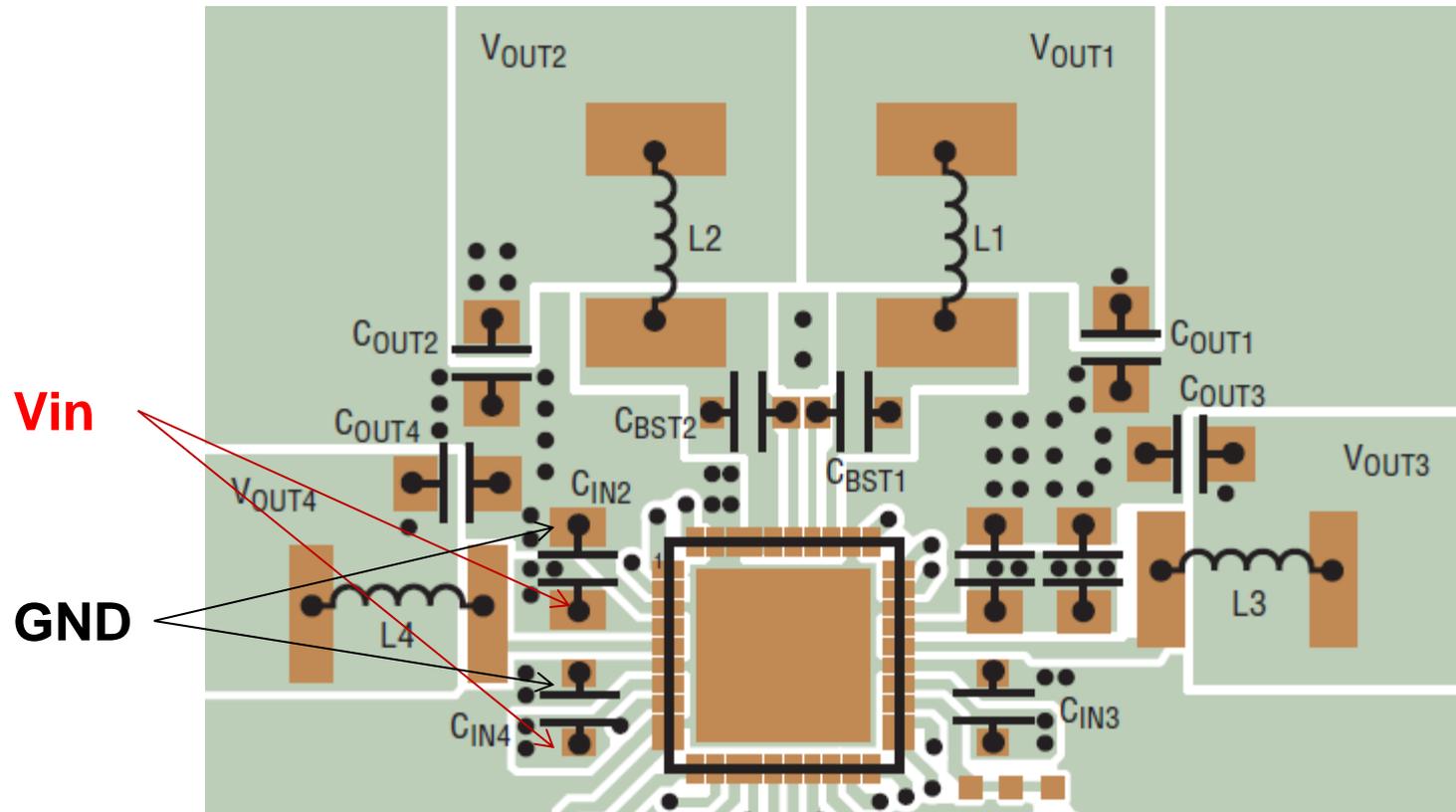EMI and layout friendly pinouts enable perfect low RFI solutions




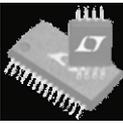


Automotive Low EMI IC's – LTC Design Advantage

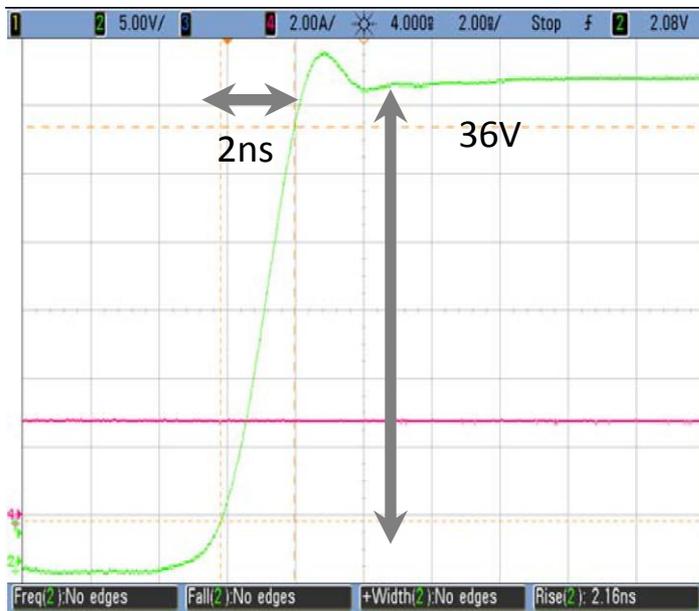


LT8614 – Silent Switcher™

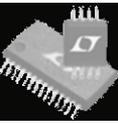


- 42V, 4A Sync buck
- Low EMI
- Max Output = 4A
- Ultra-Fast $T_{ON(MIN)}=25ns$
- 88/40m Ω $R_{DS(ON)}$ Switches
- 18-Lead QFN 3x4

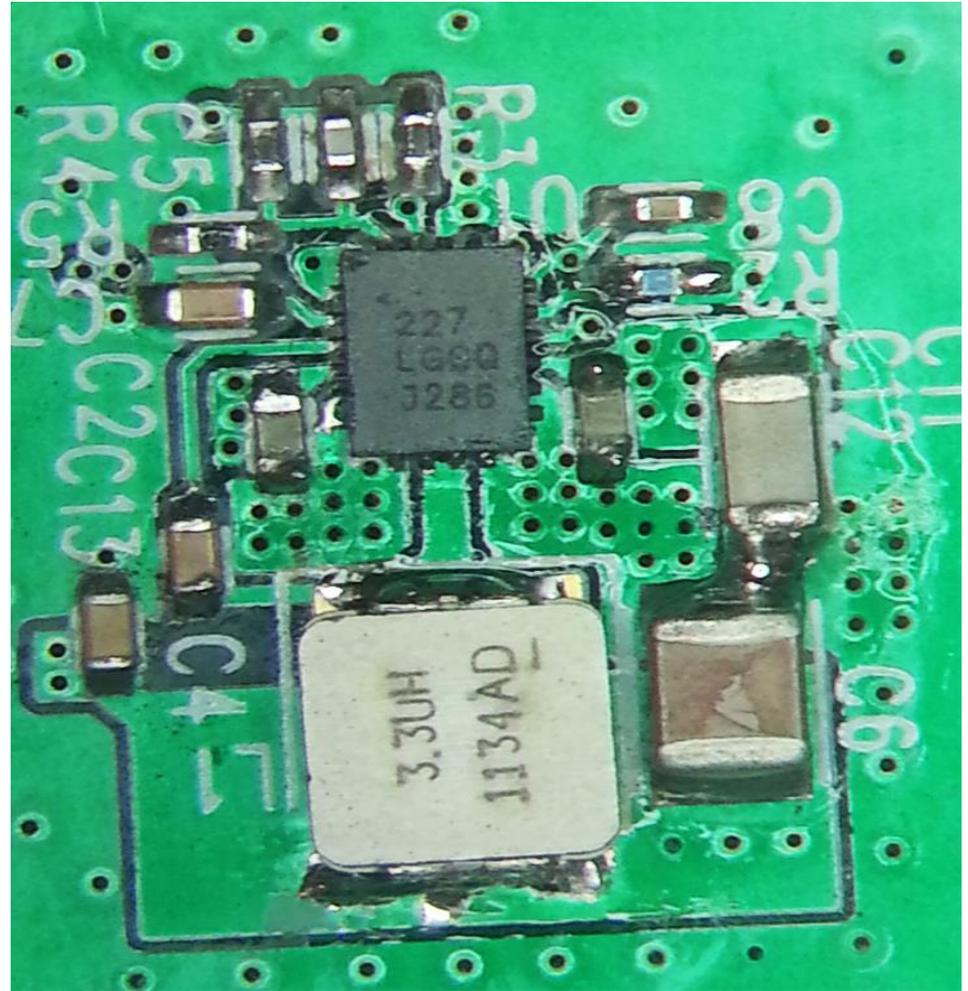

LT8614 – Silent Switcher

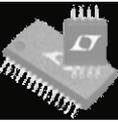


LT8610: A Synchronous Buck Regulator

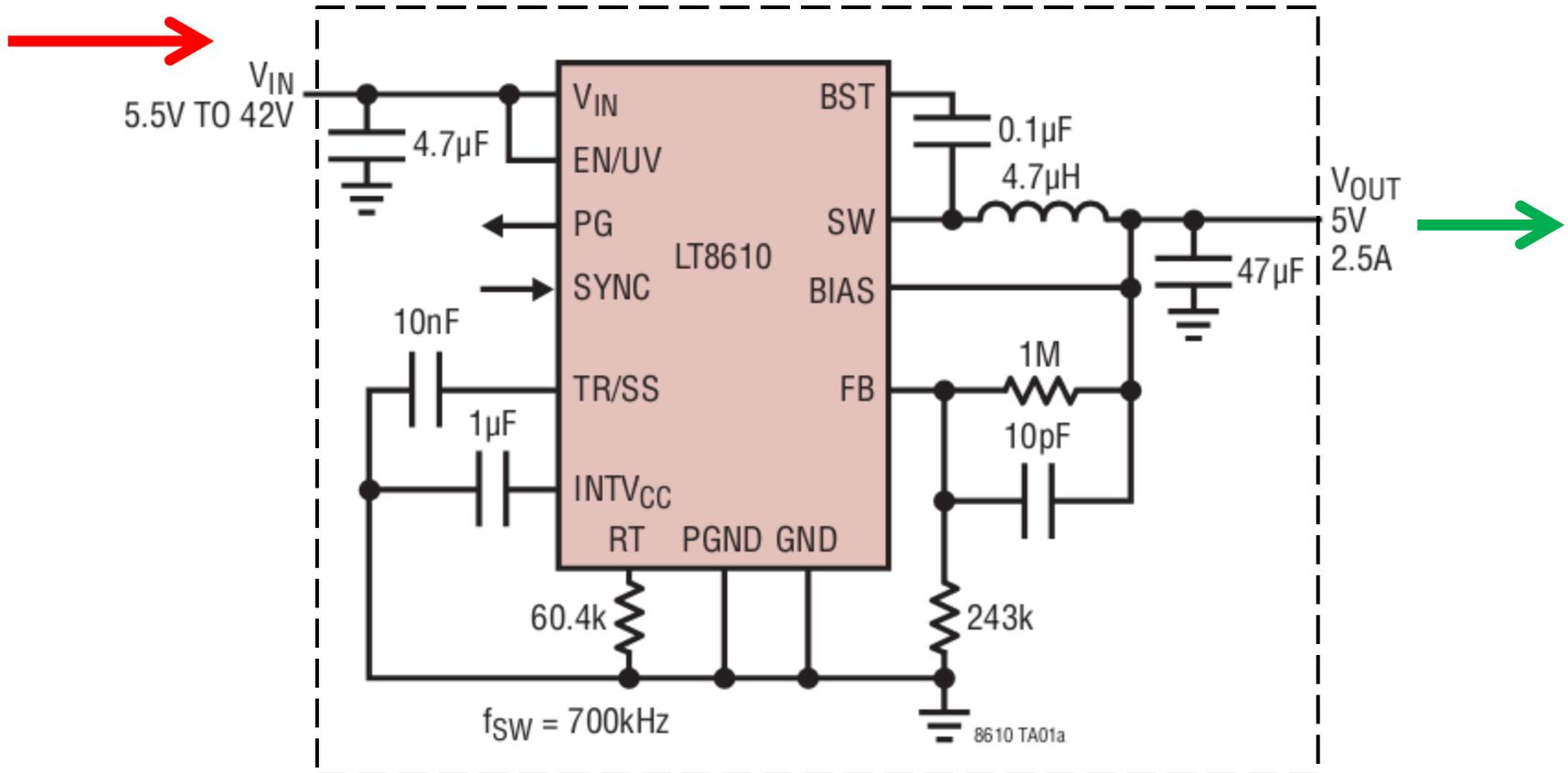

-LT8614-

LT8614 – Silent Switcher

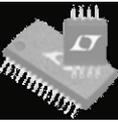



Customer Needs vs. LT8610

1. Lower EMI with simple PCB
2. Higher efficiency (at >2MHz)
3. Smaller Footprint
4. ????

Fundamental Limitations



1. C_{VIN} parasitic L
2. Bond-wire parasitic L+R

LT8614 – Silent Switcher

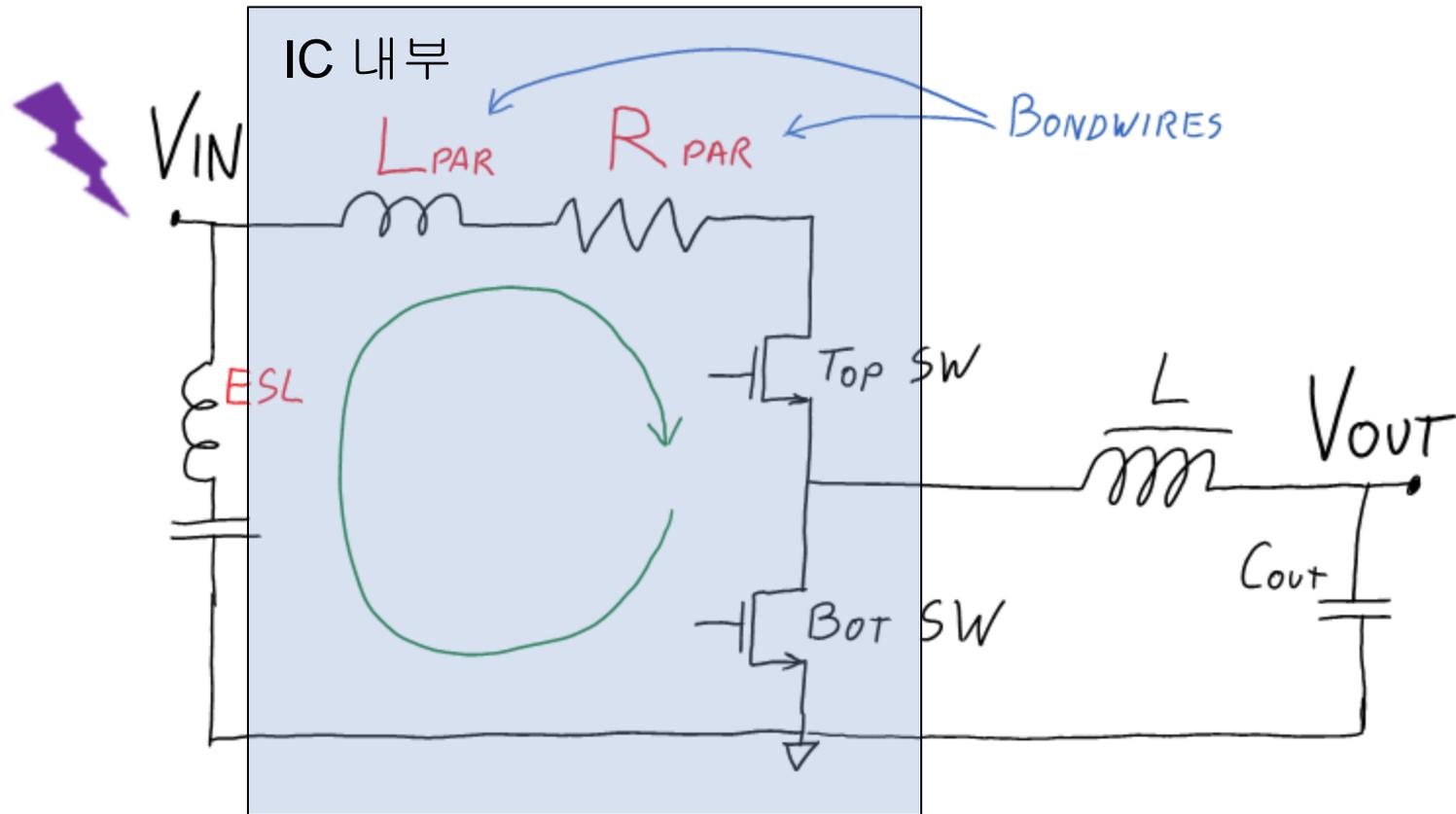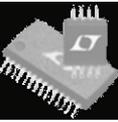


Synchronous Buck : Parasitic L+R

LT8614 – Silent Switcher

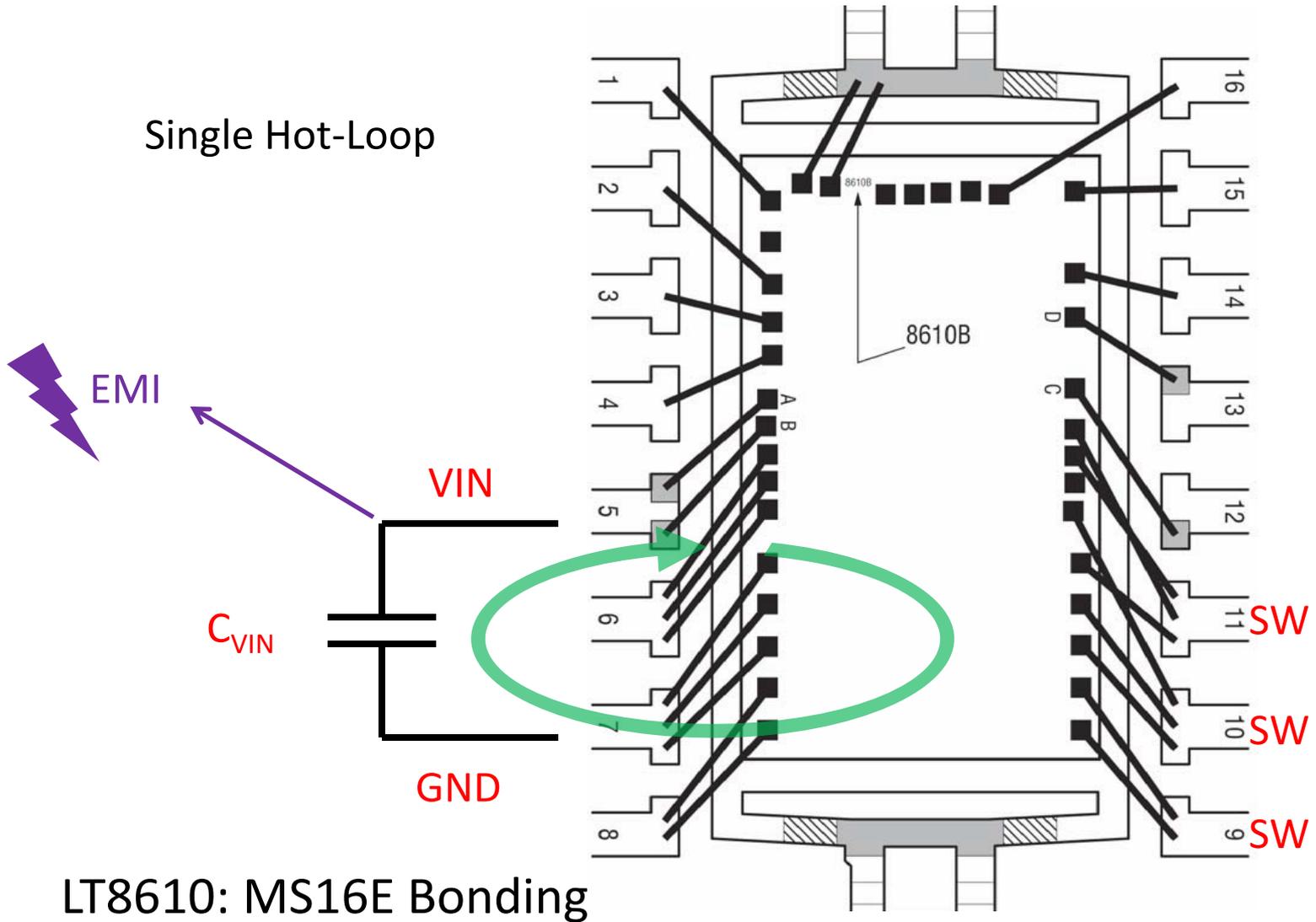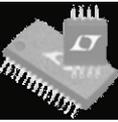


LT8610: MS16E Bonding

LT8614 – Silent Switcher

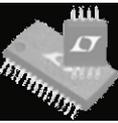

Dual Hot-Loop
+
Coupled Loops


Much Lower
Total Inductance
+
Lower EMI

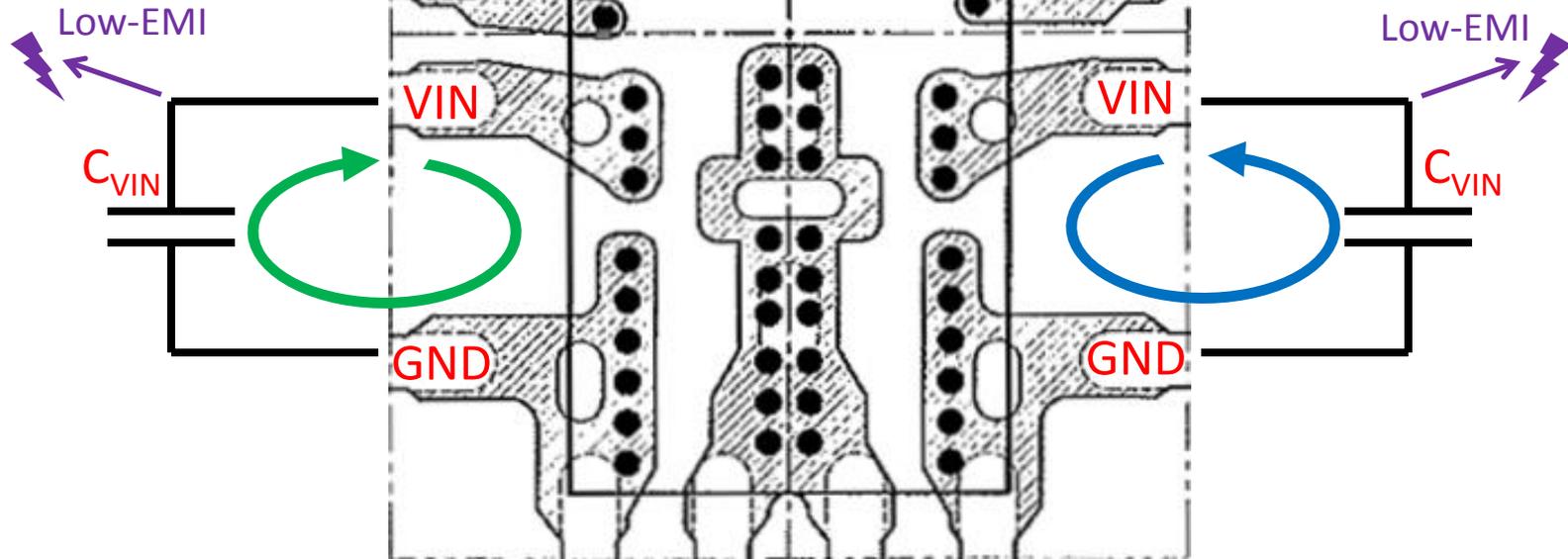

LT8614: QFN Flip-Chip


SW

LT8614 – Silent Switcher

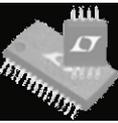


Confined
Magnetic Field
+
Low EMI


Coupled Hot Loops

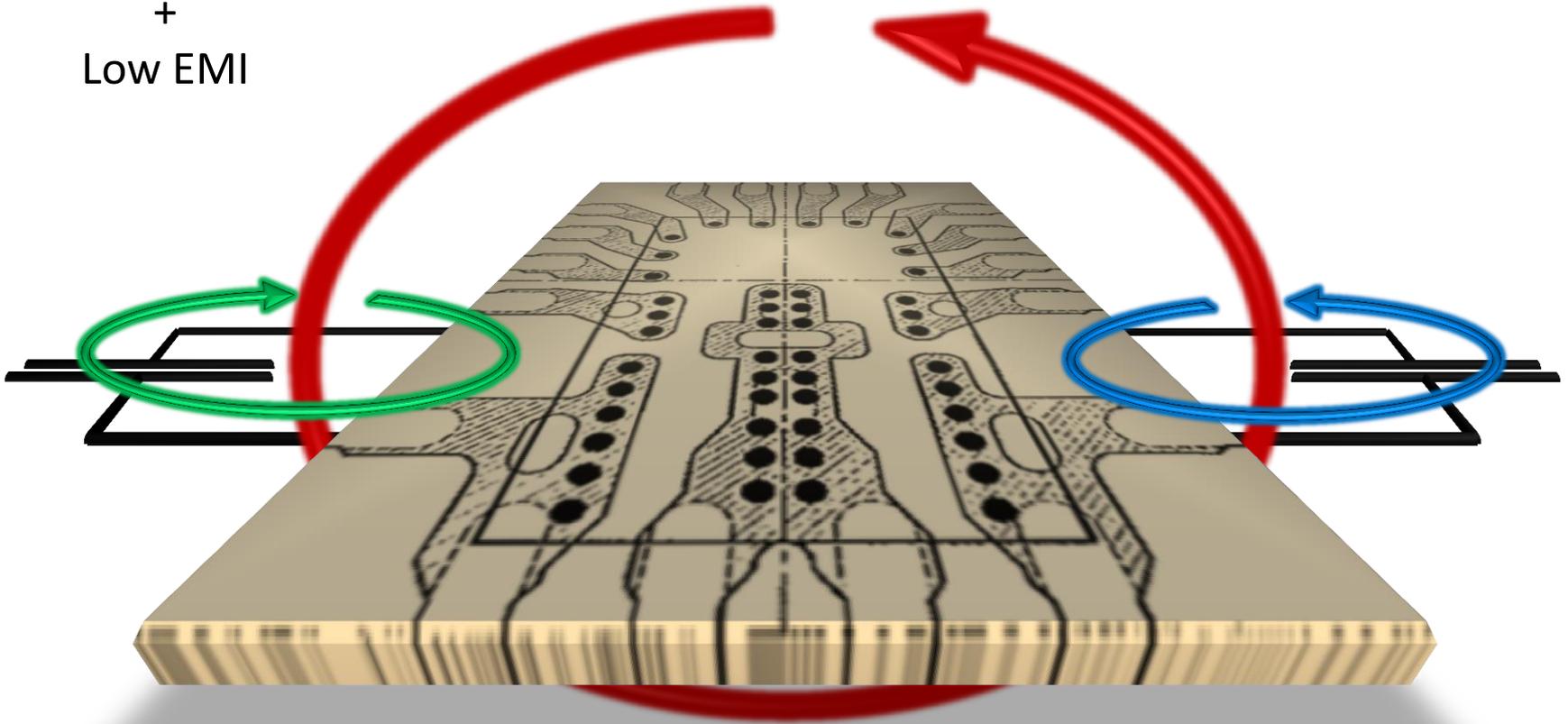


LT8614 – Silent Switcher

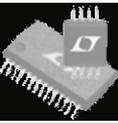


Field in a Toroid

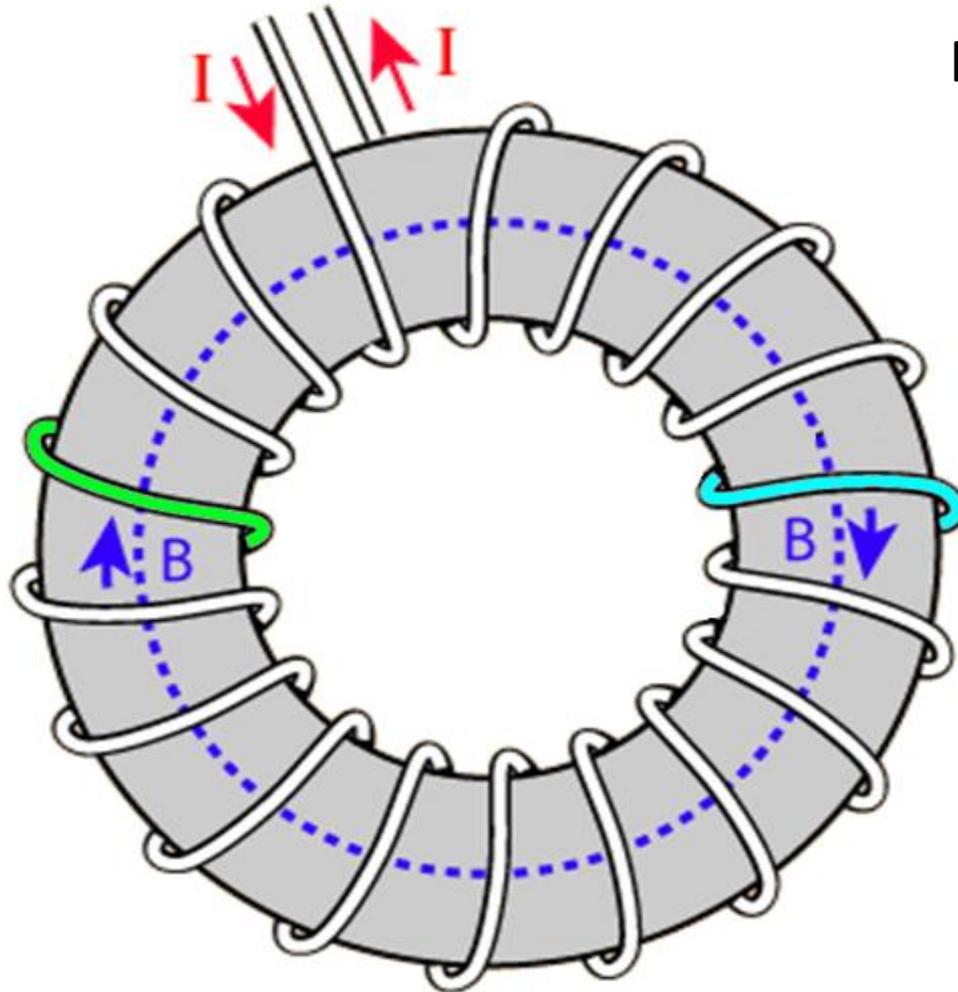

LT8614 – Silent Switcher


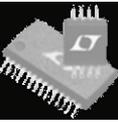


Electric loop sees
no net magnetic field

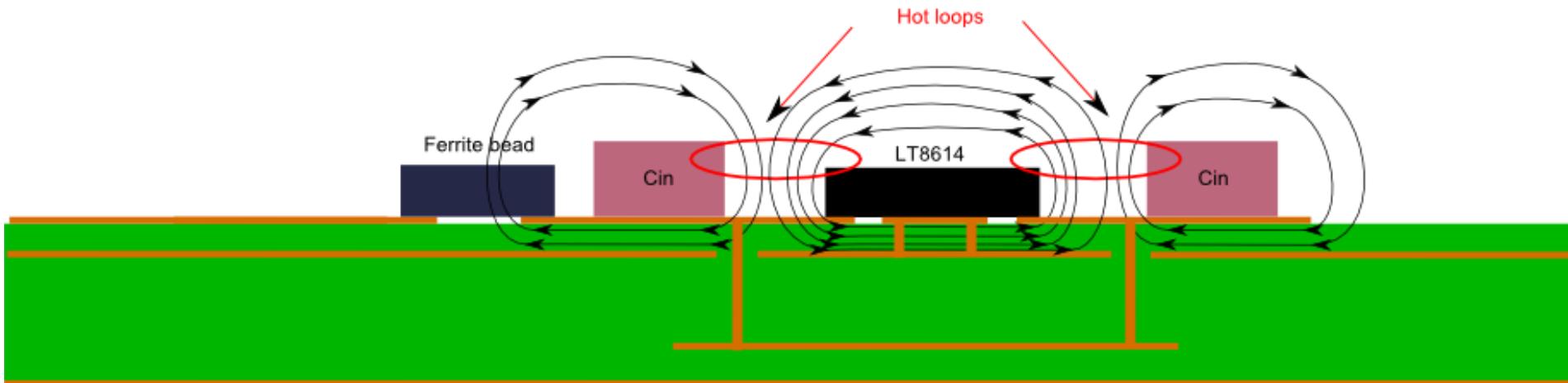



How does it work

LT8614 – Silent Switcher

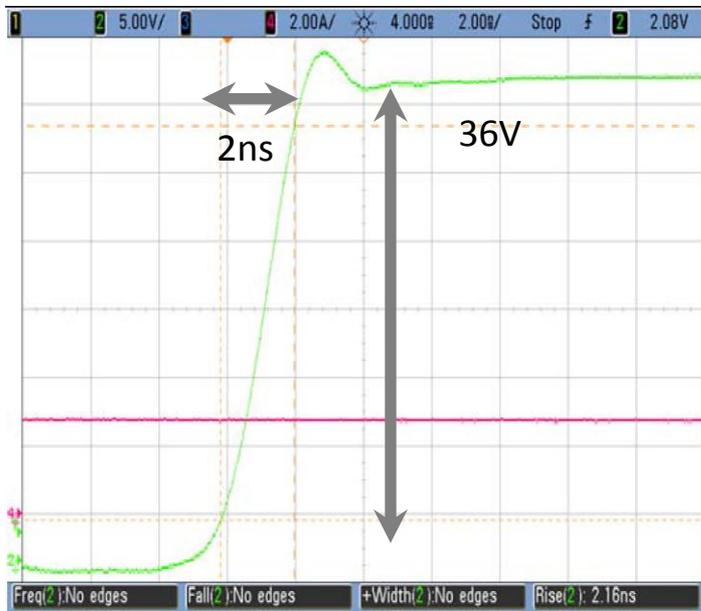
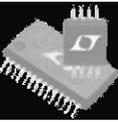


LT8614 – Silent Switcher

Efficiency vs. Switching Frequency




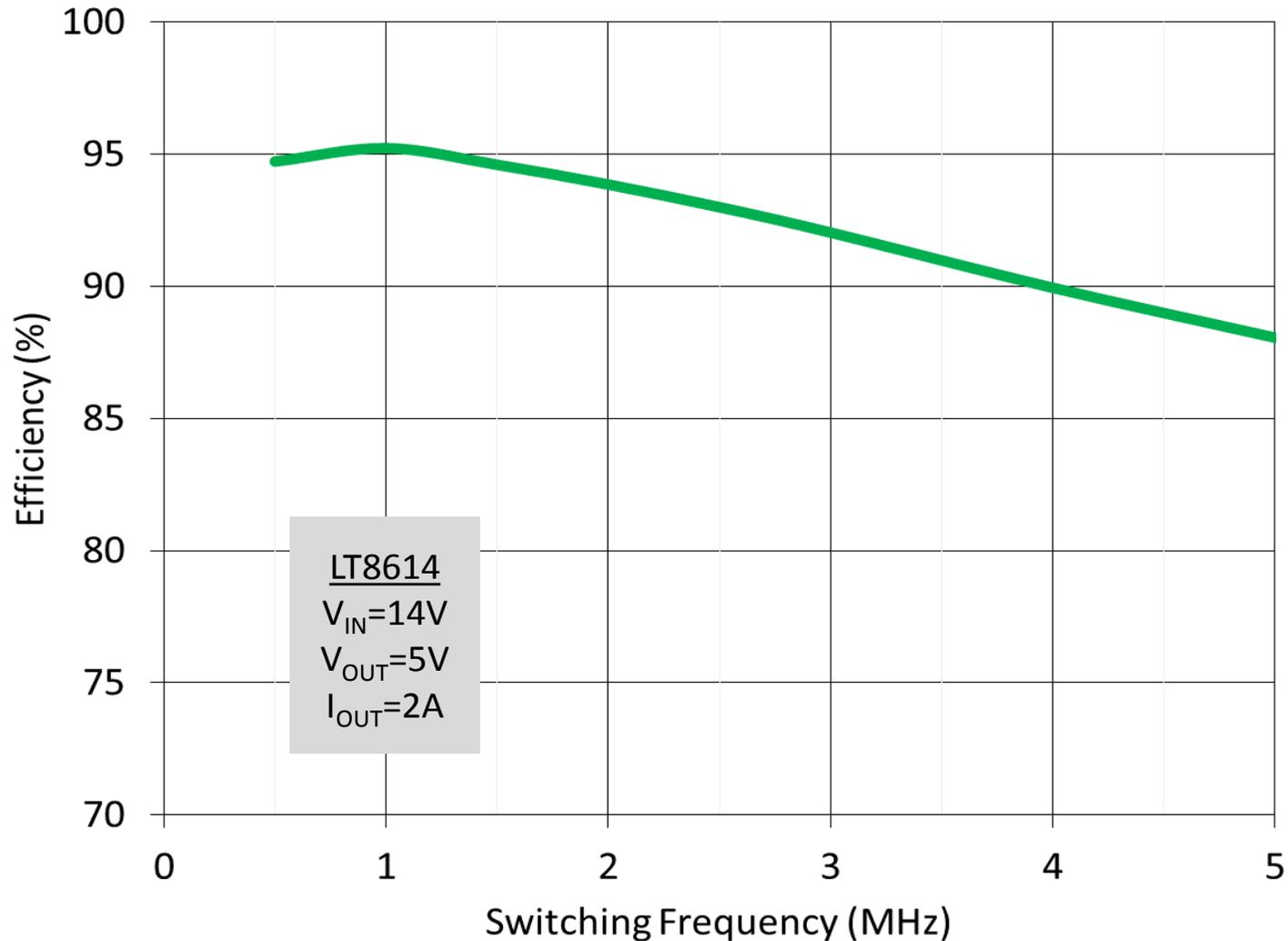
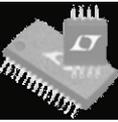


LT8614 – Silent Switcher

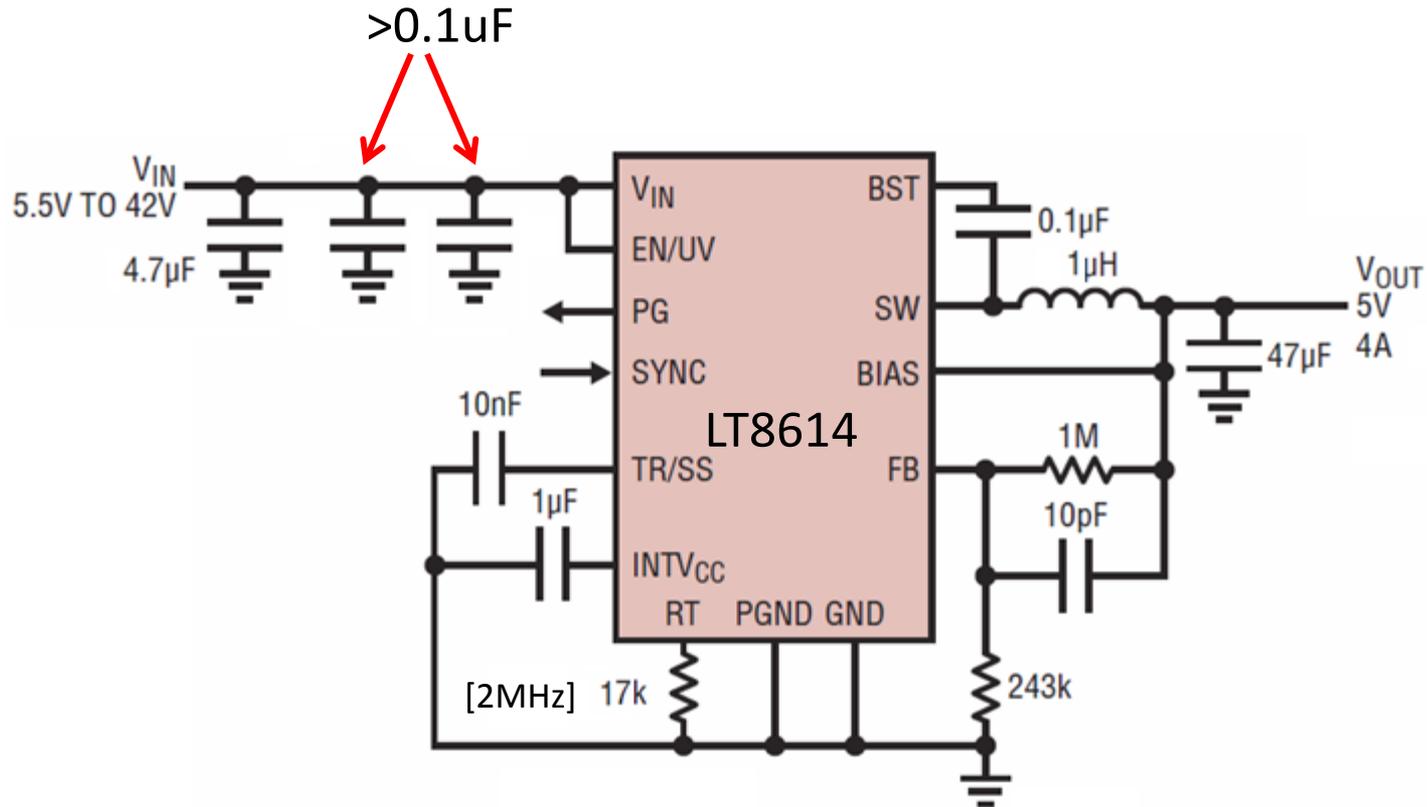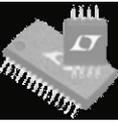


LT8614 Typical App

LT8614 EMI Performance

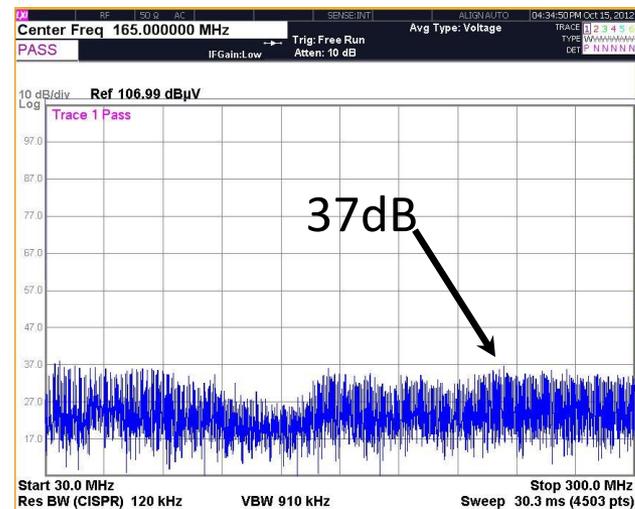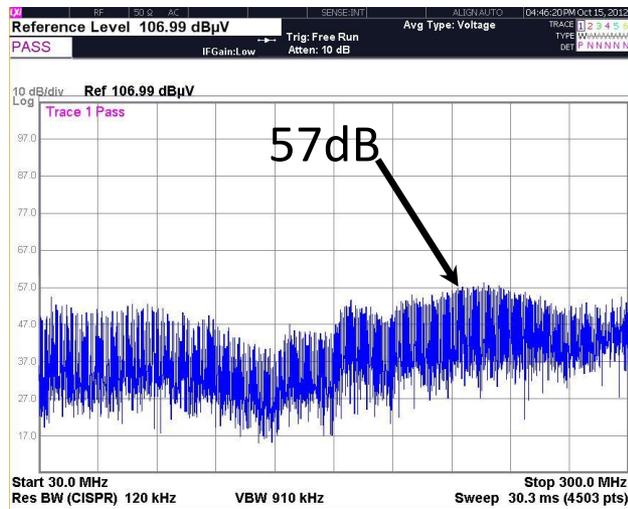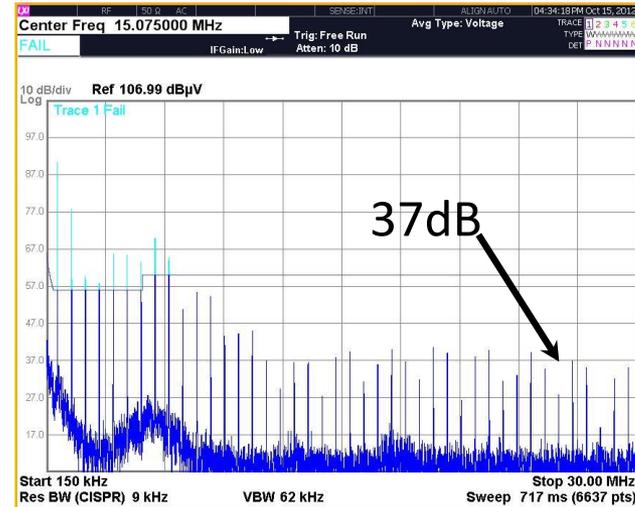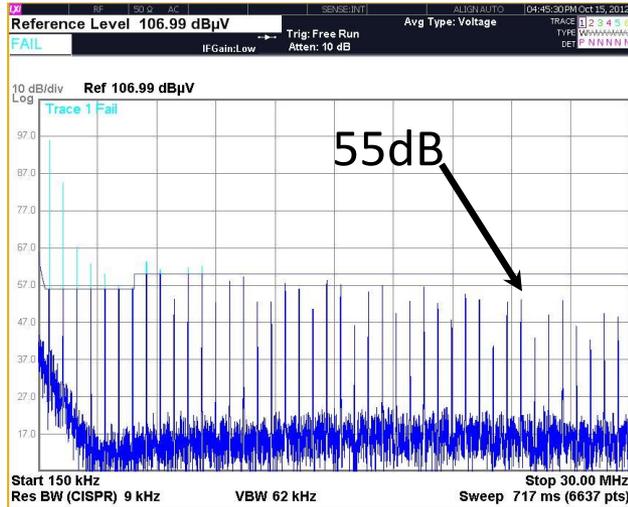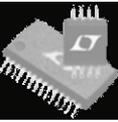

LT8610: 12V to 3.3V, 2A

LT8614: 12V to 3.3V, 2A

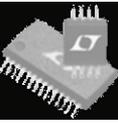

감사합니다.

